



Lab 6.

CPU Design

Instructors

Sergei Bykovskii, sergei_bykovskii@itmo.ru

Aglaia Ilina, agilina@itmo.ru



1. Stanislav Zhelnio,
<https://github.com/zhelnio/schoolRISCV>
2. David Money Harris and Sarah L Harris.
Digital Design and Computer Architecture
3. RISC-V Specification
<https://riscv.org/technical/specifications/>



- a simple processor core for practical teaching of the basics of digital circuit
- written in the Verilog language
- implements a subset of the RISCV architecture
- grew out of a similar schoolMIPS project




The features of schoolRISCV core

- One-cycle implementation
- Without data memory
- Word address of instruction memory
- Supports 9 instructions: **add, or, srl, sltu, sub, addi, lui, beq, bne**



The microarchitecture of the processor

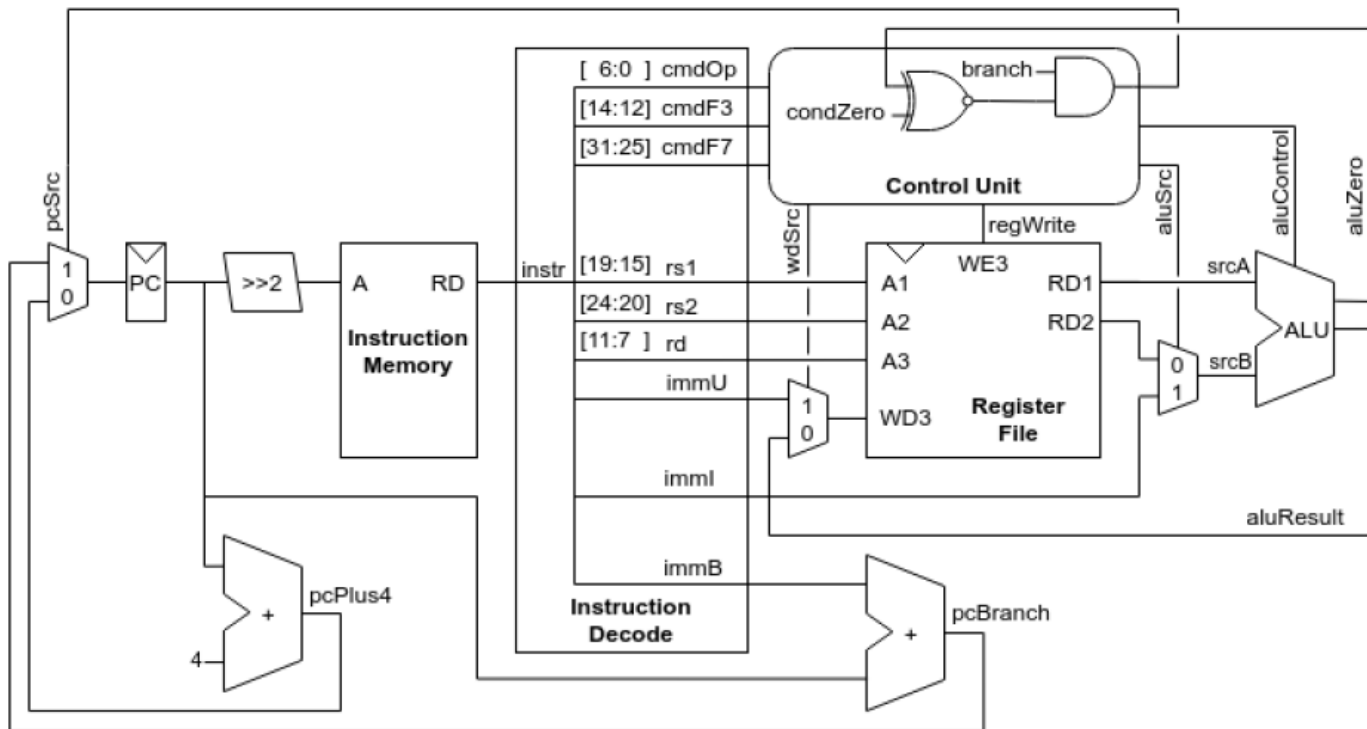



130

Volume I: RISC-V Unprivileged ISA V20191213



31	27	26	25	24	20	19	15	14	12	11	7	6	0	
funct7				rs2		rs1		funct3		rd		opcode		R-type
imm[11:0]						rs1		funct3		rd		opcode		I-type
imm[11:5]				rs2		rs1		funct3		imm[4:0]		opcode		S-type
imm[12 10:5]				rs2		rs1		funct3		imm[4 1 11]		opcode		B-type
imm[31:12]										rd		opcode		U-type
imm[20 10:1 11 19:12]										rd		opcode		J-type

RV32I Base Instruction Set

imm[31:12]				rd		0110111	LUI
imm[31:12]				rd		0010111	AUIPC
imm[20 10:1 11 19:12]				rd		1101111	JAL
imm[11:0]		rs1	000	rd		1100111	JALR
imm[12 10:5]	rs2	rs1	000	imm[4:1 11]	1100011	BEQ	
imm[12 10:5]	rs2	rs1	001	imm[4:1 11]	1100011	BNE	
imm[12 10:5]	rs2	rs1	100	imm[4:1 11]	1100011	BLT	
imm[12 10:5]	rs2	rs1	101	imm[4:1 11]	1100011	BGE	
imm[12 10:5]	rs2	rs1	110	imm[4:1 11]	1100011	BLTU	
imm[12 10:5]	rs2	rs1	111	imm[4:1 11]	1100011	BGEU	
imm[11:0]		rs1	000	rd		0000011	LB
imm[11:0]		rs1	001	rd		0000011	LH
imm[11:0]		rs1	010	rd		0000011	LW
imm[11:0]		rs1	100	rd		0000011	LBU
imm[11:0]		rs1	101	rd		0000011	LHU
imm[11:5]	rs2	rs1	000	imm[4:0]	0100011	SB	
imm[11:5]	rs2	rs1	001	imm[4:0]	0100011	SH	
imm[11:5]	rs2	rs1	010	imm[4:0]	0100011	SW	
imm[11:0]		rs1	000	rd		0010011	ADDI




ADDI: instruction fetching

  




ADDI: reading the operand

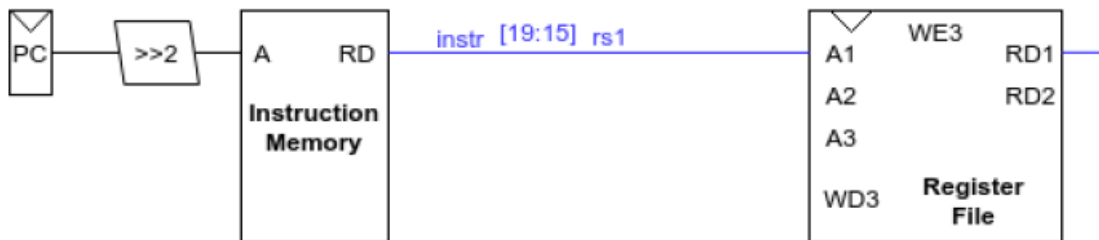


 ADDI: I-type, adds the sign-extended 12-bit immediate to register *rs1*: $rd = rs1 + imm1$






ADDI: decoding the constant

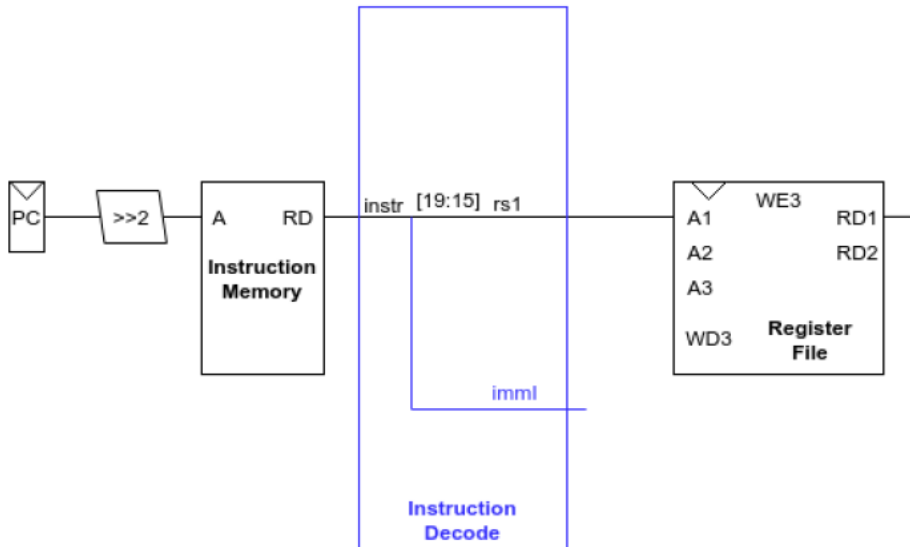


 ADDI: I-type, adds the sign-extended 12-bit immediate to register rs1: $rd = rs1 + imm$





ADDI: calculation the result

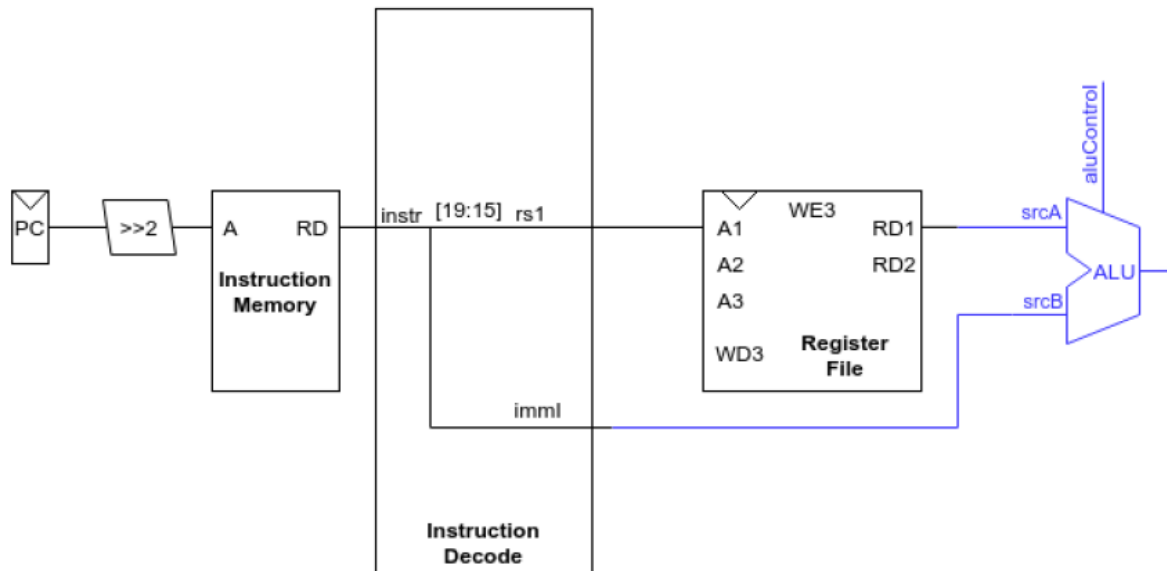


ADDI: I-type, adds the sign-extended 12-bit immediate to register rs1: $rd = rs1 + immi$






ADDI: decoding the destination address

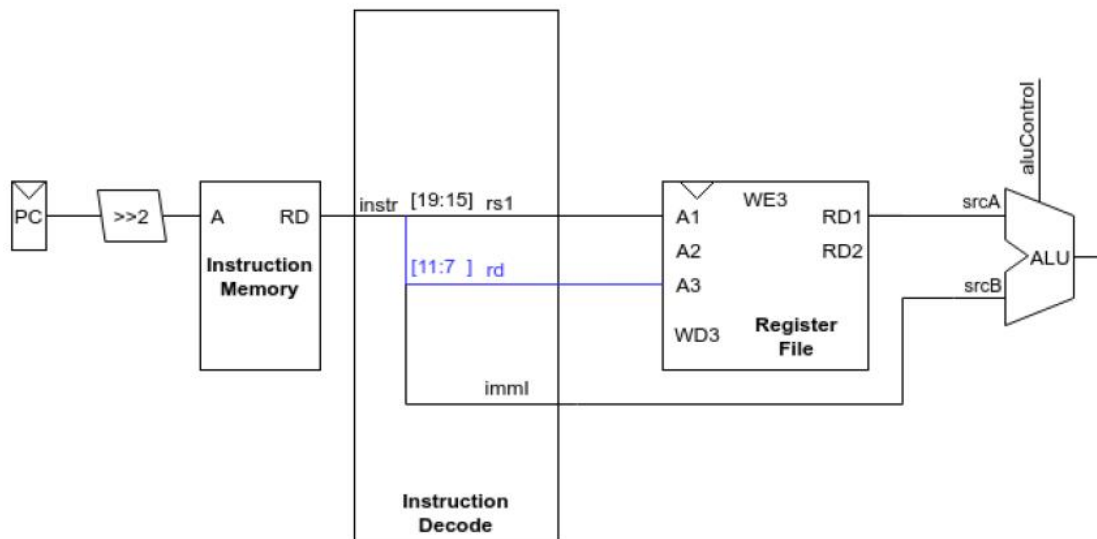


 ADDI: I-type, adds the sign-extended 12-bit immediate to register rs1: $rd = rs1 + imm1$





ADDI: writing the result

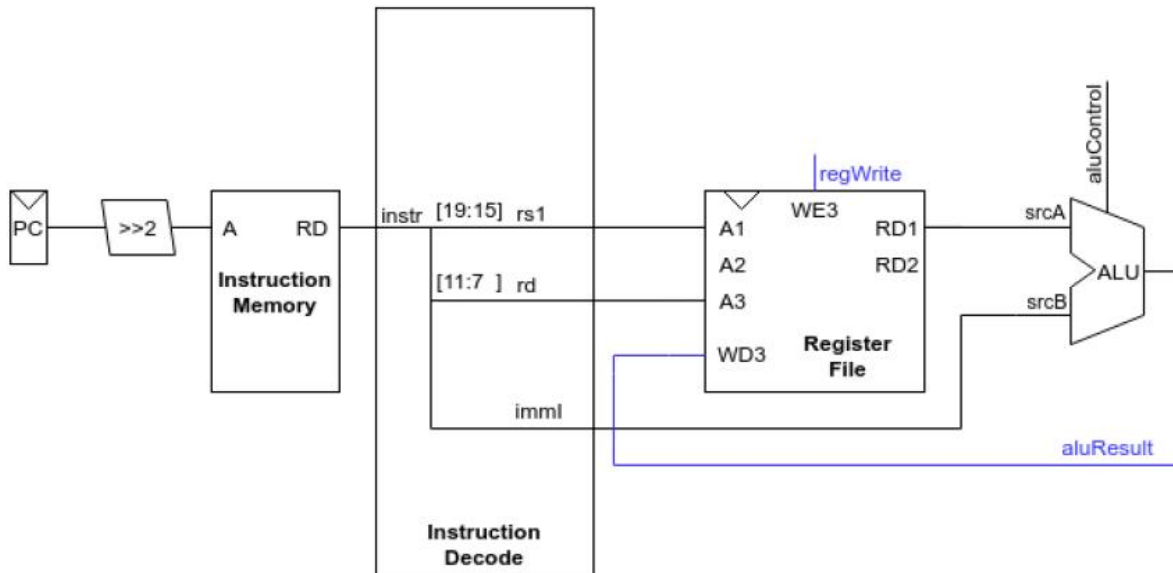


ADDI: I-type, adds the sign-extended 12-bit immediate to register rs1: $rd = rs1 + imm1$






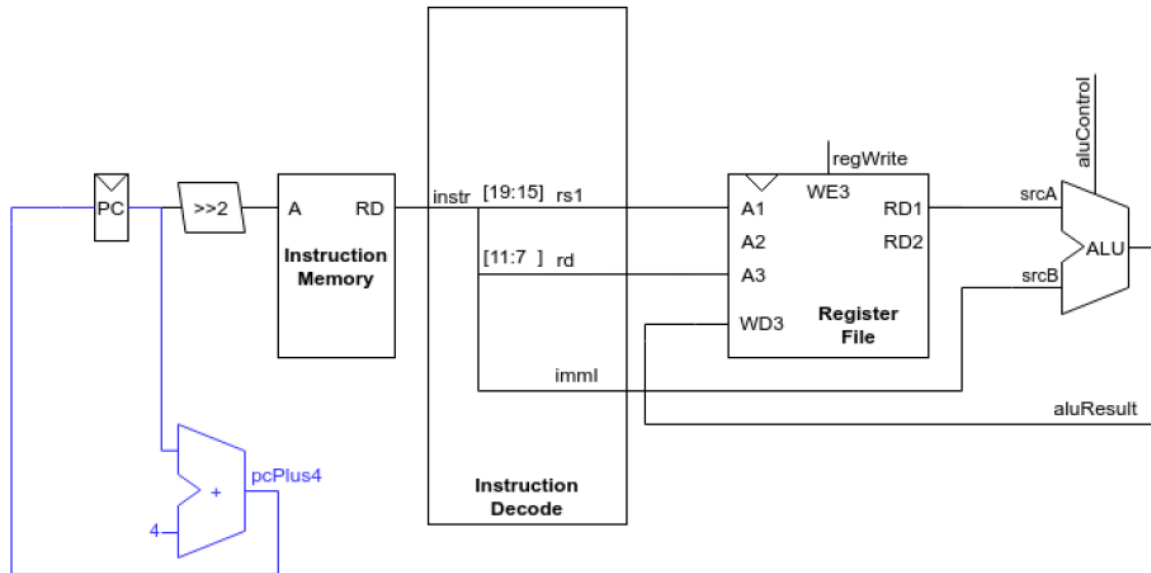ADDI: calculation the next instruction address




 ADDI: I-type, adds the sign-extended 12-bit immediate to register rs1: $rd = rs1 + imm1$






BEQ: branch address calculation

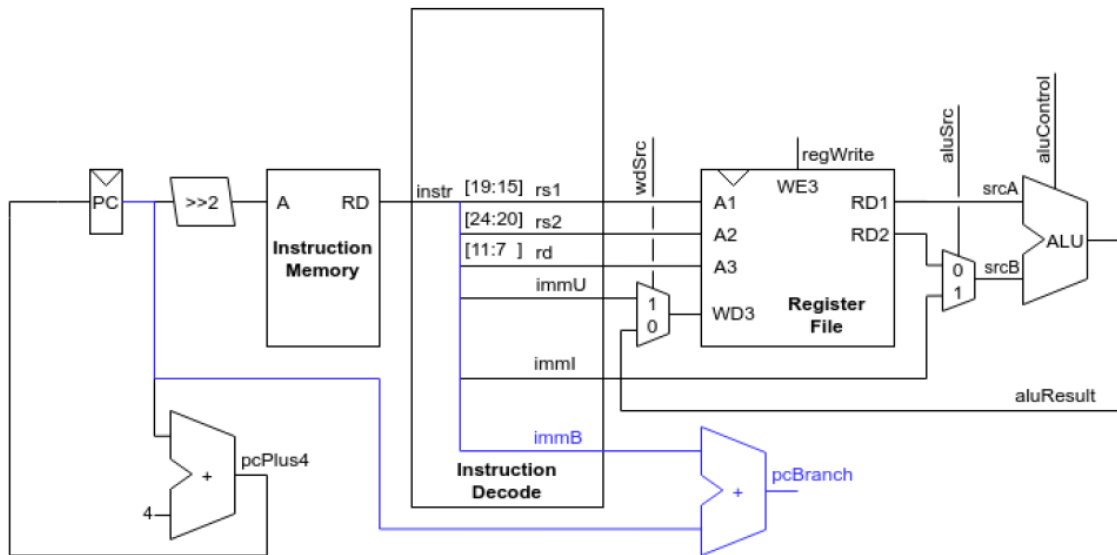


 BEQ: B-type, branch on equal: **if (rs1 == rs2) PC = PC + immB**






BEQ: address fetching

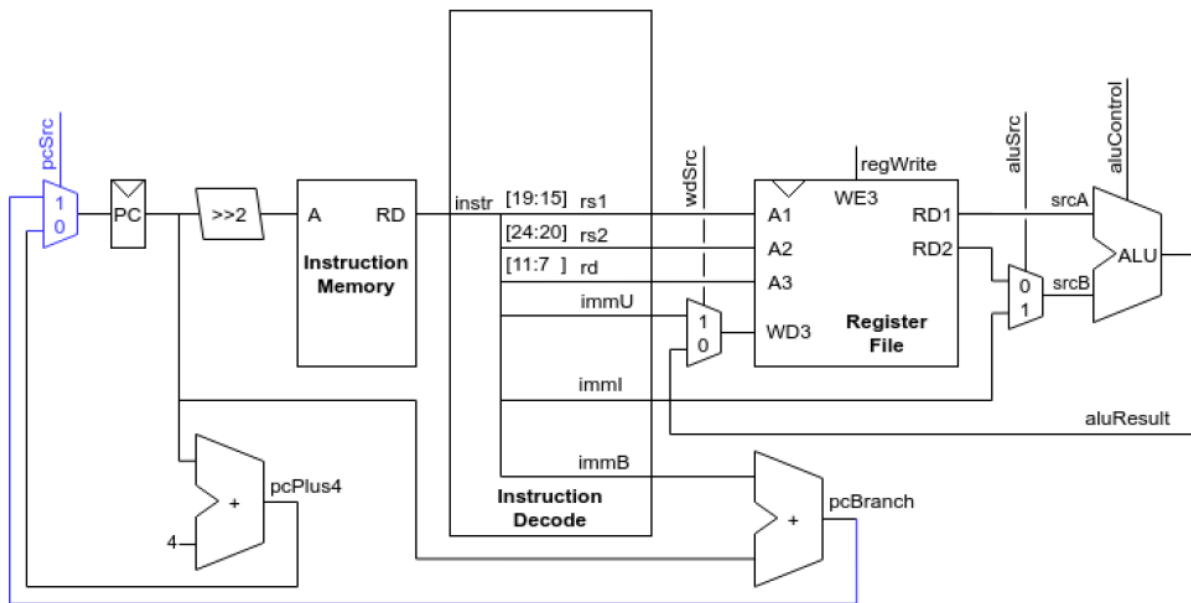


 BEQ: B-type, branch on equal: **if (rs1 == rs2) PC = PC + immB**






BEQ: check branch condition

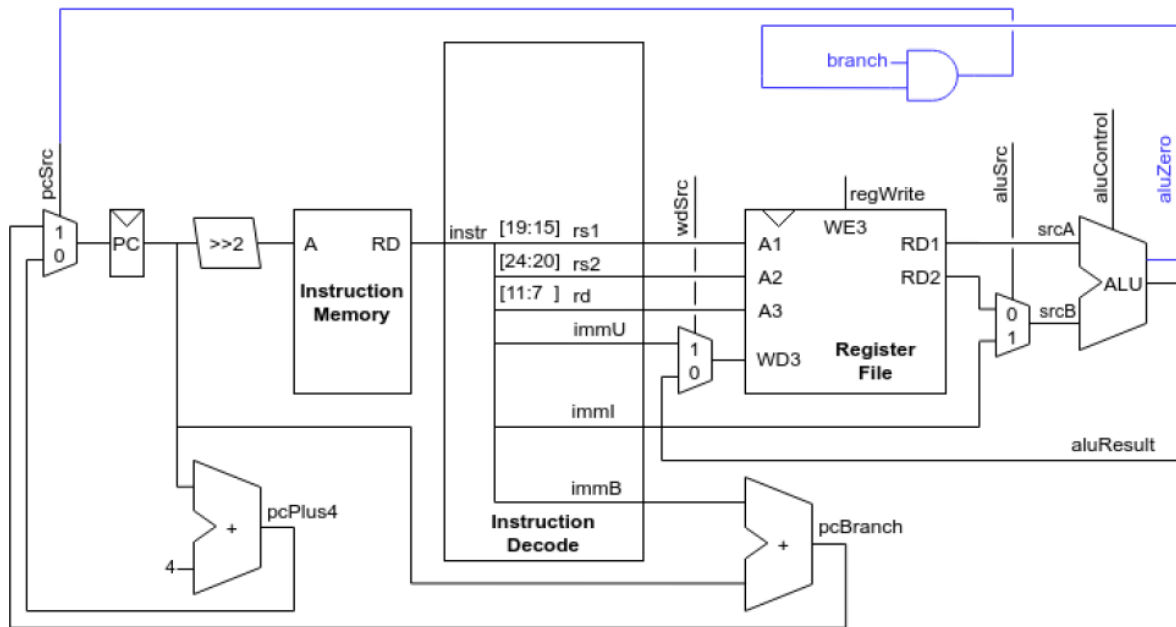

 BEQ: B-type, branch on equal: if (rs1 == rs2) PC = PC + immB





PC, adders and addresses multiplexors

```
// sm_register.v
module sm_register (
    input          clk,
    input          rst,
    input  [ 31 : 0 ] d,
    output reg [ 31 : 0 ] q
);
    always @ (posedge clk or negedge rst)
        if(~rst) q <= 32'b0;
        else    q <= d;
endmodule
```

```
// sr_cpu.v
wire [31:0] pc;
wire [31:0] pcBranch = pc + immB;
wire [31:0] pcPlus4   = pc + 4;
wire [31:0] pcNext    = pcSrc ? pcBranch : pcPlus4;
sm_register r_pc(clk ,rst_n, pcNext, pc);
```



Instruction memory

```
// sm_rom.v
module sm_rom
#(
    parameter SIZE = 64
)
(
    input  [31:0] a,
    output [31:0] rd
);
    reg [31:0] rom [SIZE - 1:0];
    assign rd = rom [a];

    initial begin
        $readmemh ("program.hex", rom);
    end

endmodule
```

```
// sm_top.v
sm_rom reset_rom(imAddr, imData);
```



Instruction decoder (1)

```
// sr_cpu.v
module sr_decode
(
    input      [31:0] instr,
    output     [ 6:0] cmdOp,
    output     [ 4:0] rd,
    output     [ 2:0] cmdF3,
    output     [ 4:0] rs1,
    output     [ 4:0] rs2,
    output     [ 6:0] cmdF7,
    output reg [31:0] immI,
    output reg [31:0] immB,
    output reg [31:0] immU
);

    assign cmdOp = instr[ 6: 0];
    assign rd   = instr[11: 7];
    assign cmdF3 = instr[14:12];
    assign rs1   = instr[19:15];
    assign rs2   = instr[24:20];
    assign cmdF7 = instr[31:25];
```



Instruction decoder (2)

```
// I-immediate
always @ (*) begin
    immI[10: 0] = instr[30:20];
    immI[31:11] = { 21 {instr[31]} };
end

// B-immediate
always @ (*) begin
    immB[ 0] = 1'b0;
    immB[ 4: 1] = instr[11:8];
    immB[10: 5] = instr[30:25];
    immB[31:11] = { 21 {instr[31]} };
end

// U-immediate
always @ (*) begin
    immU[11: 0] = 12'b0;
    immU[31:12] = instr[31:12];
end
endmodule
```



Register file

```
// sr_cpu.v
module sm_register_file
(
    input          clk,
    input  [ 4:0]  a0,
    input  [ 4:0]  a1,
    input  [ 4:0]  a2,
    input  [ 4:0]  a3,
    output [31:0]  rd0,
    output [31:0]  rd1,
    output [31:0]  rd2,
    input  [31:0]  wd3,
    input          we3
);
    reg [31:0] rf [31:0];

    assign rd0 = (a0 != 0) ? rf [a0] : 32'b0;
    assign rd1 = (a1 != 0) ? rf [a1] : 32'b0;
    assign rd2 = (a2 != 0) ? rf [a2] : 32'b0;

    always @ (posedge clk)
        if(we3) rf [a3] <= wd3;
endmodule
```



ALU operation

```
// sr_cpu.vh

`define ALU_ADD      3'b000  // A + B

`define ALU_OR       3'b001  // A | B

`define ALU_SRL      3'b010  // A >> B

`define ALU_SLTU     3'b011  // A < B ? 1 : 0

`define ALU_SUB      3'b100  // A - B
```



ALU implementation

```
// sr_cpu.v
module sr_alu
(
    input  [31:0] srcA,
    input  [31:0] srcB,
    input  [ 2:0] oper,
    output          zero,
    output reg [31:0] result
);
    always @ (*) begin
        case (oper)
            default      : result = srcA + srcB;
            `ALU_ADD     : result = srcA + srcB;
            `ALU_OR      : result = srcA | srcB;
            `ALU_SRL     : result = srcA >> srcB [4:0];
            `ALU_SLTU    : result = (srcA < srcB) ? 1 : 0;
            `ALU_SUB     : result = srcA - srcB;
        endcase
    end

    assign zero = (result == 0);
endmodule
```



Data multiplexors

```
// sr_cpu.v  
wire [31:0] srcB = aluSrc ? immI : rd2;
```

```
// sr_cpu.v  
assign wd3 = wdSrc ? immU : aluResult;
```




Control unit (1)

```
// sr_cpu.v
module sr_control
(
    input      [ 6:0] cmdOp,
    input      [ 2:0] cmdF3,
    input      [ 6:0] cmdF7,
    input      aluZero,
    output      pcSrc,
    output reg   regWrite,
    output reg   aluSrc,
    output reg   wdSrc,
    output reg [2:0] aluControl
);
    reg          branch;
    reg          condZero;
    assign pcSrc = branch & (aluZero == condZero);
```



Control unit (2)

```
// sr_cpu.v
always @ (*) begin
    branch      = 1'b0;
    condZero    = 1'b0;
    regWrite    = 1'b0;
    aluSrc      = 1'b0;
    wdSrc       = 1'b0;
    aluControl  = `ALU_ADD;

    casez( {cmdF7, cmdF3, cmdOp} )
        { `RVF7_ADD, `RVF3_ADD, `RVOP_ADD } : begin regWrite = 1'b1; aluControl = `ALU_ADD; end
        { `RVF7_OR, `RVF3_OR, `RVOP_OR } : begin regWrite = 1'b1; aluControl = `ALU_OR; end
        { `RVF7_SRL, `RVF3_SRL, `RVOP_SRL } : begin regWrite = 1'b1; aluControl = `ALU_SRL; end
        { `RVF7_SLTU, `RVF3_SLTU, `RVOP_SLTU } : begin regWrite = 1'b1; aluControl = `ALU_SLTU; end
        { `RVF7_SUB, `RVF3_SUB, `RVOP_SUB } : begin regWrite = 1'b1; aluControl = `ALU_SUB; end

        { `RVF7_ANY, `RVF3_ADDI, `RVOP_ADDI } : begin regWrite = 1'b1; aluSrc = 1'b1; aluControl = `ALU_ADD; end
        { `RVF7_ANY, `RVF3_ANY, `RVOP_LUI } : begin regWrite = 1'b1; wdSrc = 1'b1; end

        { `RVF7_ANY, `RVF3_BEQ, `RVOP_BEQ } : begin branch = 1'b1; condZero = 1'b1; aluControl = `ALU_SUB; end
        { `RVF7_ANY, `RVF3_BNE, `RVOP_BNE } : begin branch = 1'b1; aluControl = `ALU_SUB; end
    endcase
end
```