

Functional electronic circuits

Laboratory work 2 «Design of data path functional blocks»

1. Develop three types of implementations for device: one-cycle, multi-cycle, pipelined. The device should perform the function according to the variant. The signal interface is presented in Figure 1 and contents such signals as:
 - 1.1. **x** – 32 bit input value;
 - 1.2. **start** – signal to start calculation;
 - 1.3. **rst** – reset signal;
 - 1.4. **clk** – clock signal;
 - 1.5. **y** – the 32 bit result value;
 - 1.6. **rdy** – the ready signal. It is asserted when the device is ready for computation.

 


Figure 1 The developing systems

2. Develop a testbench of the device and test the device.
3. Calculate the calculation time of each implementation.
4. Draw a microarchitecture of your device.
5. Put results in the report. The report should consist:
 - 5.1. Student Name and Student ID
 - 5.2. The picture with microarchitecture of each implementation
 - 5.3. The timing diagram with simulation results
 - 5.4. Code of the testbench and the device.
6. Upload the report by this form: <https://forms.yandex.ru/u/64425ea1c09c0201fdb452ec/>

Variants

№	Device function	№	Device function	№	Device function
0	$y = x^4 + x$	2	$y = x^3 + x^2$	4	$y = x^4 + x^3$
1	$y = x^2 + x^5$	3	$y = x^5 + x^3$	5	$y = x^2 + x^4$
6	$y =$	7		8	
9		10		11	