

Functional Electronic Circuits Lab4

Student Name: CAO Xinyang


Student ID: 20321308

1. The picture of the system

 

 

 2. The timing diagram with simulation results



3. Code of the testbench and the device

busDevice.v

```
module bus(
    input [31:0] HADDR MASTER bi,
    input [31:0] HWDATA_MASTER_bi,
    input HWRITE MASTER i,
    output reg [31:0] HRDATA_MASTER_bo,
   output [31:0] HADDR_SLAVE_1_bo,
   output [31:0] HWDATA_SLAVE_1_bo,
    output reg HWRITE SLAVE 1 o,
    input [31:0] HRDATA_SLAVE_1_bi,
    output [31:0] HADDR SLAVE 2 bo,
   output [31:0] HWDATA_SLAVE_2_bo,
    output reg HWRITE SLAVE 2 o,
    input [31:0] HRDATA_SLAVE_2_bi
);
assign HADDR_SLAVE_1_bo = HADDR_MASTER_bi;
assign HADDR_SLAVE_2_bo = HADDR_MASTER_bi;
assign HWDATA SLAVE 1 bo = HWDATA MASTER bi;
assign HWDATA_SLAVE_2_bo = HWDATA_MASTER_bi;
always@*
    if (HADDR_MASTER_bi < 32'h80) begin</pre>
        HWRITE_SLAVE_1_o <= HWRITE_MASTER_i;</pre>
        HRDATA MASTER bo <= HRDATA SLAVE 1 bi;
    end else begin
        HWRITE SLAVE 2 o <= HWRITE MASTER i;
        HRDATA_MASTER_bo <= HRDATA_SLAVE_2_bi;</pre>
    end
endmodule
```

masterDevice.v

```
module master(
```

```
input HCLK_i,
    input HRESETn_i,
    input [31:0] HRDATA_bi,
    output reg [31:0] HADDR_bo,
    output reg [31:0] HWDATA_bo,
    output reg HWRITE_o
);
task write(
    input [31:0] addr,
    input [31:0] data
);
    begin
        @(posedge HCLK_i);
        HADDR bo <= addr;</pre>
        HWRITE_o <= 1;</pre>
        HWDATA_bo <= data;</pre>
        @(posedge HCLK_i);
        @(posedge HCLK_i);
        HWRITE_o <= 0;</pre>
    end
endtask
task read(
    input [31:0] addr
);
    begin
        @(posedge HCLK_i);
        HADDR_bo <= addr;</pre>
        HWRITE o <= 0;
        @(posedge HCLK_i);
        @(posedge HCLK_i);
        $display("READ DATA | addr: %h, data: %h", addr, HRDATA_bi);
endtask
initial begin
    write(32'h5, 32'h55AA);
    read(32'hA);
    read(32'h5);
    write(32'h80, 32'hAA55);
    read(32'h81);
    read(32'h80);
    $finish;
end
```

slaveDevice.v

```
module slave(
    input HCLK_i,
    input HRESETn_i,
    output reg [31:0] HRDATA_bo,
    input [31:0] HADDR_bi,
    input [31:0] HWDATA_bi,
    input HWRITE_i
);
reg [31:0] mem [255:0];
always@(posedge HCLK_i)
    if (HRESETn_i == 0)
        HRDATA_bo <= 0;</pre>
    else begin
        if (HWRITE i)
            mem[HADDR_bi] <= HWDATA_bi;</pre>
        else
            HRDATA_bo <= mem[HADDR_bi];</pre>
    end
endmodule
```

testBench.v

```
timescale 1ns/1ps
module lab4 tb;
reg clk, rst;
wire [31:0] HRDATA, HADDR, HWDATA;
wire HWRITE;
wire [31:0] HRDATA_SLAVE_1, HADDR_SLAVE_1, HWDATA_SLAVE_1;
wire HWRITE SLAVE 1;
wire [31:0] HRDATA_SLAVE_2, HADDR_SLAVE_2, HWDATA_SLAVE_2;
wire HWRITE SLAVE 2;
bus buut (
    .HADDR_MASTER_bi(HADDR),
    .HWDATA_MASTER_bi(HWDATA),
    .HRDATA_MASTER_bo(HRDATA),
    .HWRITE_MASTER_i(HWRITE),
    .HADDR_SLAVE_1_bo(HADDR_SLAVE_1),
    .HWDATA_SLAVE_1_bo(HWDATA_SLAVE_1),
```

```
.HRDATA_SLAVE_1_bi(HRDATA_SLAVE_1),
    .HWRITE_SLAVE_1_o(HWRITE_SLAVE_1),
    .HADDR_SLAVE_2_bo(HADDR_SLAVE_2),
    .HWDATA SLAVE 2 bo(HWDATA SLAVE 2),
    .HRDATA SLAVE 2 bi(HRDATA SLAVE 2),
    .HWRITE_SLAVE_2_o(HWRITE_SLAVE_2)
);
master muut(
    .HCLK i(clk),
    .HRESETn_i(rst),
    .HRDATA_bi(HRDATA),
    .HADDR_bo(HADDR),
    .HWDATA_bo(HWDATA),
    .HWRITE o(HWRITE)
);
slave suut1(
    .HCLK_i(clk),
    .HRESETn_i(rst),
    .HRDATA_bo(HRDATA_SLAVE_1),
    .HADDR_bi(HADDR_SLAVE_1),
    .HWDATA bi(HWDATA SLAVE 1),
    .HWRITE_i(HWRITE_SLAVE_1)
);
slave suut2(
    .HCLK i(clk),
    .HRESETn_i(rst),
    .HRDATA_bo(HRDATA_SLAVE_2),
    .HADDR_bi(HADDR_SLAVE_2),
    .HWDATA_bi(HWDATA_SLAVE_2),
    .HWRITE i(HWRITE SLAVE 2)
);
always #5 clk = \simclk;
initial begin
   $dumpfile("time.vcd");
   $dumpvars(1, lab4_tb);
   clk = 0;
   rst = 0;
    #20
    rst = 1;
end
```