



Laboratory Work 3

Active filter circuits design and simulation

Nikolay Nikolaev

(nanikolaev@itmo.ru)

Nikolai Poliakov

(polyakov_n_a@itmo.ru)

Roman Olekhnovich

(r.o.olekhnovich@mail.ru)

1. Filter approximation theory review
2. Laboratory work 3: ideal and real amplifier comparison
3. Active filter circuits design
4. Second Order Filters
5. Frequency Transformation
6. Step 1: check of scheme gain
7. Step 2: time domain simulation
8. Step 3: Step response (time domain simulation)
9. Step 4: frequency domain simulation)
10. Results and conclusions
11. Uploading report

parameters that fully describe the filter transfer function

$$\{H_o, H_C, H_S, \Omega_S\} \quad (\Omega_C = 1)$$


In terms of logarithmic gain

$$\{\alpha_o, \alpha_{\max}, \alpha_{\min}, \Omega_S\} \quad (\Omega_C = 1)$$


If $H_o = 1$, the filter requirements can be determined by three parameters

$$\Omega_S \quad \text{and} \quad \{H_C, H_S\} \quad \text{or} \quad \{\alpha_{\max}, \alpha_{\min}\}$$

Plain gain

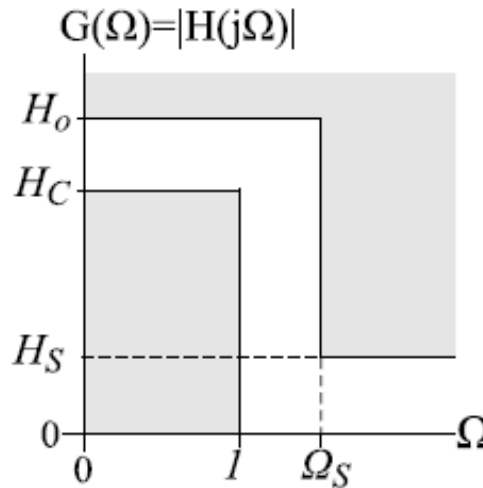

Logarithmic gain

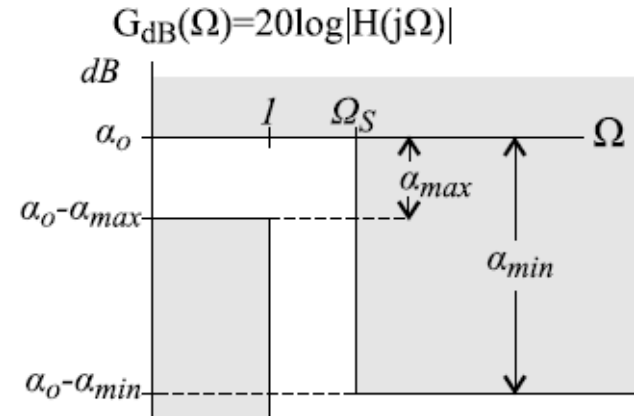

Butterworth proposed the monotonic function

$$G(\Omega) = \frac{H_o}{\sqrt{1 + \beta^2 \Omega^{2N}}}$$

with N , the order of the approximation, a positive integer, and β a design parameter related to the passband tolerance.

$$G(\Omega) = \frac{H_o}{\sqrt{1 + \beta^2 \Omega^{2N}}}$$


For $\Omega = 0$

$$G(0) = H_o$$


$$G(1) = \frac{H_o}{\sqrt{1 + \beta^2}} \geq H_C \quad \Leftrightarrow \quad \beta^2 \leq (H_o/H_C)^2 - 1$$

$$\beta \leq \beta_{\max} = \sqrt{\left(\frac{H_o}{H_C}\right)^2 - 1} = \sqrt{10^{\frac{a_{\max}}{10}} - 1}$$

Plain gain

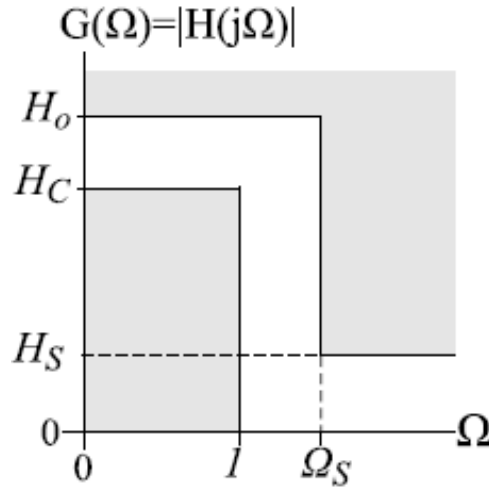

Logarithmic gain

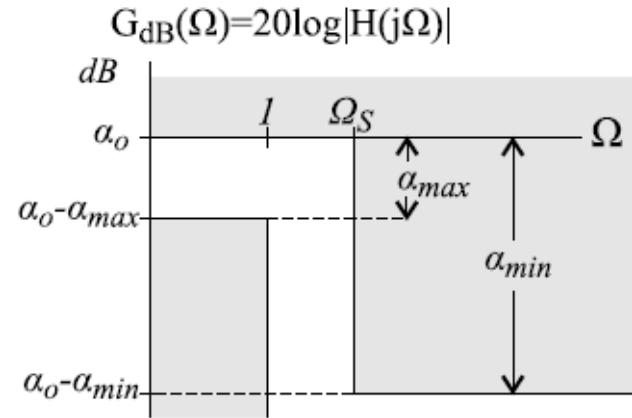


For $\beta = \beta_{\max}$ the gain $G(1) = H_C$

The Butterworth Approximation

$$G(\Omega) = \frac{H_o}{\sqrt{1 + \beta^2 \Omega^{2N}}}$$
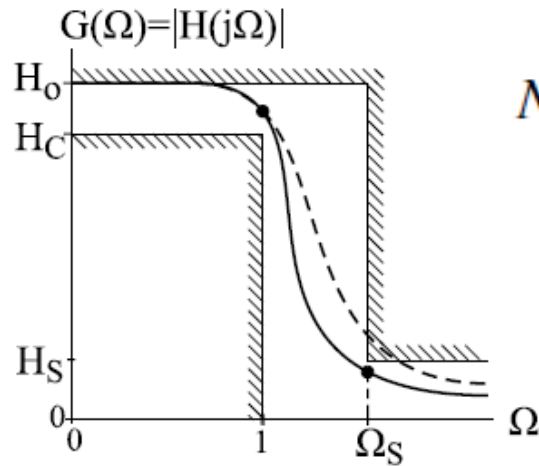
$$G(\Omega_S) = \frac{H_o}{\sqrt{1 + \beta^2 \Omega_S^{2N}}} \leq H_S$$





$$N \geq \frac{\log\left(\frac{(H_o/H_S)^2 - 1}{\beta^2}\right)}{2 \log \Omega_S}$$

$$N \geq N_d = \frac{\log\left(\frac{(H_o/H_S)^2 - 1}{\beta^2}\right)}{2 \log \Omega_S}$$

$$n_{f \min} = \frac{\log\left(\frac{\frac{H_o^2}{H_S^2} - 1}{\frac{H_o^2}{H_C^2} - 1}\right)}{2 \log \Omega_S} = \frac{\log\left(\frac{10^{\frac{a_{\min}}{10}} - 1}{10^{\frac{a_{\max}}{10}} - 1}\right)}{2 \log \Omega_S}$$

The Butterworth Approximation

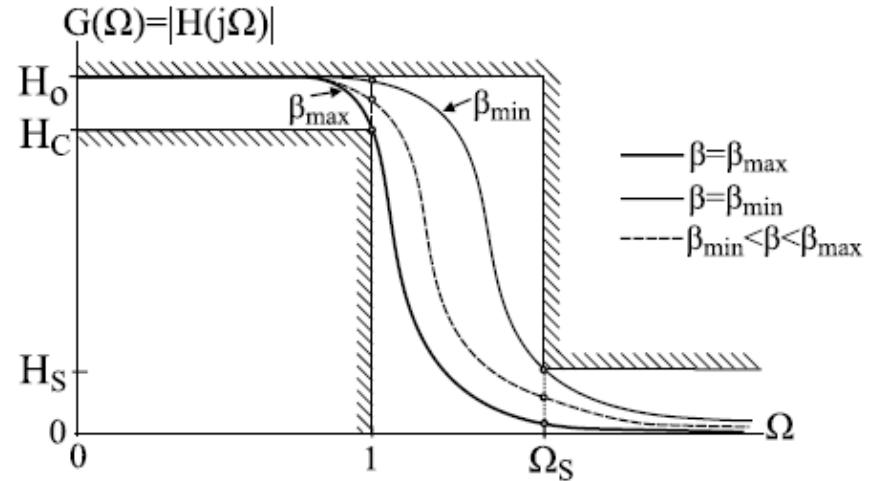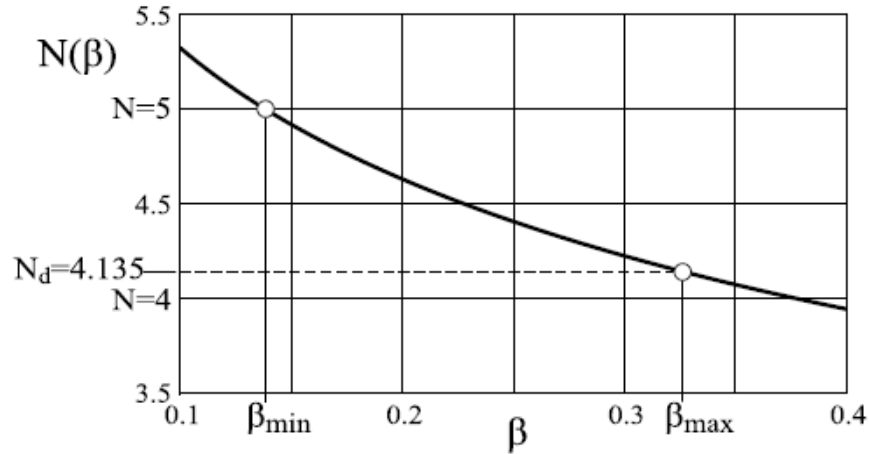


filter designed with normalized specifications

$$H_o = 1, H_C = 0.95, H_S = 0.05 \text{ and } \Omega_S = 2.7$$

$$\beta_{\min} = \frac{\sqrt{\frac{H_o^2}{H_S^2} - 1}}{\Omega_S^N} \leq \beta \leq \sqrt{\frac{H_o^2}{H_C^2} - 1} = \beta_{\max}$$

$$\beta_{\min} = \frac{\sqrt{10^{\frac{\alpha_{\min}}{10}} - 1}}{\Omega_S^N} \leq \beta \leq \sqrt{10^{\frac{\alpha_{\max}}{10}} - 1} = \beta_{\max}$$

The Butterworth Approximation

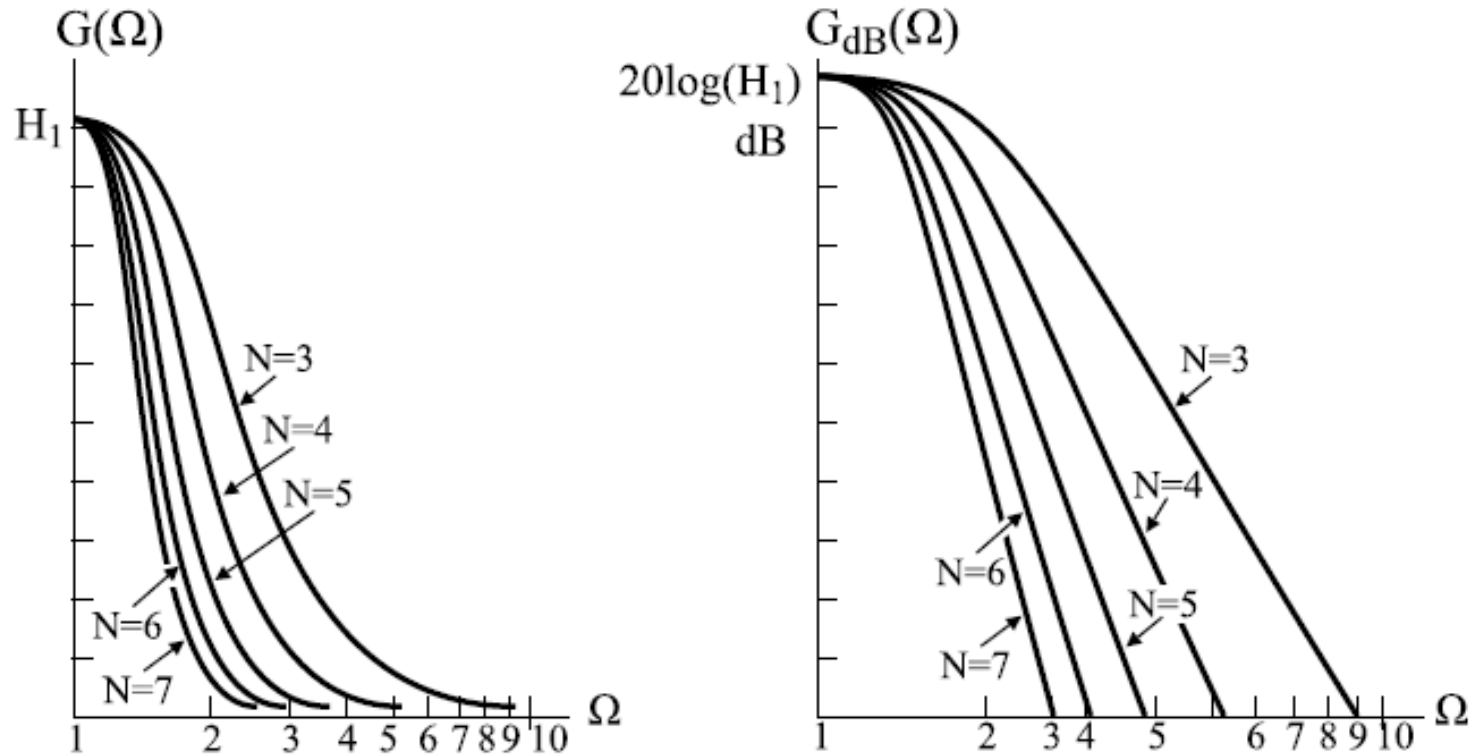

parameters that fully describe the filter transfer function

$$\{H_o, H_C, H_S, \Omega_S\} \quad (\Omega_C = 1)$$


In terms of logarithmic gain

$$\{\alpha_o, \alpha_{\max}, \alpha_{\min}, \Omega_S\} \quad (\Omega_C = 1)$$

If $H_o = 1$, the filter requirements can be determined by three parameters

$$\Omega_S \quad \text{and} \quad \{H_C, H_S\} \quad \text{or} \quad \{\alpha_{\max}, \alpha_{\min}\}$$


Plain gain

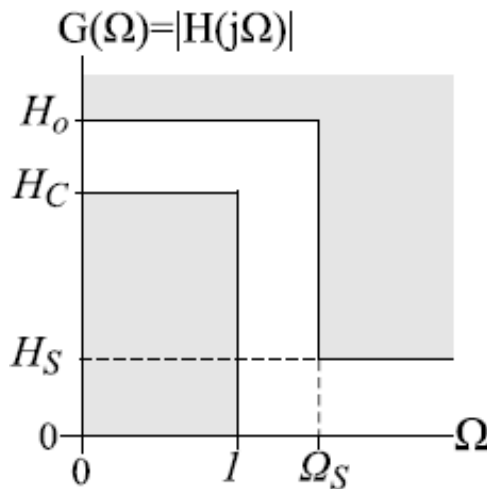

Chebyshev approximation

$$G_{CH}(\Omega) = \frac{H_o}{\sqrt{1 + \varepsilon^2 C_N^2(\Omega)}}$$

Logarithmic gain

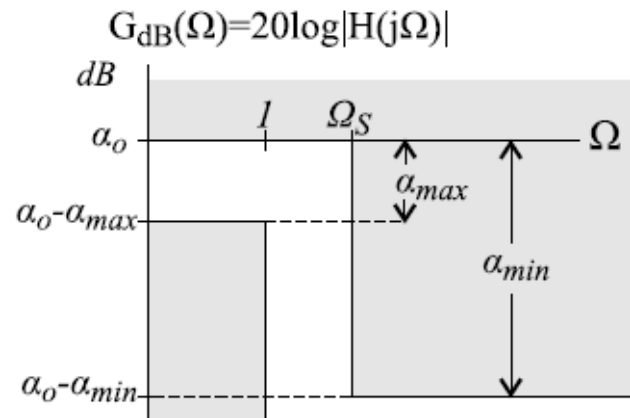

The ripple factor ε and order N are so chosen to keep the response $G_{CH}(\Omega)$ within the specifications.

$$G_{CH}(\Omega) = \frac{H_o}{\sqrt{1 + \varepsilon^2 C_N^2(\Omega)}}$$



$$\varepsilon \leq \sqrt{\frac{H_o^2}{H_C^2} - 1} = \sqrt{10^{\frac{\alpha_{\max}}{10}} - 1} = \varepsilon_{\max}$$

For $\varepsilon \leq \varepsilon_{\max}$

$$H_o \geq G_{CH}(\Omega) \geq \frac{H_o}{\sqrt{1 + \varepsilon^2}} \geq H_C$$

For $\Omega = 1$
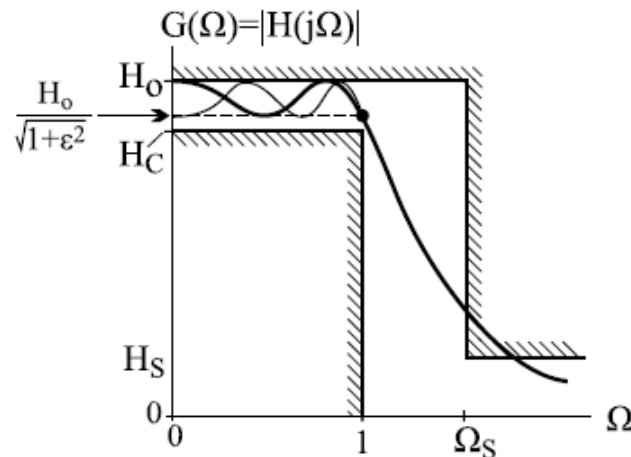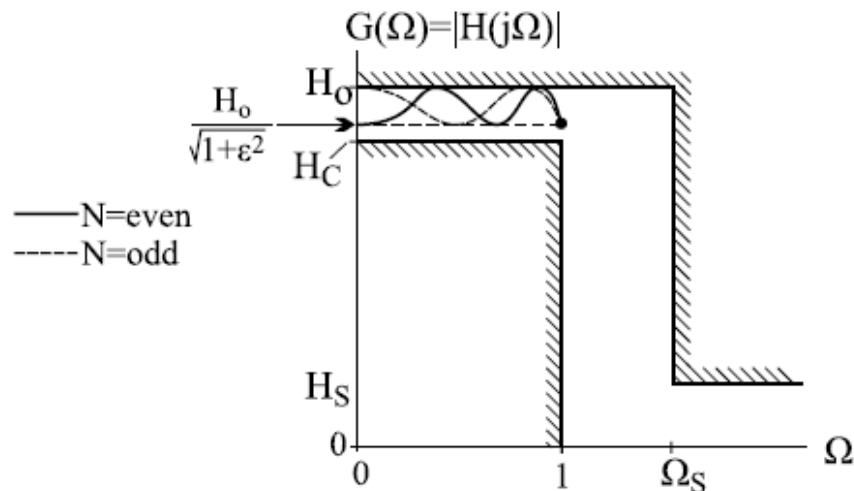
$$G_{CH}(1) = \frac{H_o}{\sqrt{1 + \varepsilon^2}} \geq H_C$$



$$G_{CH}(\Omega_S) = \frac{H_o}{\sqrt{1 + \varepsilon^2 C_N^2(\Omega_S)}} \leq H_S$$


$$\Leftrightarrow C_N^2(\Omega_S) \geq \frac{(H_o/H_S)^2 - 1}{\varepsilon^2}$$

$$\Leftrightarrow N \cosh^{-1}(\Omega_S) \geq \cosh^{-1} \sqrt{\frac{(H_o/H_S)^2 - 1}{\varepsilon^2}}$$



for N: $N \geq N_d = \frac{\cosh^{-1}(\sqrt{\frac{(H_o/H_S)^2 - 1}{\varepsilon^2}})}{\cosh^{-1}(\Omega_S)}$

$$N \geq N_d = \frac{\cosh^{-1}(\sqrt{\frac{(H_o/H_S)^2 - 1}{\varepsilon_{\max}^2}})}{\cosh^{-1}(\Omega_S)} = \frac{\cosh^{-1}(\sqrt{\frac{(H_o/H_S)^2 - 1}{(H_o/H_C)^2 - 1}})}{\cosh^{-1}(\Omega_S)}$$



logarithmic gain
specifications

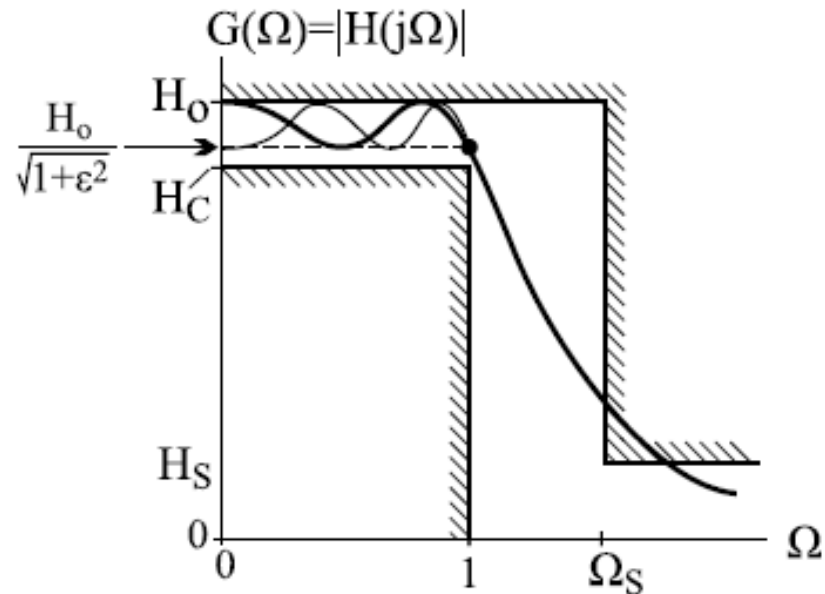

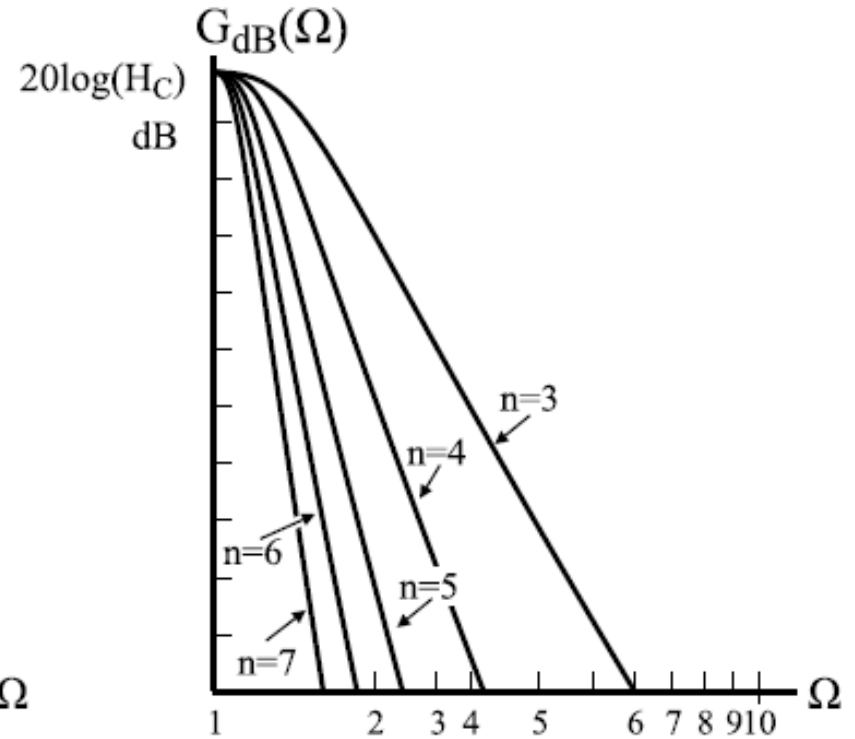
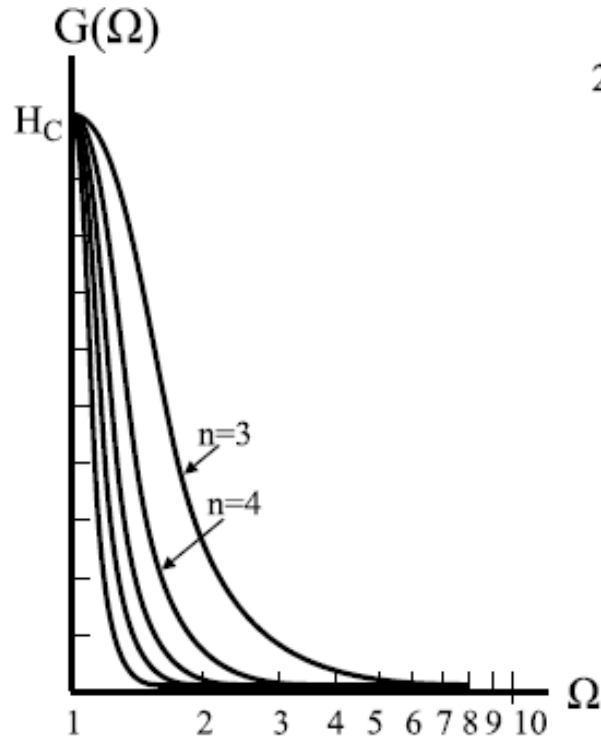
$$N \geq N_d = \frac{\cosh^{-1}(\sqrt{\frac{10^{\frac{\alpha_{\min}}{10}} - 1}{10^{\frac{\alpha_{\max}}{10}} - 1}})}{\cosh^{-1}(\Omega_S)}$$



Comparison of Amplitude Response

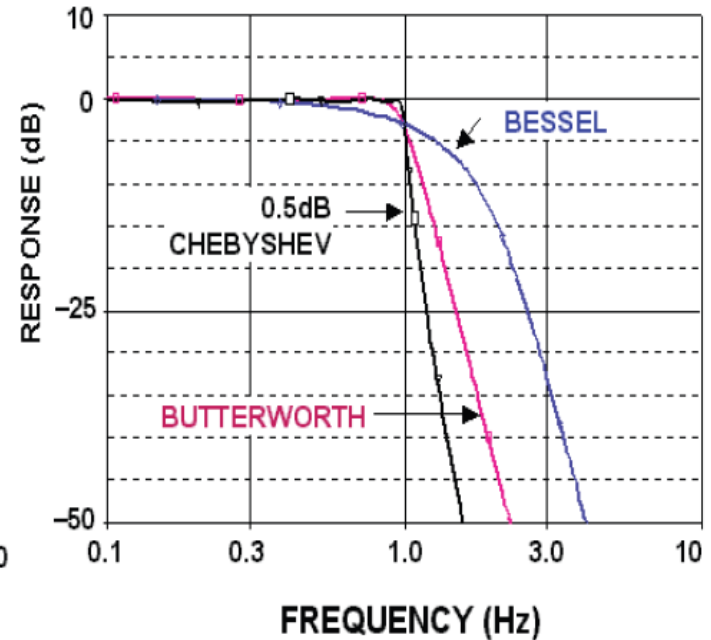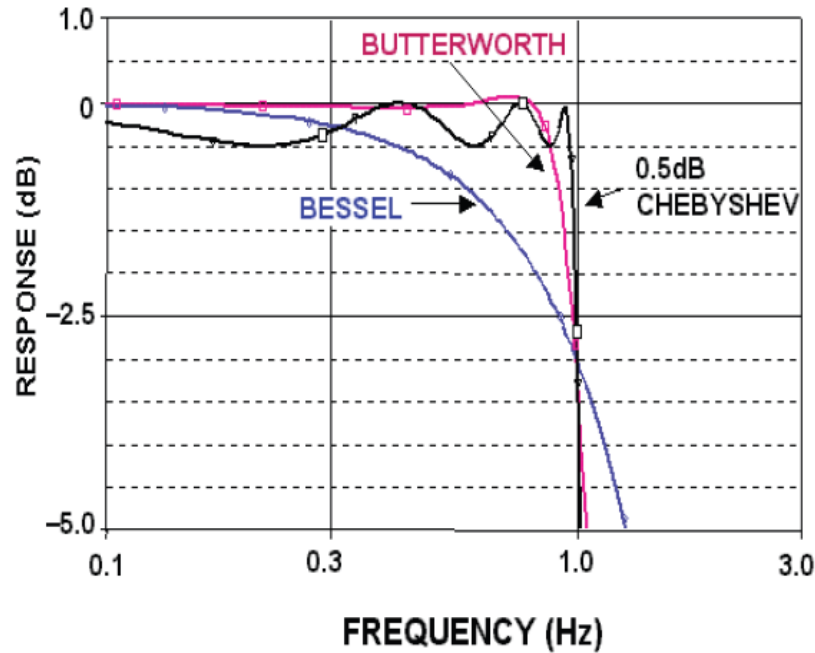

Comparison of Step and Impulse Responses

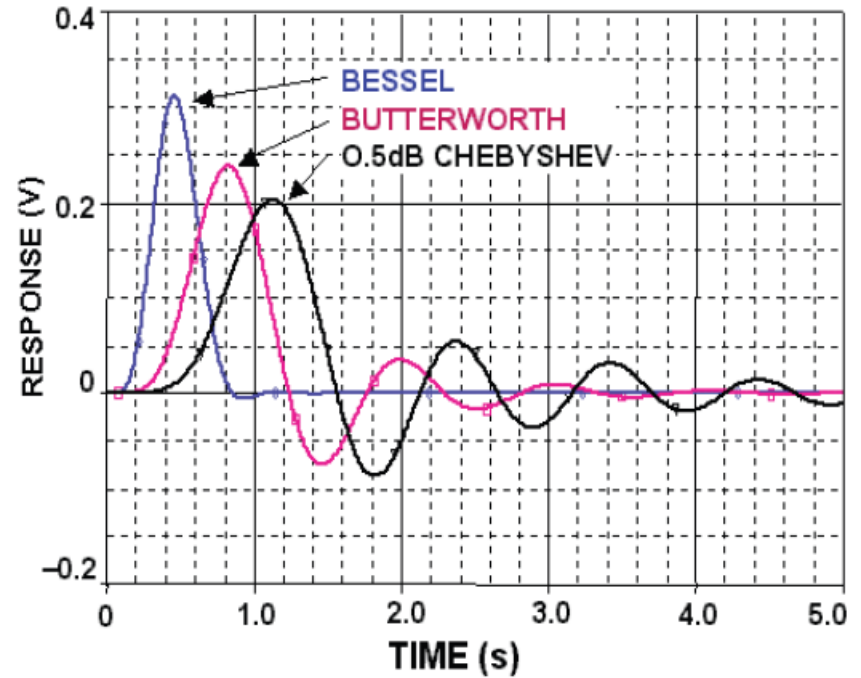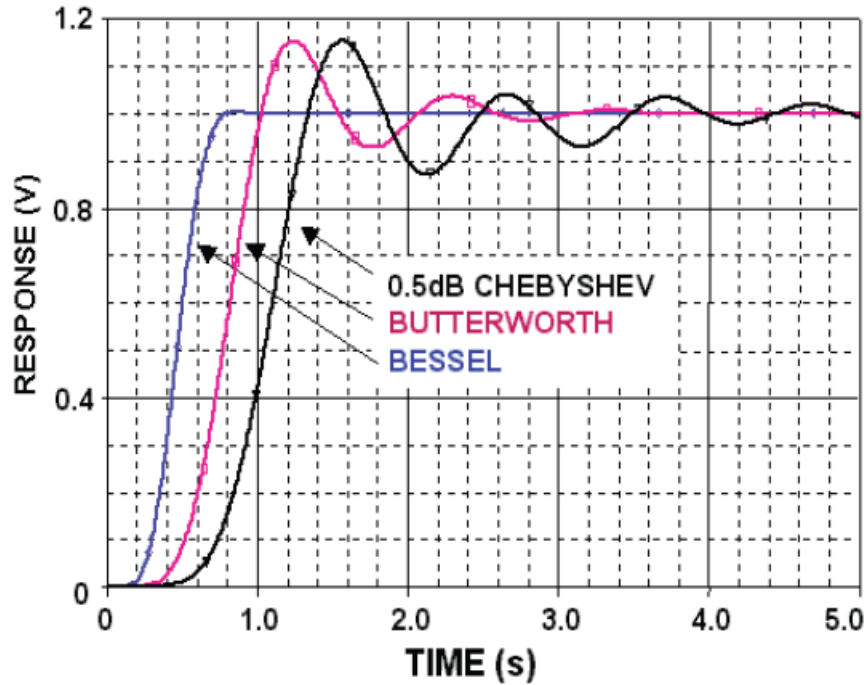

Butterworth VS Chebyshev

	Butterworth Filter	Chebyshev Filter
Order of Filter	The order of the Butterworth filter is higher than the Chebyshev filter for the same desired specifications.	The order of the Chebyshev filter is less compared to the Butterworth filter for the same desired specifications.
Hardware	It requires more hardware.	It requires less hardware.
Ripple	There is no ripple in passband and stopband of frequency response.	There is either ripple in passband or stopband.
Poles	All poles lie on a circle having a radius of the cutoff frequency.	All poles lie on ellipse having major axis R , ξ , minor axis r .
Transition band	The Butterworth filter has a wider transition band compared to the Chebyshev filter.	The Chebyshev filter has a narrow transition band compared to the Butterworth filter.
Types	It doesn't have any types.	It has two types; type-1 and type-2.
Cutoff Frequency	The cutoff frequency of this filter is not equal to the passband frequency.	The cutoff frequency of this filter is equal to the passband frequency.



Laboratory Work 3

Active filter circuits design and simulation

Nikolay Nikolaev

(nanikolaev@itmo.ru)

Nikolai Poliakov



(polyakov_n_a@itmo.ru)

Roman Olekhnovich

(r.o.olekhnovich@mail.ru)

Active High Pass Filter

First-order Filter

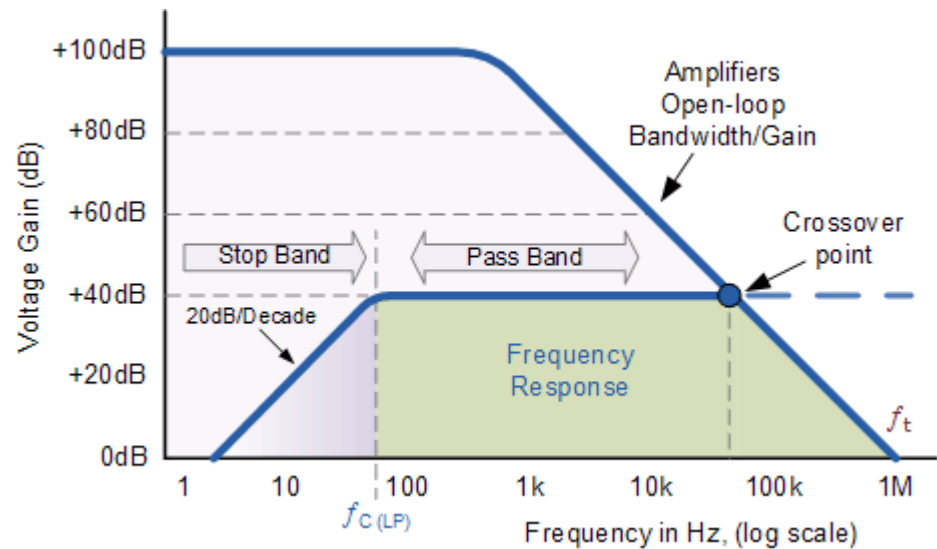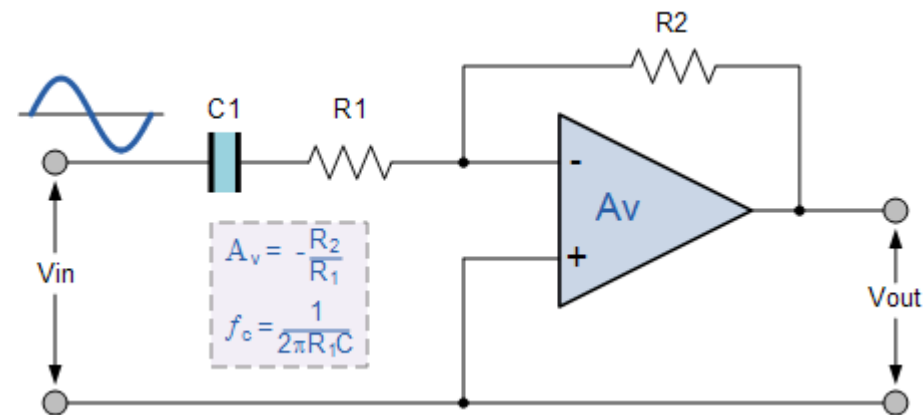



Second Order Filters

Nikolay Nikolaev

(nanikolaev@itmo.ru)


Nikolai Poliakov

(polyakov_n_a@itmo.ru)

Roman Olekhnovich

(r.o.olekhnovich@mail.ru)

Second Order Low Pass Filter

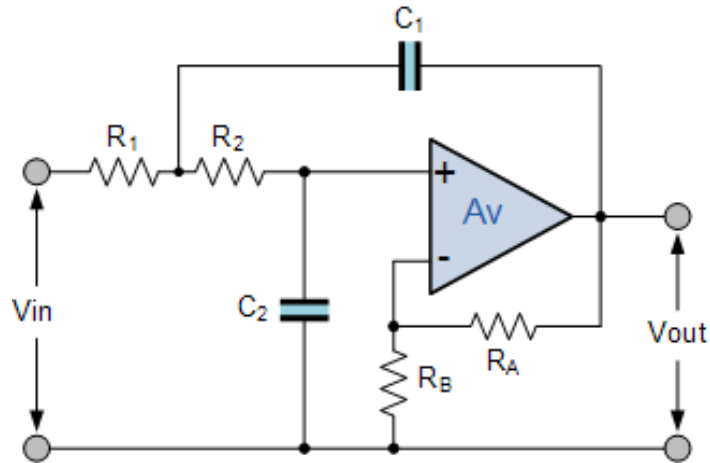


$$\text{Gain } (A_v) = 1 + \frac{R_A}{R_B}$$

If Resistor and Capacitor values are different:


$$f_c = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

If Resistor and Capacitor values are the same:

$$f_c = \frac{1}{2\pi RC}$$

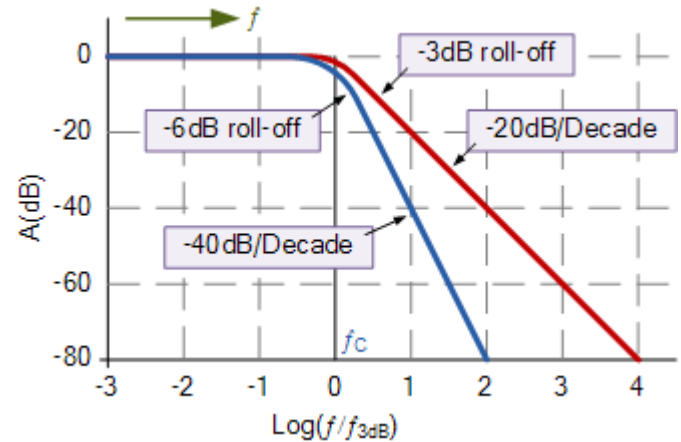

Second Order High Pass Filter

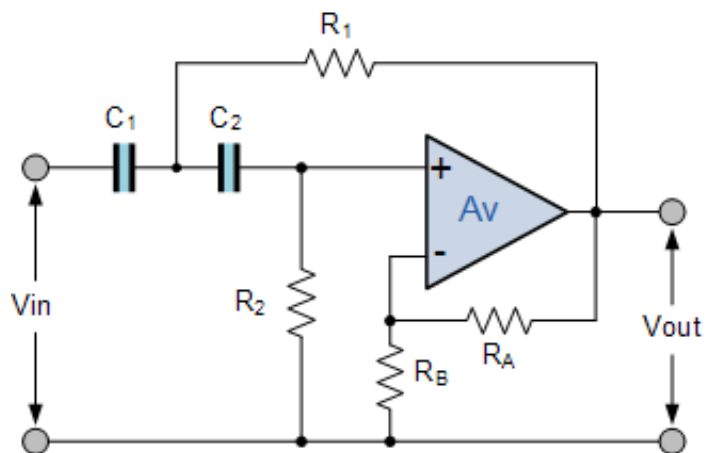


$$\text{Gain } (A_v) = 1 + \frac{R_A}{R_B}$$


If Resistor and Capacitor values are different:



$$f_c = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

If Resistor and Capacitor values are the same:

$$f_c = \frac{1}{2\pi RC}$$

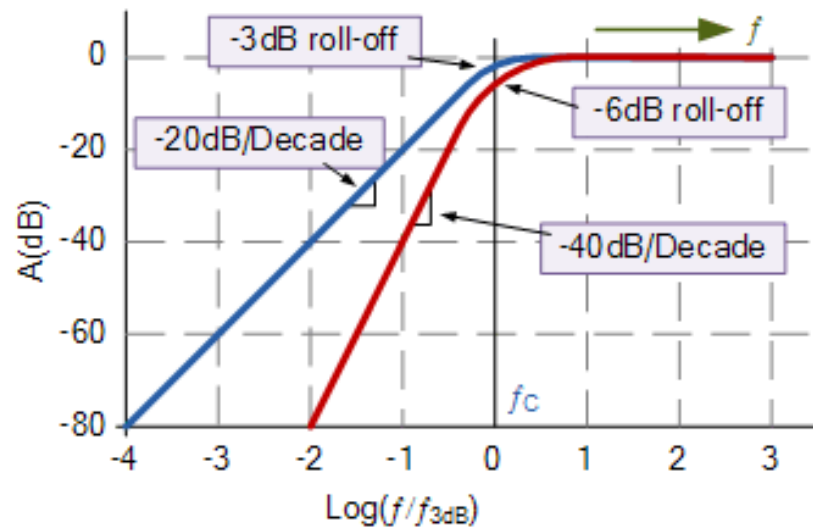

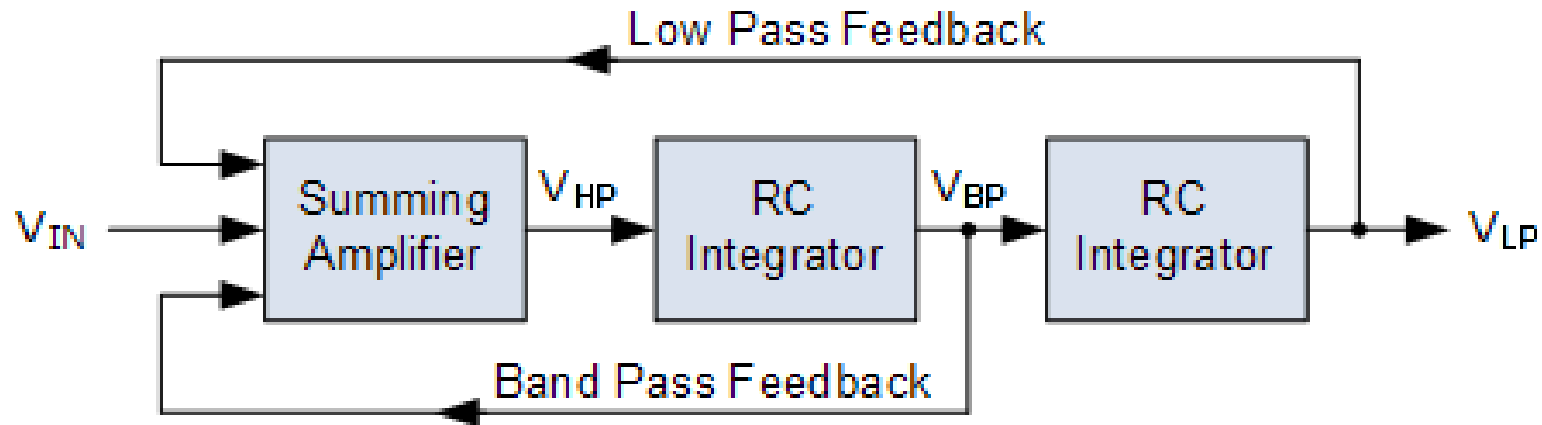

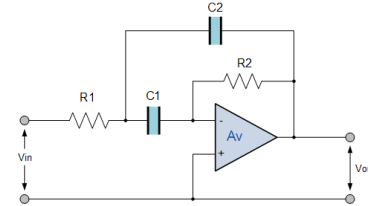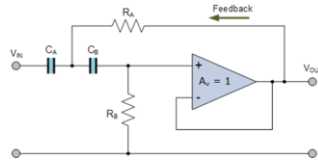

Sallen-Key

Non-inverting

Very precise DC-gain of 1

Less components for gain = 1

Op-amp input capacitance must possibly be taken into account

Resistive load for sources even in high-pass filters

Multiple Feedback

Inverting

Any gain is dependent on the resistor precision

Less components for gain > 1 or < 1

Op-amp input capacitance has almost no effect

Capacitive loads can become very high for sources in high-pass filters



Frequency Transformation

Nikolay Nikolaev

(nanikolaev@itmo.ru)

Nikolai Poliakov

(polyakov_n_a@itmo.ru)

Roman Olekhnovich

(r.o.olekhnovich@mail.ru)

Typical values of low-pass filter parameters


$$H_{LP}(f) := \frac{K}{b_1 \cdot \left(\left(\frac{2 \cdot \pi \cdot f \cdot i}{\omega_p} \right)^2 \right) + a_1 \cdot \frac{(2 \cdot \pi \cdot f \cdot i)}{\omega_p} + 1}$$

n	i	a_i	b_i	f_0/f_s	Q_i
Butterworth					
1	1	1.0000	0.0000	1.000	—
2	1	1.4142	1.0000	1.000	0.71
3	1	1.0000	0.0000	1.000	—
	2	1.0000	1.0000	1.272	1.00
4	1	1.8478	1.0000	0.719	0.54
	2	0.7654	1.0000	1.390	1.31
5	1	1.0000	0.0000	1.000	—
	2	1.6180	1.0000	0.859	0.62
	3	0.6180	1.0000	1.448	1.62
6	1	1.9319	1.0000	0.676	0.52
	2	1.4142	1.0000	1.000	0.71
	3	0.5176	1.0000	1.479	1.93
7	1	1.0000	0.0000	1.000	—
	2	1.8019	1.0000	0.745	0.55
	3	1.2470	1.0000	1.117	0.80
	4	0.4450	1.0000	1.499	2.25
8	1	1.9616	1.0000	0.661	0.51
	2	1.6629	1.0000	0.829	0.60
	3	1.1111	1.0000	1.206	0.90
	4	0.3902	1.0000	1.512	2.56
9	1	1.0000	0.0000	1.000	—
	2	1.8794	1.0000	0.703	0.53
	3	1.5321	1.0000	0.917	0.65
	4	1.0000	1.0000	1.272	1.00
	5	0.3473	1.0000	1.521	2.88
10	1	1.9754	1.0000	0.655	0.51
	2	1.7820	1.0000	0.756	0.56
	3	1.4142	1.0000	1.000	0.71
	4	0.9080	1.0000	1.322	1.10
	5	0.3129	1.0000	1.527	3.20

n	i	a_i	b_i	f_0/f_s	Q_i
Chebyshev					
1	1	1.0000	0.0000	1.000	—
2	1	1.0650	1.9305	1.000	1.30
3	1	3.3496	0.0000	0.299	—
	2	0.3559	1.1923	1.396	3.07
4	1	2.1853	5.5339	0.557	1.08
	2	0.1964	1.2009	1.410	5.58
5	1	5.6334	0.0000	0.178	—
	2	0.7620	2.6530	0.917	2.14
	3	0.1172	1.0686	1.500	8.82
6	1	3.2721	11.6773	0.379	1.04
	2	0.4077	1.9873	1.086	3.46
	3	0.0815	1.0861	1.489	12.78
7	1	7.9064	0.0000	0.126	—
	2	1.1159	4.8963	0.670	1.98
	3	0.2515	1.5944	1.222	5.02
	4	0.0582	1.0348	1.527	17.46
8	1	4.3583	20.2948	0.286	1.03
	2	0.5791	3.1808	0.855	3.08
	3	0.1765	1.4507	1.285	6.83
	4	0.0448	1.0478	1.517	22.87
9	1	10.1759	0.0000	0.098	—
	2	1.4585	7.8971	0.526	1.93
	3	0.3561	2.3651	1.001	4.32
	4	0.1294	1.3165	1.351	8.87
	5	0.0348	1.0210	1.537	29.00
10	1	5.4449	31.3788	0.230	1.03
	2	0.7414	4.7363	0.699	2.94
	3	0.2479	1.9952	1.094	5.70
	4	0.1008	1.2638	1.380	11.15
	5	0.0283	1.0304	1.530	35.85


n	i	a_i	b_i	f_0/f_s	Q_i
Bessel					
1	1	1.0000	0.0000	1.000	—
2	1	1.3617	0.6180	1.000	0.58
3	1	0.7560	0.0000	1.323	—
	2	0.9996	0.4772	1.414	0.69
4	1	1.3397	0.4889	0.978	0.52
	2	0.7743	0.3890	1.797	0.81
5	1	0.6656	0.0000	1.502	—
	2	1.1402	0.4128	1.184	0.56
	3	0.6216	0.3245	2.138	0.92
6	1	1.2217	0.3887	1.063	0.51
	2	0.9686	0.3505	1.431	0.61
	3	0.5131	0.2756	2.447	1.02
7	1	0.5937	0.0000	1.684	—
	2	1.0944	0.3395	1.207	0.53
	3	0.8304	0.3011	1.695	0.66
	4	0.4332	0.2381	2.731	1.13
8	1	1.1112	0.3162	1.164	0.51
	2	0.9754	0.2979	1.381	0.56
	3	0.7202	0.2621	1.963	0.71
	4	0.3728	0.2087	2.992	1.23
9	1	0.5386	0.0000	1.857	—
	2	1.0244	0.2834	1.277	0.52
	3	0.8710	0.2636	1.574	0.59
	4	0.6320	0.2311	2.226	0.76
	5	0.3257	0.1854	3.237	1.32
10	1	1.0215	0.2650	1.264	0.50
	2	0.9393	0.2549	1.412	0.54
	3	0.7815	0.2351	1.780	0.62
	4	0.5604	0.2059	2.479	0.81
	5	0.2883	0.1665	3.466	1.42

Lowpass Filter

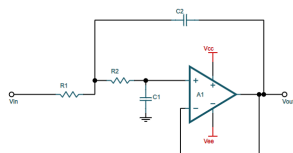

Sallen-Key

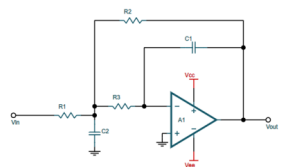
$$H_{LP_SK}(f) := \frac{K}{(2 \cdot \pi \cdot f \cdot i)^2 \cdot R_{1LP} \cdot R_{2LP} \cdot C_{1LP} \cdot C_{2LP} + C_{2LP} \cdot (R_{1LP} + R_{2LP}) \cdot (2 \cdot \pi \cdot f \cdot i) + 1}$$



Multiple Feedback


$$H_{LP_MF}(f) := \frac{\frac{R_{2LP}}{R_{1LP}}}{(2 \cdot \pi \cdot f \cdot i)^2 \cdot R_{2LP} \cdot R_{3LP} \cdot C_{1LP} \cdot C_{2LP} + C_{1LP} \cdot \left(R_{2LP} + R_{3LP} + \frac{R_{2LP} \cdot R_{3LP}}{R_{1LP}} \right) \cdot (2 \cdot \pi \cdot f \cdot i) + 1}$$

Highpass Filter

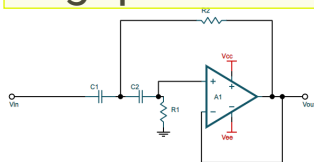

Sallen-Key
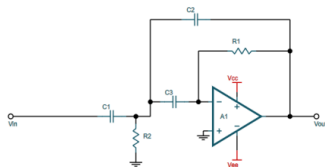
$$H_{HP_SK}(f) := \frac{K}{\frac{1}{(2 \cdot \pi \cdot f \cdot i)^2 \cdot R_{1HP} \cdot R_{2HP} \cdot C_{1HP} \cdot C_{2HP}} + \frac{R_{2HP} \cdot (C_{1HP} + C_{2HP}) + (1 - K) \cdot R_{1HP} \cdot C_{2HP}}{R_{1HP} \cdot R_{2HP} \cdot C_{1HP} \cdot C_{2HP} \cdot 2 \cdot \pi \cdot f \cdot i} + 1}$$



Multiple Feedback

$$H_{HP_MF}(f) := \frac{(2 \cdot \pi \cdot f \cdot i)^2 \cdot R_{1HP} \cdot R_{2HP} \cdot C_{1HP} \cdot C_{3HP}}{(2 \cdot \pi \cdot f \cdot i)^2 \cdot R_{1HP} \cdot R_{2HP} \cdot C_{2HP} \cdot C_{3HP} + R_{2HP} \cdot (C_{1HP} + C_{2HP} + C_{3HP}) \cdot (2 \cdot \pi \cdot f \cdot i) + 1}$$

Type of Transformation	Frequency transform
The Lowpass to Highpass (LP-HP) Frequency Transformation	$s \Leftrightarrow \frac{1}{s}$ $H_{HP}(s) = H_{LP}\left(\frac{1}{s}\right)$
The Lowpass to Bandpass (LP-BP) Frequency Transformation	$s \Leftrightarrow \frac{s^2 + \omega_0^2}{sBW}$ $H_{BP}(s) = H_{LP}\left(\frac{s^2 + \omega_0^2}{sBW}\right)$
The Lowpass to Band-Reject (LP-BR) Frequency Transformation	$s \Leftrightarrow \frac{sBW}{s^2 + \omega_0^2}$ $H_{BR}(s) = H_{LP}\left(\frac{sBW}{s^2 + \omega_0^2}\right)$

Typical values of High-pass filter parameters

$$H_{HP}(f) := \frac{K}{\frac{b_1}{\left(\frac{2 \cdot \pi \cdot f \cdot i}{\omega_p}\right)^2} + \frac{a_1}{\omega_p} + 1}$$

n	i	a_i	b_i	f_{θ}/f_s	Q_i
Butterworth					
1	1	1,0000	0,0000	1,000	–
2	1	1,4142	1,0000	1,000	0,71
3	1	1,0000	0,0000	1,000	–
	2	1,0000	1,0000	1,272	1,00
4	1	1,8478	1,0000	0,719	0,54
	2	0,7654	1,0000	1,390	1,31
5	1	1,0000	0,0000	1,000	–
	2	1,6180	1,0000	0,859	0,62
	3	0,6180	1,0000	1,448	1,62
6	1	1,9319	1,0000	0,676	0,52
	2	1,4142	1,0000	1,000	0,71
	3	0,5176	1,0000	1,479	1,93
7	1	1,0000	0,0000	1,000	–
	2	1,8019	1,0000	0,745	0,55
	3	1,2470	1,0000	1,117	0,80
	4	0,4450	1,0000	1,499	2,25
8	1	1,9616	1,0000	0,661	0,51
	2	1,6629	1,0000	0,829	0,60
	3	1,1111	1,0000	1,206	0,90
	4	0,3902	1,0000	1,512	2,56
9	1	1,0000	0,0000	1,000	–
	2	1,8794	1,0000	0,703	0,53
	3	1,5321	1,0000	0,917	0,65
	4	1,0000	1,0000	1,272	1,00
	5	0,3473	1,0000	1,521	2,88
10	1	1,9754	1,0000	0,655	0,51
	2	1,7820	1,0000	0,756	0,56
	3	1,4142	1,0000	1,000	0,71
	4	0,9080	1,0000	1,322	1,10
	5	0,3129	1,0000	1,527	3,20


n	i	a_i	b_i	f_{θ}/f_s	Q_i
Chebyshev					
1	1	1,0000	0,0000	1,000	–
2	1	1,0650	1,9305	1,000	1,30
3	1	3,3496	0,0000	0,299	–
	2	0,3559	1,1923	1,396	3,07
4	1	2,1853	5,5339	0,557	1,08
	2	0,1964	1,2009	1,410	5,58
5	1	5,6334	0,0000	0,178	–
	2	0,7620	2,6530	0,917	2,14
	3	0,1172	1,0686	1,500	8,82
6	1	3,2721	11,6773	0,379	1,04
	2	0,4077	1,9873	1,086	3,46
	3	0,0815	1,0861	1,489	12,78
7	1	7,9064	0,0000	0,126	–
	2	1,1159	4,8963	0,670	1,98
	3	0,2515	1,5944	1,222	5,02
	4	0,0582	1,0348	1,527	17,46
8	1	4,3583	20,2948	0,286	1,03
	2	0,5791	3,1808	0,855	3,08
	3	0,1765	1,4507	1,285	6,83
	4	0,0448	1,0478	1,517	22,87
9	1	10,1759	0,0000	0,098	–
	2	1,4585	7,8971	0,526	1,93
	3	0,3561	2,3651	1,001	4,32
	4	0,1294	1,3165	1,351	8,87
	5	0,0348	1,0210	1,537	29,00
10	1	5,4449	31,3788	0,230	1,03
	2	0,7414	4,7363	0,699	2,94
	3	0,2479	1,9952	1,094	5,70
	4	0,1008	1,2638	1,380	11,15
	5	0,0283	1,0304	1,530	35,85

n	i	a_i	b_i	f_{θ}/f_s	Q_i
Bessel					
1	1	1,0000	0,0000	1,000	–
2	1	1,3617	0,6180	1,000	0,58
3	1	0,7560	0,0000	1,323	–
	2	0,9996	0,4772	1,414	0,69
4	1	1,3397	0,4889	0,978	0,52
	2	0,7743	0,3890	1,797	0,81
5	1	0,6656	0,0000	1,502	–
	2	1,1402	0,4128	1,184	0,56
	3	0,6216	0,3245	2,138	0,92
6	1	1,2217	0,3887	1,063	0,51
	2	0,9686	0,3505	1,431	0,61
	3	0,5131	0,2756	2,447	1,02
7	1	0,5937	0,0000	1,684	–
	2	1,0944	0,3395	1,207	0,53
	3	0,8304	0,3011	1,695	0,66
	4	0,4332	0,2381	2,731	1,13
8	1	1,1112	0,3162	1,164	0,51
	2	0,9754	0,2979	1,381	0,56
	3	0,7202	0,2621	1,963	0,71
	4	0,3728	0,2087	2,992	1,23
9	1	0,5386	0,0000	1,857	–
	2	1,0244	0,2834	1,277	0,52
	3	0,8710	0,2636	1,574	0,59
	4	0,6320	0,2311	2,226	0,76
	5	0,3257	0,1854	3,237	1,32
10	1	1,0215	0,2650	1,264	0,50
	2	0,9393	0,2549	1,412	0,54
	3	0,7815	0,2351	1,780	0,62
	4	0,5604	0,2059	2,479	0,81
	5	0,2883	0,1665	3,466	1,42


Typical values of low-pass filter parameters

Filter scheme	Filter type	Voltage source power supply [V]		Required absolute gain of amplifier (sign of the gain is not considered)	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage amplitude, [V]	Load resistance, [Ω]	Filter resistance, [Ω]			Resistor tolerance	Filter capacitance, [Ω]			
		V_{cc}	V_{ee}							R_1	R_2	R_3		C_1	C_2	C_3	Capacitor tolerance
Sallen-Key Multiple Feedback	Lowpass Highpass	V_{cc}	V_{ee}	$ K_{NI} $	f_{test_1}	f_{test_2}	f_{test_3}	$V_{test_AC} = V_{test}$	R_{Load}	R_1	R_2	R_3	Resistor tolerance	C_1	C_2	C_3	Capacitor tolerance
Sallen-Key	Lowpass	6	-6	1,000	50	1000	100000	2,000	1000000	8200	15000	-	5%	1e-9	2,20E-09	-	20%
Multiple Feedback	Highpass	6	-6	1,000	60	1200	120000	2,000	1000000	3300	820	-	5%	1,50E-08	1,50E-08	2,20E-08	20%

Lowpass Filter

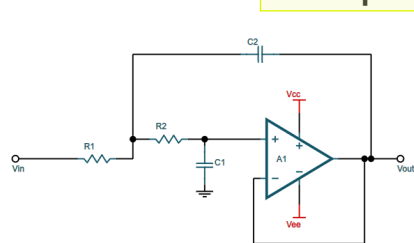


Sallen-Key

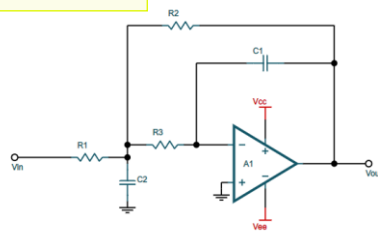


Multiple
Feedback

Highpass Filter

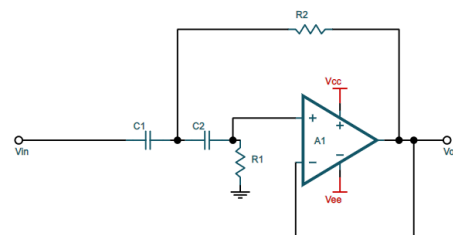

Sallen-Key


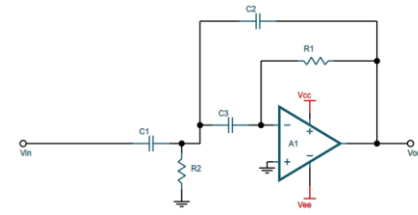


Multiple
Feedback

Collect the scheme

Filter scheme	Filter type	Voltage source power supply [V]		Required absolute gain of amplifier (sign of the gain is not considered)	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage amplitude, [V]	Load resistance, [Ω]	Filter resistance, [Ω]			Resistor tolerance	Filter capacitance, [Ω]			
		V_{cc}	V_{ee}							R_1	R_2	R_3		C_1	C_2	C_3	Capacitor tolerance
Sallen-Key Multiple Feedback	Lowpass Highpass	V_{cc}	V_{ee}	$ K_{NI} $	f_{test_1}	f_{test_2}	f_{test_3}	$V_{test_AC} = V_{test}$	R_{Load}	R_1	R_2	R_3		C_1	C_2	C_3	
Sallen-Key	Lowpass	6	-6	1,000	50	1000	100000	2,000	1000000	8200	15000	-	5%	1e-9	2,20E-09	-	20%
Multiple Feedback	Highpass	6	-6	1,000	60	1200	120000	2,000	1000000	3300	820	-	5%	1,50E-08	1,50E-08	2,20E-08	20%

Lowpass Filter

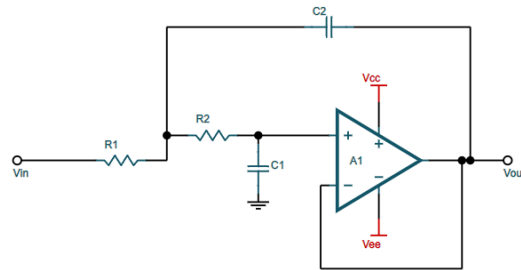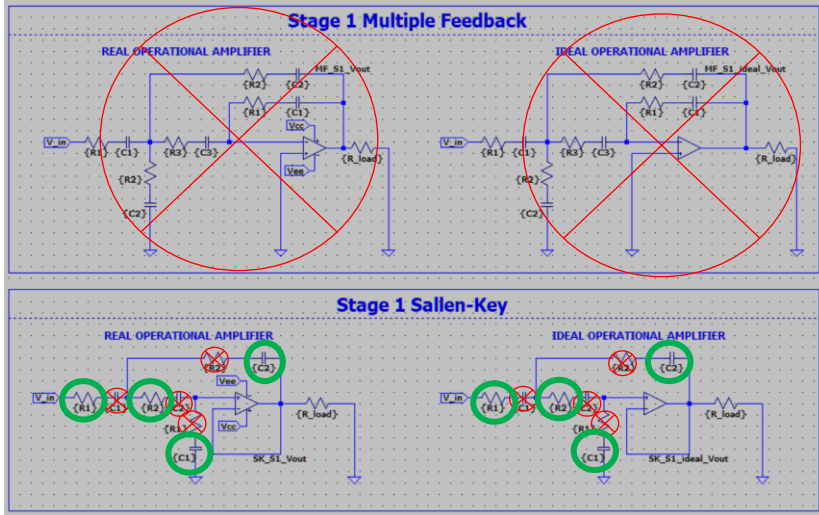

Specify your personal .lib file according to your variant

Right-click to edit

Lib: OPAMP_V10.lib

Simulation parameters:

Transient analysis parameters:

Time step parameters:

Signal source voltage amplitude [V]:

Step source voltage amplitude [V]:

Signal test frequency 1 [Hz]:

Signal test frequency 2 [Hz]:

Signal test frequency 3 [Hz]:

AC sweep analysis parameters:

Signal source voltage amplitude AC [V]:

Element parameters for simulation:

R1 [Ω]:

R2 [Ω]:

R3 [Ω]:

C1 [F]:

C2 [F]:

C3 [F]:

Load resistance R_load [Ω]:

Power supply source voltage Vcc [V]:

Power supply source voltage Vee [V]:

Step for R1 Tolerance:

Step for R2 Tolerance:

Step for R3 Tolerance:

Step for C1 Tolerance:

Step for C2 Tolerance:

Step for C3 Tolerance:




Step for R_load:

This line is required to simulate ideal OpAMP:

Lib: opamp.lib

Define the filter passband

Filter scheme	Filter type	Voltage source power supply [V]		Required absolute gain of amplifier (sign of the gain is not considered)	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage amplitude, [V]	Load resistance, [Ω]	Filter resistance, [Ω]			Resistor tolerance	Filter capacitance, [Ω]			Capacitor tolerance
Sallen-Key Multiple Feedback	Lowpass Highpass	V_{cc}	V_{ee}	$ K_{NT} $	f_{test_1}	f_{test_2}	f_{test_3}	$V_{testAC}=V_{test}$	R_{Load}	R_1	R_2	R_3		C_1	C_2	C_3	
Sallen-Key	Lowpass	6	-6	1,000	50	1000	100000	2,000	1000000	8200	15000	-	5%	1e-9	2,20E-09	-	20%
Multiple Feedback	Highpass	6	-6	1,000	60	1200	120000	2,000	1000000	3300	820	-	5%	1,50E-08	1,50E-08	2,20E-08	20%

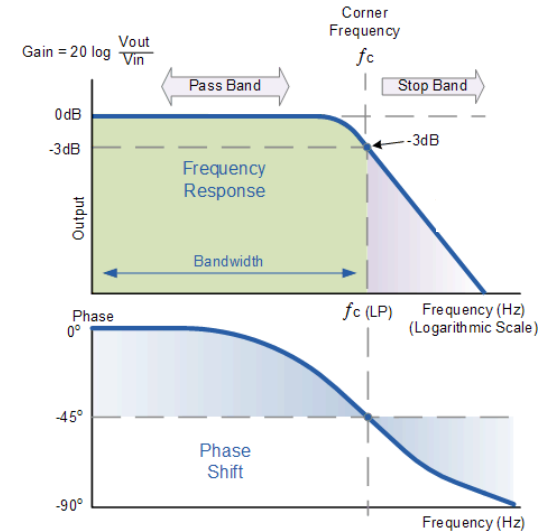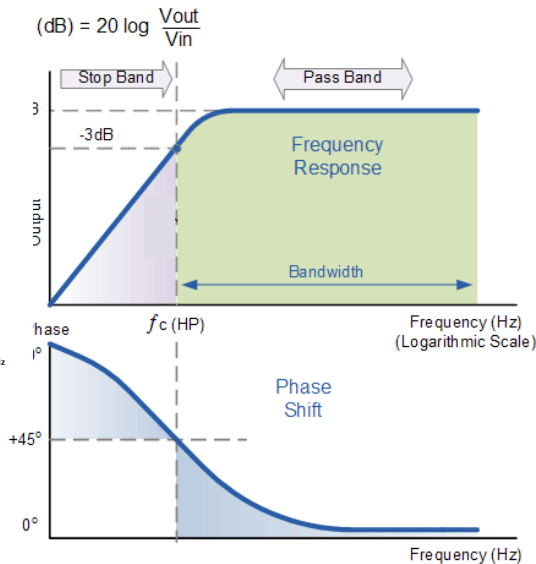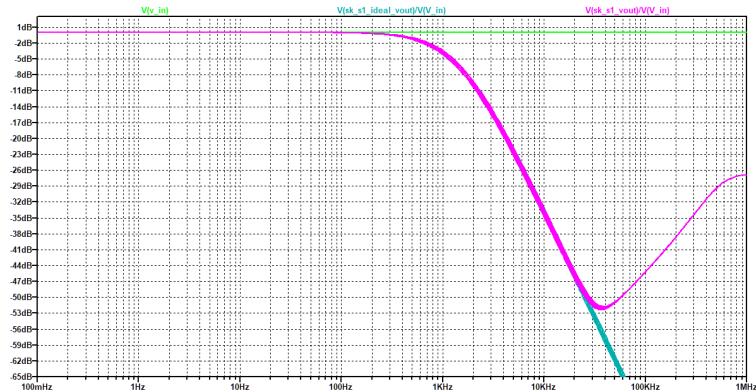

Define the filter approximation

Filter scheme	Filter type	Voltage source power supply [V]		Required absolute gain of amplifier (sign of the gain is not considered)	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage amplitude, [V]	Load resistance, [Ω]	Filter resistance, [Ω]			Resistor tolerance	Filter capacitance, [n]			Capacitor tolerance
Sallen-Key Multiple Feedback	Lowpass Highpass	V _{cc}	V _{ee}	K _{NT}	f _{test_1}	f _{test_2}	f _{test_3}	V _{testAC} =V _{test}	R _{Load}	R ₁	R ₂	R ₃		C ₁	C ₂	C ₃	
Sallen-Key	Lowpass	6	-6	1,000	50	1000	100000	2,000	1000000	8200	15000	-	5%	1e-9	2,20E-09	-	20%
Multiple Feedback	Highpass	6	-6	1,000	60	1200	120000	2,000	1000000	3300	820	-	5%	1,50E-08	1,50E-08	2,20E-08	20%


n	i	a _i	b _i	f _B /f _R	Q _i
Butterworth					
1	1	1,0000	0,0000	1,000	-
2	1	1,4142	1,0000	1,000	0,71

n	i	a _i	b _i	f _B /f _R	Q _i
Chebyshev					
1	1	1,0000	0,0000	1,000	-
2	1	1,0650	1,9305	1,000	1,30


n	i	a _i	b _i	f _B /f _R	Q _i
Bessel					
1	1	1,0000	0,0000	1,000	-
2	1	1,3617	0,6180	1,000	0,58

$$H_{LP}(f) := \frac{K}{b_1 \cdot \left(\left(\frac{2 \cdot \pi \cdot f \cdot i}{\omega_p} \right)^2 + a_1 \cdot \frac{2 \cdot \pi \cdot f \cdot i}{\omega_p} + 1 \right)}$$

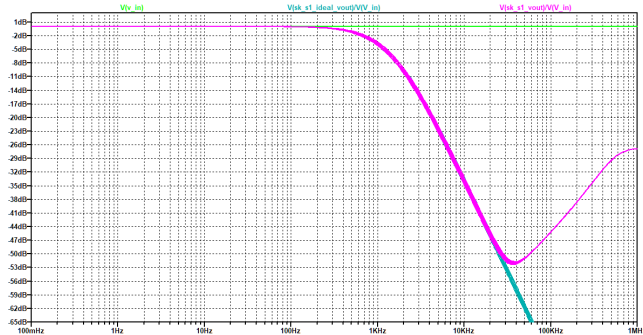
$$H_{HP}(f) := \frac{K}{\left(\left(\frac{2 \cdot \pi \cdot f \cdot i}{\omega_p} \right)^2 + \frac{a_1}{\frac{2 \cdot \pi \cdot f \cdot i}{\omega_p}} + 1 \right)}$$




Butterworth

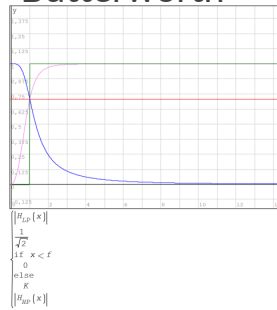

Chebyshev

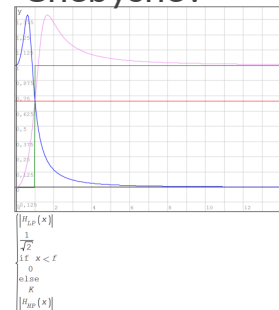


Bessel

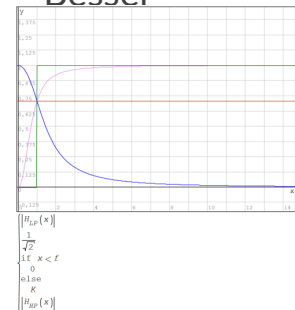

Define the filter approximation


Filter scheme	Filter type	Voltage source power supply [V]		Required absolute gain of amplifier (sign of the gain is not considered)	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage amplitude, [V]	Load resistance, [Ω]	Filter resistance, [Ω]			Resistor tolerance	Filter capacitance, [nF]			Capacitor tolerance
Sallen-Key Multiple Feedback	Lowpass Highpass	V_{cc}	V_{ee}	$ K_{NT} $	f_{test_1}	f_{test_2}	f_{test_3}	$V_{testAC}=V_{test}$	R_{Load}	R_1	R_2	R_3		C_1	C_2	C_3	
Sallen-Key	Lowpass	6	-6	1,000	50	1000	100000	2,000	1000000	8200	15000	-	5%	1e-9	2,20E-09	-	20%
Multiple Feedback	Highpass	6	-6	1,000	60	1200	120000	2,000	1000000	3300	820	-	5%	1,50E-08	1,50E-08	2,20E-08	20%

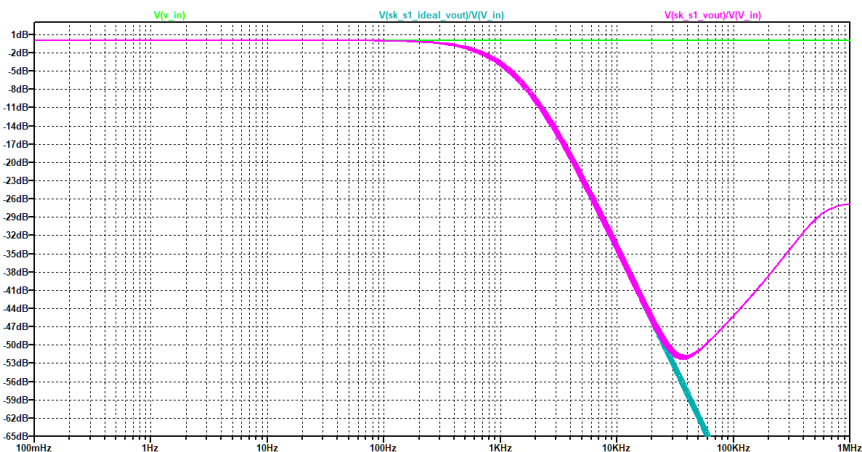


Butterworth

Chebyshev


Bessel

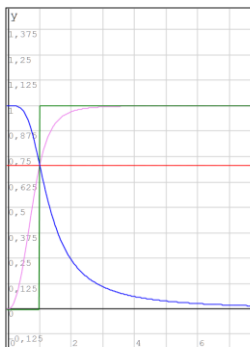

$$\begin{cases} |H_{LP}(x)| \\ \frac{1}{\sqrt{2}} \\ \text{if } x < f \\ 0 \\ \text{else} \\ K \\ |H_{HP}(x)| \end{cases}$$

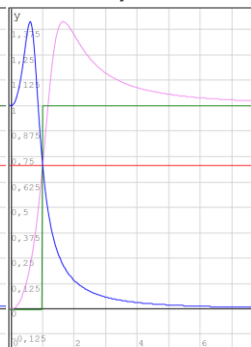





$$\begin{cases} |H_{LP}(x)| \\ \frac{1}{\sqrt{2}} \\ \text{if } x < f \\ 0 \\ \text{else} \\ K \\ |H_{HP}(x)| \end{cases}$$

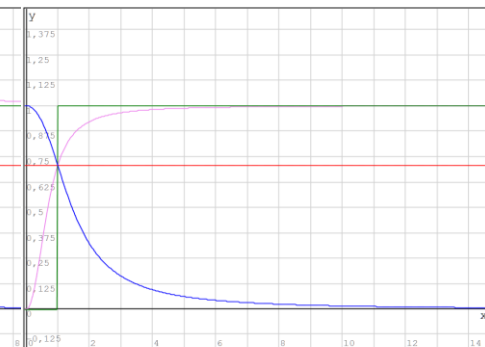

$$\begin{cases} |H_{LP}(x)| \\ \frac{1}{\sqrt{2}} \\ \text{if } x < f \\ 0 \\ \text{else} \\ K \\ |H_{HP}(x)| \end{cases}$$





Define the filter approximation

Filter scheme	Filter type	Voltage source power supply [V]		Required absolute gain of amplifier (sign of the gain is not considered)	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage amplitude, [V]	Load resistance, [Ω]	Filter resistance, [Ω]			Resistor tolerance	Filter capacitance, [Ω]			Capacitor tolerance
Sallen-Key Multiple Feedback	Lowpass Highpass	V_{cc}	V_{ee}	$ K_{NT} $	f_{test_1}	f_{test_2}	f_{test_3}	$V_{testAC}=V_{test}$	R_{Load}	R_1	R_2	R_3		C_1	C_2	C_3	
Sallen-Key	Lowpass	6	-6	1,000	50	1000	100000	2,000	1000000	8200	15000	-	5%	1e-9	2,20E-09	-	20%
Multiple Feedback	Highpass	6	-6	1,000	60	1200	120000	2,000	1000000	3300	820	-	5%	1,50E-08	1,50E-08	2,20E-08	20%

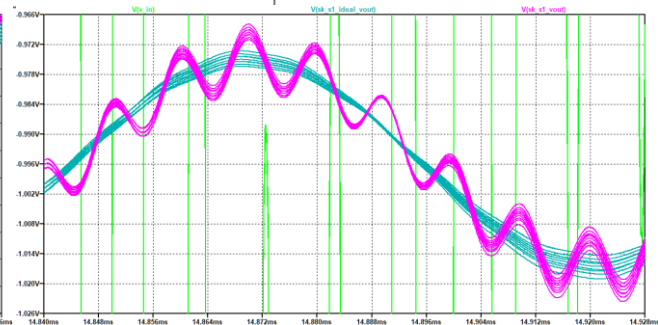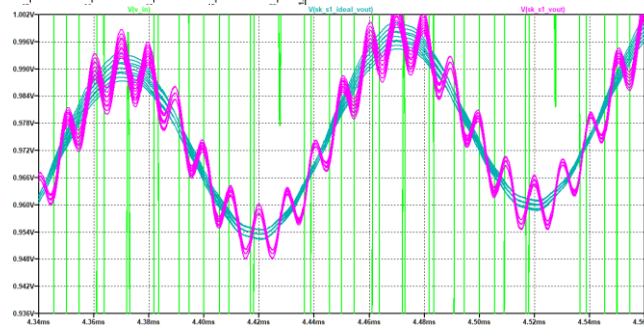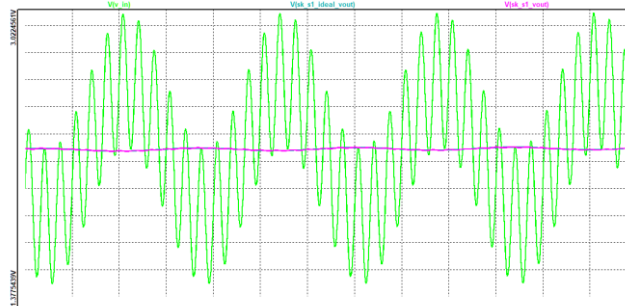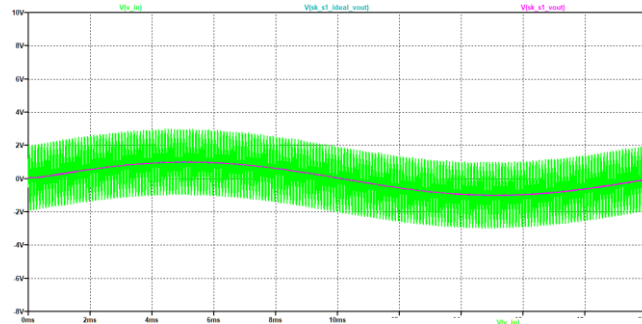

Define the filter approximation

Filter scheme	Filter type	Voltage source power supply [V]		Required absolute gain of amplifier (sign of the gain is not considered)	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage amplitude, [V]	Load resistance, [Ω]	Filter resistance, [Ω]			Resistor tolerance	Filter capacitance, [Ω]			Capacitor tolerance
Sallen-Key Multiple Feedback	Lowpass Highpass	V_{cc}	V_{ee}	$ K_{NT} $	f_{test_1}	f_{test_2}	f_{test_3}	$V_{testAC}=V_{test}$	R_{Load}	R_1	R_2	R_3		C_1	C_2	C_3	
Sallen-Key	Lowpass	6	-6	1,000	50	1000	100000	2,000	1000000	8200	15000	-	5%	1e-9	2,20E-09	-	20%
Multiple Feedback	Highpass	6	-6	1,000	60	1200	120000	2,000	1000000	3300	820	-	5%	1,50E-08	1,50E-08	2,20E-08	20%

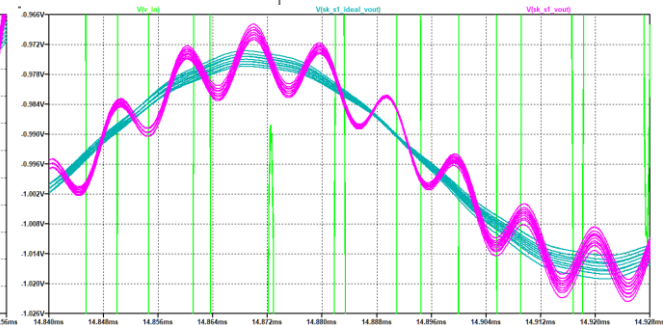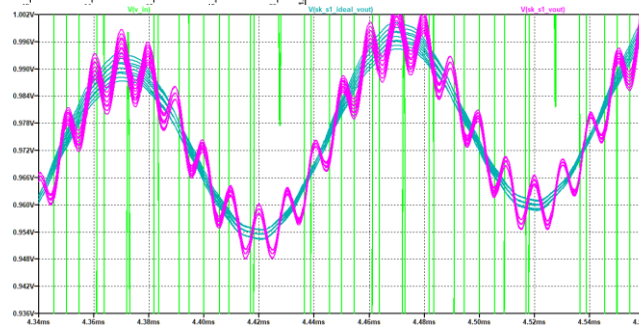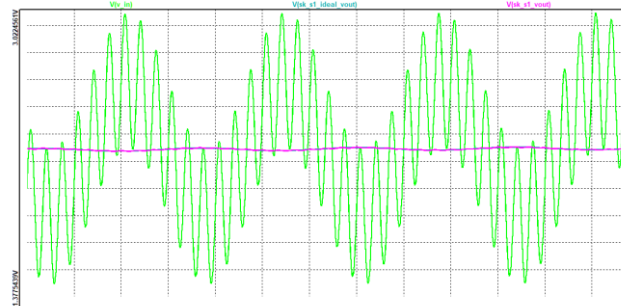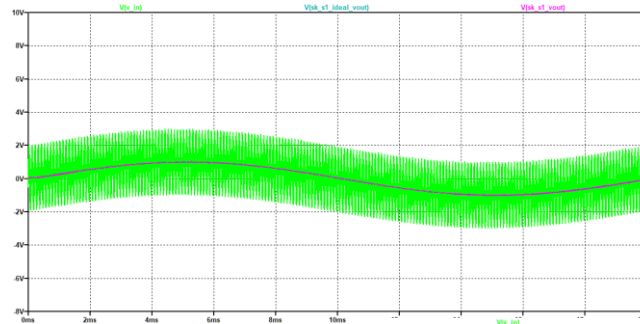

Define the step response

Filter scheme	Filter type	Voltage source power supply [V]		Required absolute gain of amplifier (sign of the gain is not considered)	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage frequency, [Hz]	Source voltage amplitude, [V]	Load resistance, [Ω]	Filter resistance, [Ω]			Resistor tolerance	Filter capacitance, [Ω]			Capacitor tolerance
Sallen-Key Multiple Feedback	Lowpass Highpass	V_{cc}	V_{ee}	$ K_{NT} $	f_{test_1}	f_{test_2}	f_{test_3}	$V_{testAC}=V_{test}$	R_{Load}	R_1	R_2	R_3		C_1	C_2	C_3	
Sallen-Key	Lowpass	6	-6	1,000	50	1000	100000	2,000	1000000	8200	15000	-	5%	1e-9	2,20E-09	-	20%
Multiple Feedback	Highpass	6	-6	1,000	60	1200	120000	2,000	1000000	3300	820	-	5%	1,50E-08	1,50E-08	2,20E-08	20%

Edit Simulation Command

Transient AC Analysis DC sweep Noise DC Transfer DC op pnt

Perform a non-linear, time-domain simulation.

Stop time:

Time to start saving data:

Maximum Timestep:

Start external DC supply voltages at 0V: ☐

Stop simulating if steady state is detected: ☐

Don't reset T=0 when steady state is detected: ☐

Step the load current source: ☐

Skip initial operating point solution: ☒

Syntax: .tran <Tprint> <Tstop> [<Tstart> [<Tmaxstep>]] [<option> [<option>] ...]

.tran 0 {1*1/f_test_1} {0*1/f_test_2} {1/f_test_3/50} uic

Cancel OK


$V_{step}=1$

$V_{test}=0$

```

Signal source voltage step(DC)          parameter V_step=1
Step source voltage step(DC)           parameter V_step=1
Signal test frequency 1 [Hz]            parameter f_test_1=50
Signal test frequency 2 [Hz]            parameter f_test_2=1000
Signal test frequency 3 [Hz]            parameter f_test_3=100000
AC source voltage amplitude              parameter V_test=2000
Signal source voltage step(DC)           parameter V_step=1000000

```

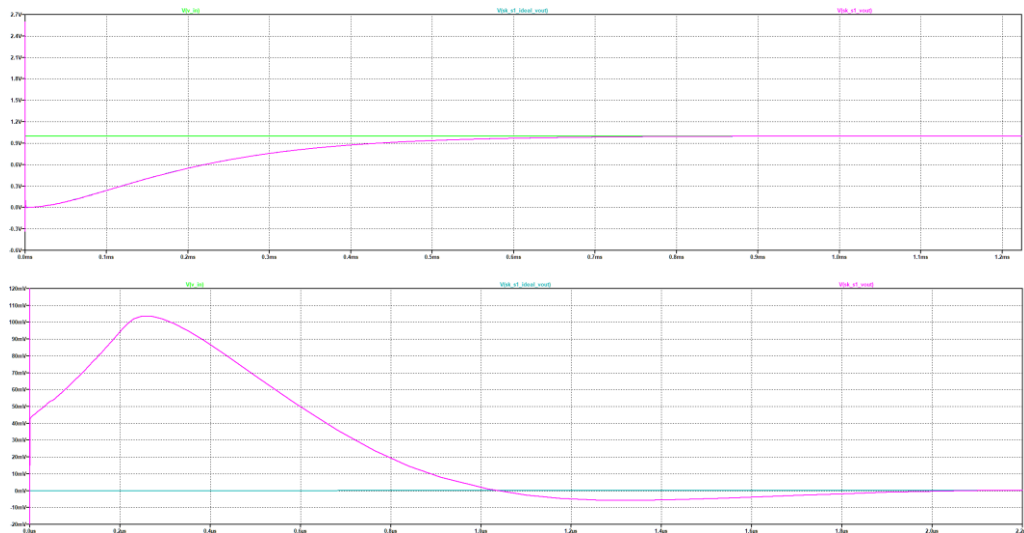

Filter scheme	Filter type	Voltage source power supply [V]		Required absolute gain of amplifier (sign of the gain is not considered)	Source voltage frequency, [Hz]		Source voltage frequency, [Hz]	Source voltage amplitude, [V]	Load resistance, [Ω]	Filter resistance, [Ω]			Resistor tolerance	Filter capacitance, [Ω]			Capacitor tolerance
		V_{cc}	V_{ee}		f_{test_1}	f_{test_2}				R_1	R_2	R_3		C_1	C_2	C_3	
Sallen-Key Multiple Feedback	Lowpass Highpass			$ K_{NT} $				$V_{testAC}=V_{test}$	R_{Load}								
Sallen-Key	Lowpass	6	-6	1,000	50	1000	100000	2,000	1000000	8200	15000	-	5%	1e-9	2,20E-09	-	20%
Multiple Feedback	Highpass	6	-6	1,000	60	1200	120000	2,000	1000000	3300	820	-	5%	1,50E-08	1,50E-08	2,20E-08	20%


Conclusions should contain:

- Which filter type were used?
- What was the bandwidth?
- What was the maximum/minimum gain relation in the passband?

<https://forms.yandex.com/cloud/637a65df5d2a068973e26fba/>

<https://clck.ru/32jqcy>

1st deadline: 02.12.2022 23:59 (GMT +8)

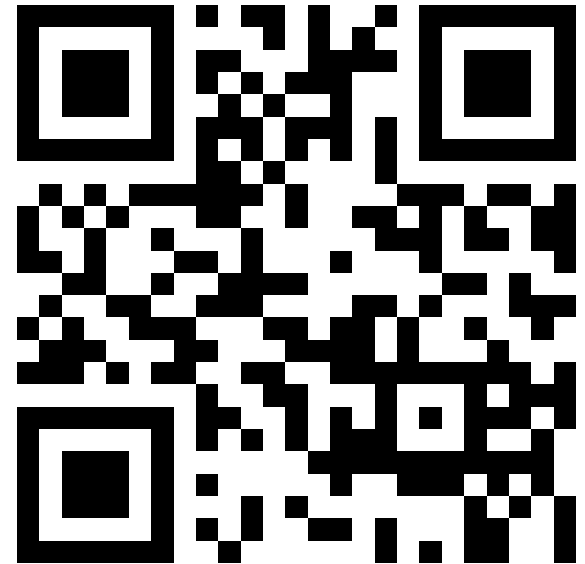

The background features a dark gray grid pattern. In the top right and bottom left corners, there are decorative wavy lines in a bright purple color, creating a modern, abstract aesthetic.

iTMO

Thanks for your attention!