 


Functional electronic circuits

Laboratory work 4 «System bus design»

1. Develop the system with master device, slave device and interconnection matrix according to the scheme, timing diagram and memory map presented below.



Memory map

| Addresses | Device |
|-------------|----------|
| 0x00 - 0x1F | Slave 1 |
| 0x20 - 0x2F | Slave 2 |
| 0x30 - 0x3F | Slave 3 |
| 0x40 - 0x4F | Slave 4 |
| 0x50 - ... | Reserved |

Figure 1 – Scheme of the system and memory map


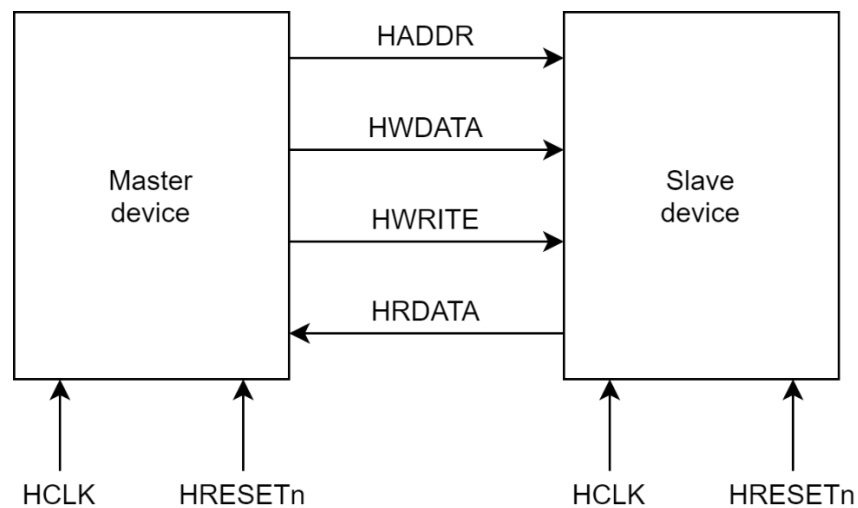


Figure 2 – The interface between master and slave device

WRITE data

 

READ data

 


Figure 3 – Timing diagrams of write and read operations

2. Develop a testbench for the system and test the system.
3. Put results in the report. The report should consist:
 - 3.1. Student Name and Student ID
 - 3.2. The picture of the system
 - 3.3. The timing diagram with simulation results
 - 3.4. Code of the testbench and the device.
4. Upload the report by this form: <https://forms.yandex.ru/u/645e08b3c769f175ad7c6e64/>