

# Functional electronic circuits

## Laboratory work 1 «Verilog HDL Basics»

1. Develop the device that can read N values (x values) from the external memory and perform the operations according the variant task. The signal interface is presented in Figure 1 and contents such signals as:
  - 1.1. **x** – 32 bit input value;
  - 1.2. **rd** – read signal;
  - 1.3. **start** – signal to start calculation;
  - 1.4. **rst** – reset signal;
  - 1.5. **clk** – clock signal;
  - 1.6. **y** – the 32 bit result value;
  - 1.7. **rdy** – the ready signal. It is asserted when the device is ready for computation.

 


Figure 1. The developing system

2. Draw a microarchitecture of your device.
3. Put results in the report. The report should consist:
  - 3.1. Student Name and Student ID
  - 3.2. The picture with microarchitecture
  - 3.3. The timing diagram with simulation results
  - 3.4. Code of the testbench and the device.
4. Upload the report by this form: <https://forms.yandex.ru/u/642fa91d5056900badef4398/>

## Variants

Nº	Device function	N
0	Calculate the sum of elements	5
1	Find the greatest element	7
2	Find the lowest element	6
3	Calculate the sum of elements that greater 2	7
4	Count zeros in input data	5
5	Perform cyclic shift of the value 1 to the right. The input value (x value) should be used as a count of shift operations.	8
6	Perform cyclic shift of the value 1 to the left. The input value (x value) should be used as a count of shift operations.	10