



Practice 4 - Bandpass filters detailed instructions

Nikolay Nikolaev

(nanikolaev@itmo.ru)

Nikolai Poliakov

(polyakov_n_a@itmo.ru)

Roman Olekhnovich

(r.o.olekhnovich@mail.ru)


<https://forms.yandex.com/cloud/637a6d72eb614687d53f9b86/>

<https://clck.ru/32jqdb>

1st deadline: 02.12.2022 23:59 (GMT +8)




Active Band Pass Filter

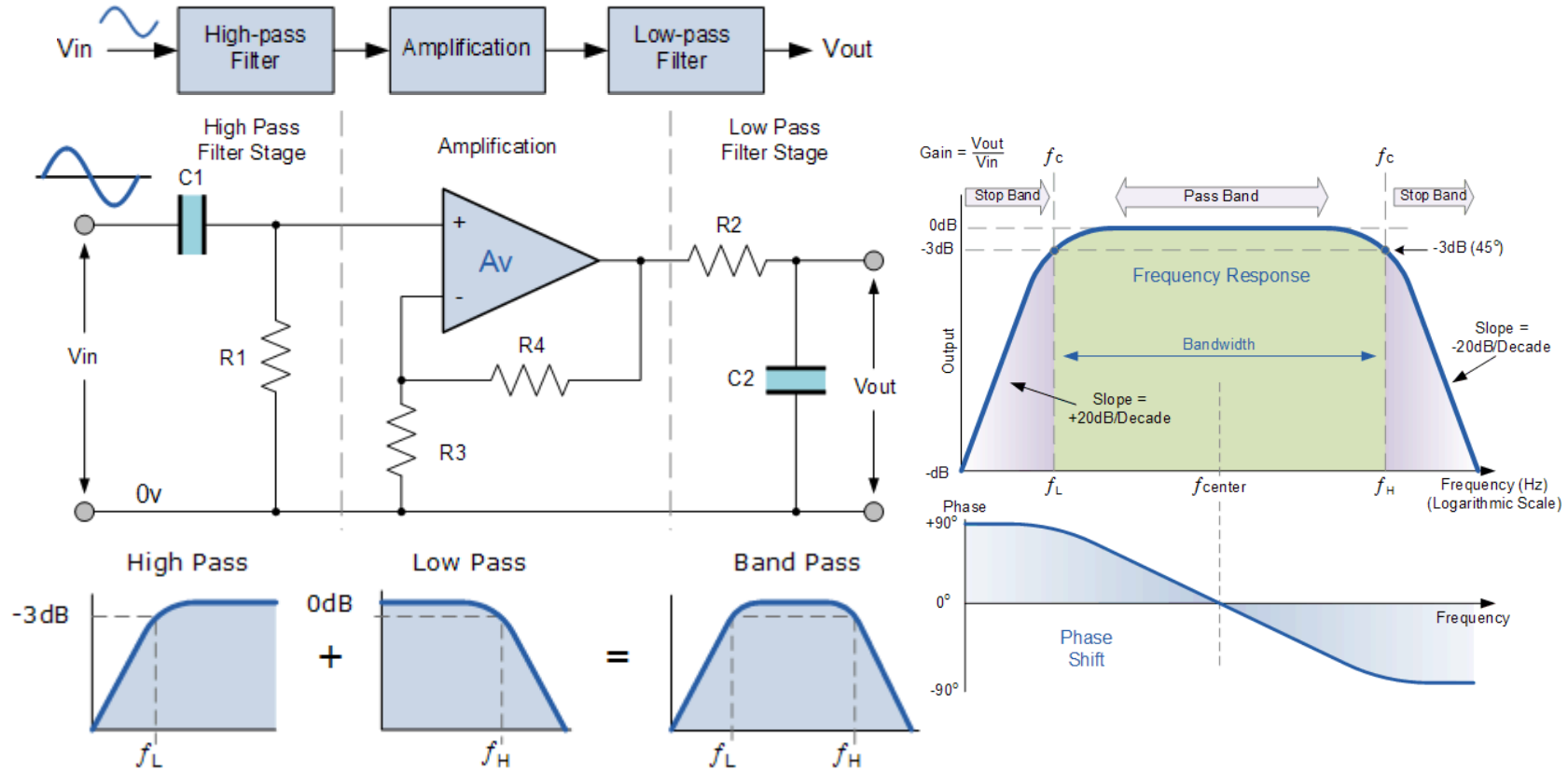

Active Band Pass Filter


Inverting Band Pass Filter Circuit

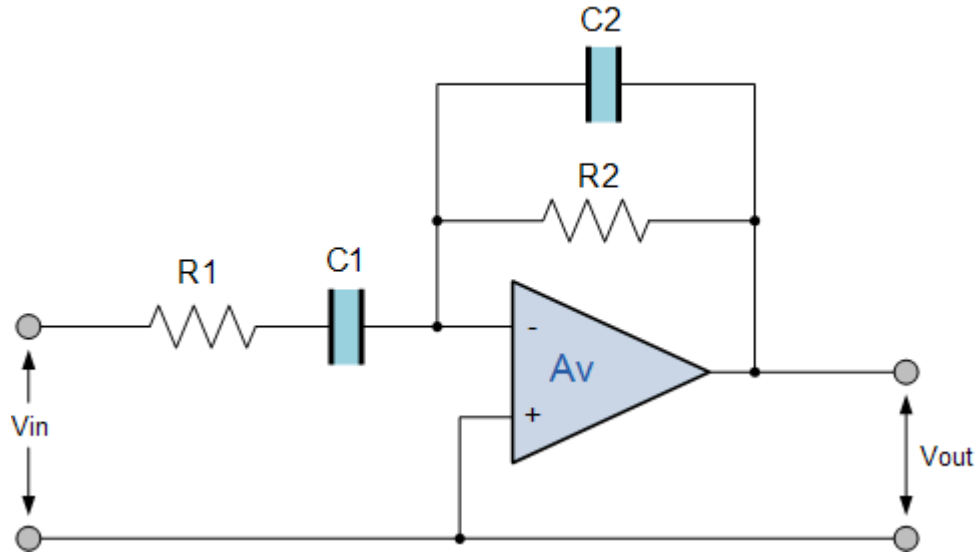

$$f_{C1} = \frac{1}{2\pi R_1 C_1}$$

$$f_{C2} = \frac{1}{2\pi R_2 C_2}$$

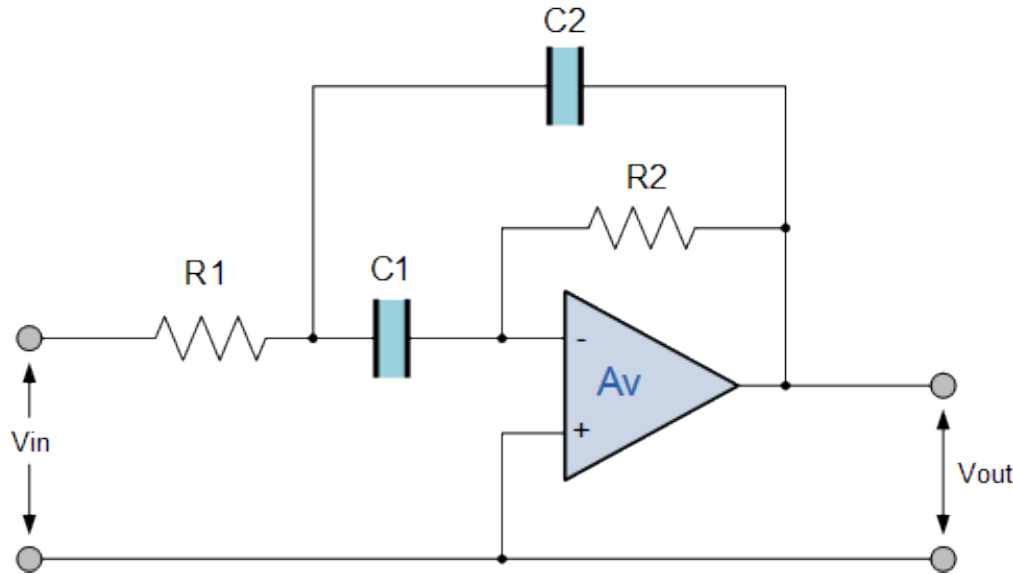Multiple Feedback Band Pass Active Filter



infinite-gain multiple-feedback (IGMF) band pass filter


the characteristics of the IGMF filter

$$f_r = \frac{1}{2\pi\sqrt{R_1 C_1 R_2 C_2}}$$

$$Q = \frac{f_r}{BW_{-3dB}} = \frac{1}{2} \sqrt{\frac{R_2}{R_1}}$$

$$\text{Max gain} \sim -\frac{R_2}{2R_1} = 2Q^2$$

Sallen-Key

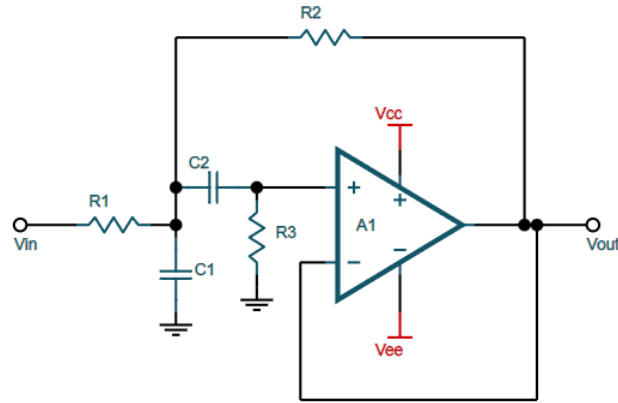

the characteristics of the IGMF filter

$$\frac{U_{out}(p)}{U_{in}(p)} = \frac{KRC\omega_0 p}{R^2 C^2 \omega_0^2 p^2 + RC(3-K)\omega_0 p + 1}$$

$$Max\ gain \sim K = 1 + \frac{R_2}{R_3}$$

$$C_1 = C_2 = C$$

$$R_1 = R_2 = \frac{1}{2} R_3$$

Middle frequency of bandpass:

$$\omega_0 = \frac{1}{RC}$$

Bandwidth:

$$B = \omega_0(3 - K)$$

Type of Transformation	Frequency transform
The Lowpass to Highpass (LP-HP) Frequency Transformation	$s \Leftrightarrow \frac{1}{s}$ $H_{HP}(s) = H_{LP}\left(\frac{1}{s}\right)$
The Lowpass to Bandpass (LP-BP) Frequency Transformation	$s \Leftrightarrow \frac{s^2 + \omega_0^2}{sBW}$ $H_{BP}(s) = H_{LP}\left(\frac{s^2 + \omega_0^2}{sBW}\right)$
The Lowpass to Band-Reject (LP-BR) Frequency Transformation	$s \Leftrightarrow \frac{sBW}{s^2 + \omega_0^2}$ $H_{BR}(s) = H_{LP}\left(\frac{sBW}{s^2 + \omega_0^2}\right)$


Typical values of Bandpass filter parameters

$$H_{BP2}(p) = \frac{K \frac{\omega_0}{Q} p}{p^2 + \frac{\omega_0}{Q} p + \omega_0^2} = \frac{K}{1 + Q(\frac{p}{\omega_0} + \frac{\omega_0}{p})}$$

$$\omega_0 = \sqrt{\omega_{P1} \omega_{P2}}$$

$$Q = \omega_0 / B$$

$$B = \omega_{p2} - \omega_{p1}$$

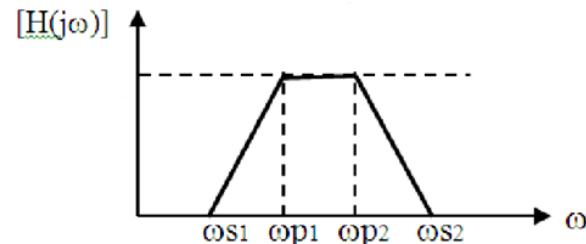

<i>n</i>	<i>i</i>	<i>a_i</i>	<i>b_i</i>	<i>f_ω/f_κ</i>	<i>Q_i</i>
Butterworth					
1	1	1.0000	0.0000	1.000	—
2	1	1.4142	1.0000	1.000	0.71
3	1	1.0000	0.0000	1.000	—
2	2	1.0000	1.0000	1.272	1.00
4	1	1.8478	1.0000	0.719	0.54
2	2	0.7654	1.0000	1.390	1.31
5	1	1.0000	0.0000	1.000	—
2	2	1.6180	1.0000	0.859	0.62
3	3	0.6180	1.0000	1.448	1.62
6	1	1.9319	1.0000	0.676	0.52
2	2	1.4142	1.0000	1.000	0.71
3	3	0.5176	1.0000	1.479	1.93
7	1	1.0000	0.0000	1.000	—
2	2	1.8019	1.0000	0.745	0.55
3	3	1.2470	1.0000	1.117	0.80
4	4	0.4450	1.0000	1.499	2.25
8	1	1.9616	1.0000	0.661	0.51
2	2	1.6629	1.0000	0.829	0.60
3	3	1.1111	1.0000	1.206	0.90
4	4	0.3902	1.0000	1.512	2.56
9	1	1.0000	0.0000	1.000	—
2	2	1.8794	1.0000	0.703	0.53
3	3	1.5321	1.0000	0.917	0.65
4	4	1.0000	1.0000	1.272	1.00
5	5	0.3473	1.0000	1.521	2.88
10	1	1.9754	1.0000	0.655	0.51
2	2	1.7820	1.0000	0.756	0.56
3	3	1.4142	1.0000	1.000	0.71
4	4	0.9080	1.0000	1.322	1.10
5	5	0.3129	1.0000	1.527	3.20

<i>n</i>	<i>i</i>	<i>a_i</i>	<i>b_i</i>	<i>f_ω/f_κ</i>	<i>Q_i</i>
Chebyshev					
1	1	1.0000	0.0000	1.000	—
2	1	1.0650	1.9305	1.000	1.30
3	1	3.3496	0.0000	0.299	—
2	2	0.3559	1.1923	1.396	3.07
4	1	2.1853	5.5339	0.557	1.08
2	2	0.1964	1.2009	1.410	5.58
5	1	5.6334	0.0000	0.178	—
2	2	0.7620	2.6530	0.917	2.14
3	3	0.1172	1.0686	1.500	8.82
6	1	3.2721	11.6773	0.379	1.04
2	2	0.4077	1.9873	1.086	3.46
3	3	0.0815	1.0861	1.489	12.78
7	1	7.9064	0.0000	0.126	—
2	2	1.1159	4.8963	0.670	1.98
3	3	0.2515	1.5944	1.222	5.02
4	4	0.0582	1.0348	1.527	17.46
8	1	4.3583	20.2948	0.286	1.03
2	2	0.5791	3.1808	0.853	3.08
3	3	0.1765	1.4507	1.285	6.83
4	4	0.0448	1.0478	1.517	22.87
9	1	10.1759	0.0000	0.098	—
2	2	1.4585	7.8971	0.526	1.93
3	3	0.3561	2.3651	1.001	4.32
4	4	0.1294	1.3165	1.351	8.87
5	5	0.0348	1.0210	1.537	29.00
10	1	5.4449	31.3788	0.230	1.03
2	2	0.7414	4.7363	0.699	2.94
3	3	0.2479	1.9952	1.094	5.70
4	4	0.1008	1.2638	1.380	11.15
5	5	0.0283	1.0304	1.530	35.85

<i>n</i>	<i>i</i>	<i>a_i</i>	<i>b_i</i>	<i>f_ω/f_κ</i>	<i>Q_i</i>
Bessel					
1	1	1.0000	0.0000	1.000	—
2	1	1.3617	0.6180	1.000	0.58
3	1	0.7560	0.0000	1.323	—
2	2	0.9996	0.4772	1.414	0.69
4	1	1.3397	0.4889	0.978	0.52
2	2	0.7743	0.3890	1.797	0.81
5	1	0.6656	0.0000	1.502	—
2	2	1.1402	0.4128	1.184	0.56
3	3	0.6216	0.3245	2.138	0.92
6	1	1.2217	0.3887	1.063	0.51
2	2	0.9686	0.3505	1.431	0.61
3	3	0.5131	0.2756	2.447	1.02
7	1	0.5937	0.0000	1.684	—
2	2	1.0944	0.3395	1.207	0.53
3	3	0.8304	0.3011	1.695	0.66
4	4	0.4332	0.2381	2.731	1.13
8	1	1.1112	0.3162	1.164	0.51
2	2	0.9754	0.2979	1.381	0.56
3	3	0.7202	0.2621	1.963	0.71
4	4	0.3728	0.2087	2.992	1.23
9	1	0.5386	0.0000	1.857	—
2	2	1.0244	0.2834	1.277	0.52
3	3	0.8710	0.2636	1.574	0.59
4	4	0.6320	0.2311	2.226	0.76
5	5	0.3257	0.1854	3.237	1.32
10	1	1.0215	0.2650	1.264	0.50
2	2	0.9393	0.2549	1.412	0.54
3	3	0.7815	0.2351	1.780	0.62
4	4	0.5604	0.2059	2.479	0.81
5	5	0.2883	0.1665	3.466	1.42

Model templates:

2021.11.02 - Practice - Bandpass filters.asc

2021.11.02 - Practice - Bandpass filters.plt

OPAMP_VXX.lib



Stage 3 -Save a screenshot of your LTSPICE schematic

Specify your personal .lib file according to your variant.

Right-click to edit:

.lib OPAMP_V10.lib

Simulation parameters:

Transient analysis parameters:

*.tran 0 {10*1/f_test} {0*1/f_test} {1/f_test/200} ulc

Time step parameters:

Signal source voltage amplitude [V]:

.param V_test=1

Step source voltage amplitude [V]:

.param V_step=0

Signal source voltage frequency [Hz]:

.param f_test=1k

AC sweep analysis parameters:

.ac dec 100 0.1 1000000

Signal source voltage amplitude AC [V]:

.param V_test_AC={V_test}

Element parameters for simulation:

R1 [Ω]:

.param R1=10k

R2 [Ω]:

.param R2=50k

R3 [Ω]:

.param R3=10k

C1 [F]:

.param C1=10n

C2 [F]:

.param C2=10n

C3 [F]:

.param C3=10n

Load resistance R_load [Ω]:

.param R_load =1000k

Power supply source voltage VPP+[V]:

.param Vpp_plus=12

Power supply source voltage VPP-[V]:

.param Vpp_minus=12

Step for R1 Tolerance

*.step param R1 list 9500 10000 10500

Step for R2 Tolerance

*.step param R2 list 9500 10000 10500

Step for R3 Tolerance

*.step param R3 list 9500 10000 10500

Step for C1 Tolerance

.step param C1 list 9500p 10000p 10500p

Step for C2 Tolerance

.step param C2 list 9500p 10000p 10500p

Step for C3 Tolerance

.step param C3 list 9500p 10000p 10500p

Step for R_load


*.step param R_load list 0.01k 0.1k 10k 50k 100k

This line is required to simulate ideal OpAMP:


.lib opamp.sub

Stage 1 Multiple Feedback (Bandpass)

REAL OPERATIONAL AMPLIFIER

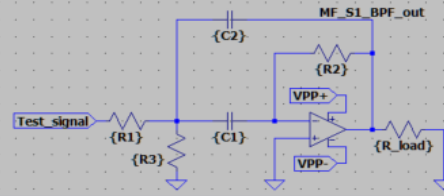


IDEAL OPERATIONAL AMPLIFIER

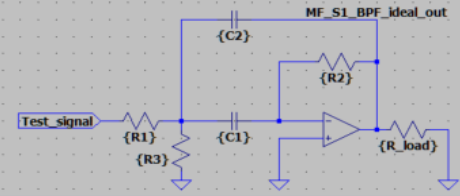


Stage 1 Multiple Feedback (Bandpass)

REAL OPERATIONAL AMPLIFIER

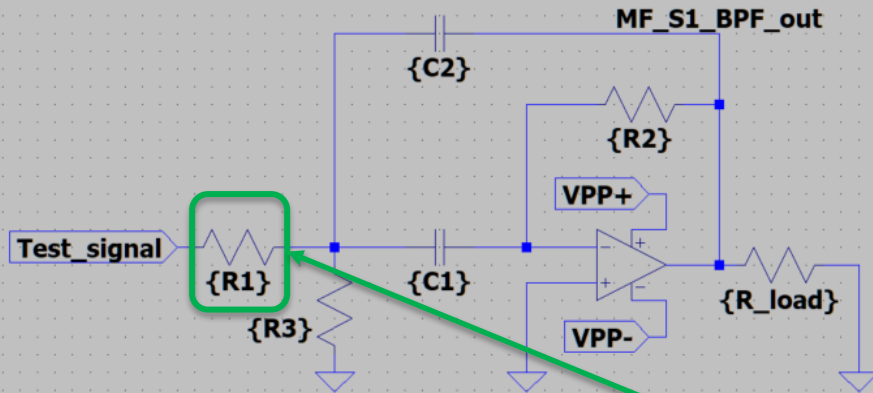

IDEAL OPERATIONAL AMPLIFIER

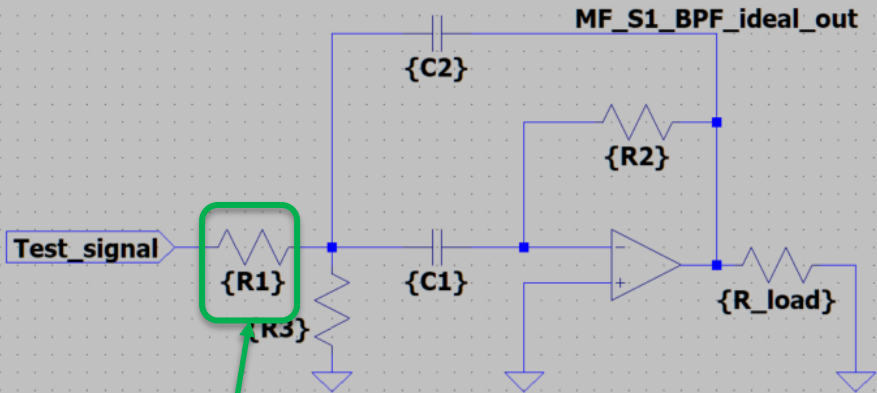

Element parameters for simulation:

R1 [Ω]:

R2 [Ω]:

R3 [Ω]:

C1 [F]:

C2 [F]:

C3 [F]:

.param R1=

.param R2=

.param R3=

.param C1=

.param C2=


.param C3=

R_1


You have R1, R2, R3 in the task and you have to choose C1, C2 by yourself to provide f_0 value from your variant

Stage 1 Multiple Feedback (Bandpass)

REAL OPERATIONAL AMPLIFIER

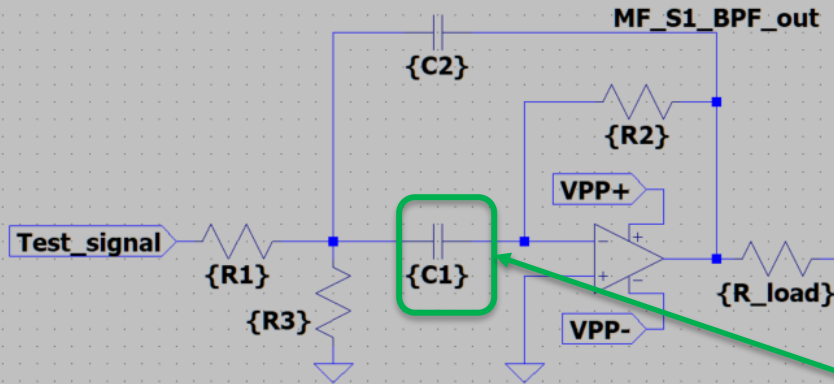

IDEAL OPERATIONAL AMPLIFIER

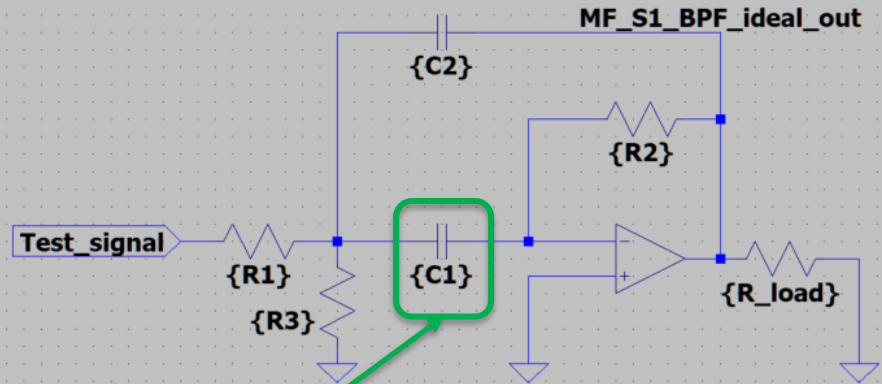

Element parameters for simulation:

R1 [Ω]:

R2 [Ω]:

R3 [Ω]:

C1 [F]:

C2 [F]:

C3 [F]:

.param R1=

.param R2=

.param R3=

.param C1=

.param C2=


.param C3=

C_1


You have R1, R2, R3 in the task and you have to choose C1, C2 by yourself to provide f_0 value from your variant

Stage 1 Multiple Feedback (Bandpass)

REAL OPERATIONAL AMPLIFIER

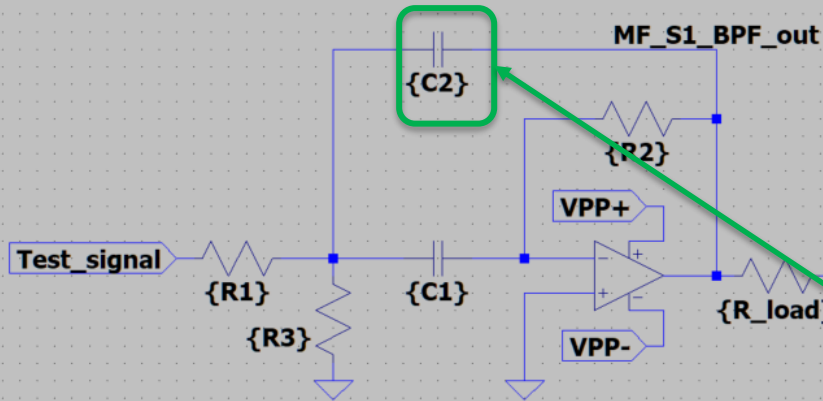

IDEAL OPERATIONAL AMPLIFIER

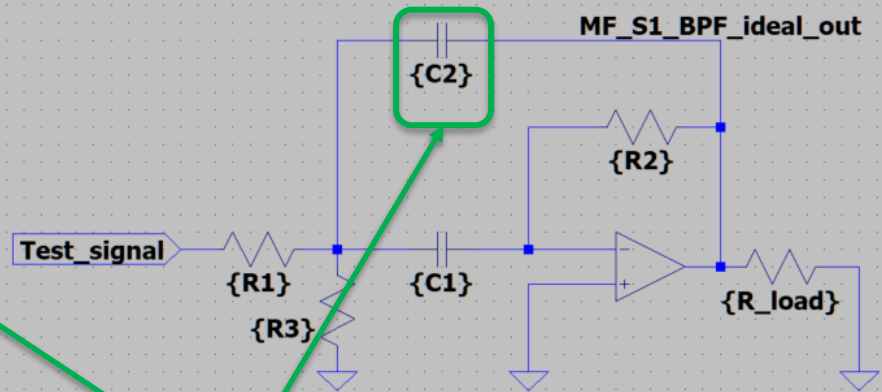

Element parameters for simulation:

R1 [Ω]:

R2 [Ω]:

R3 [Ω]:

C1 [F]:

C2 [F]:

C3 [F]:

.param R1=

.param R2=

.param R3=

.param C1=

.param C2=


.param C3=

C_2


You have R1, R2, R3 in the task and you have to choose C1, C2 by yourself to provide f_0 value from your variant

Stage 1 Multiple Feedback (Bandpass)

REAL OPERATIONAL AMPLIFIER

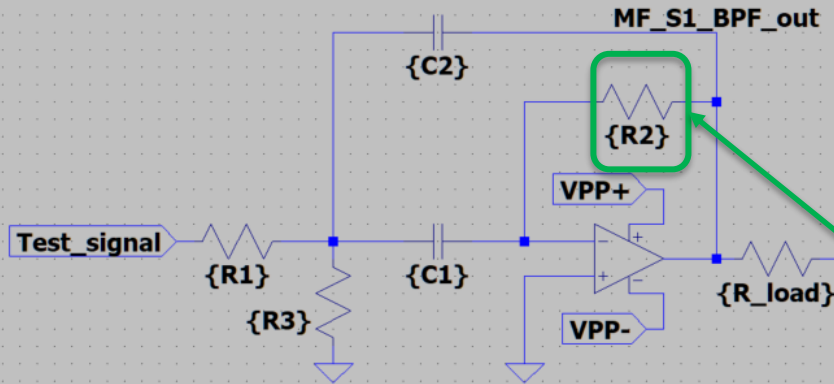

IDEAL OPERATIONAL AMPLIFIER

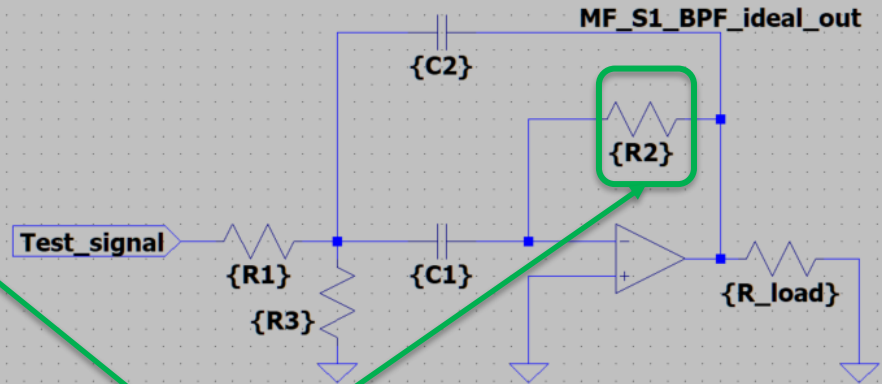

Element parameters for simulation:

R1 [Ω]:

R2 [Ω]:

R3 [Ω]:

C1 [F]:

C2 [F]:

C3 [F]:

.param R1=

.param R2=

.param R3=

.param C1=

.param C2=


.param C3=

R_2


You have R1, R2, R3 in the task and you have to choose C1, C2 by yourself to provide f_0 value from your variant

Stage 1 Multiple Feedback (Bandpass)

REAL OPERATIONAL AMPLIFIER

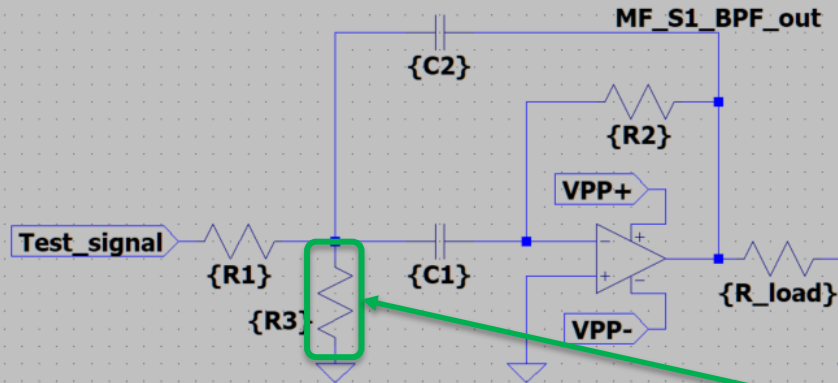

IDEAL OPERATIONAL AMPLIFIER

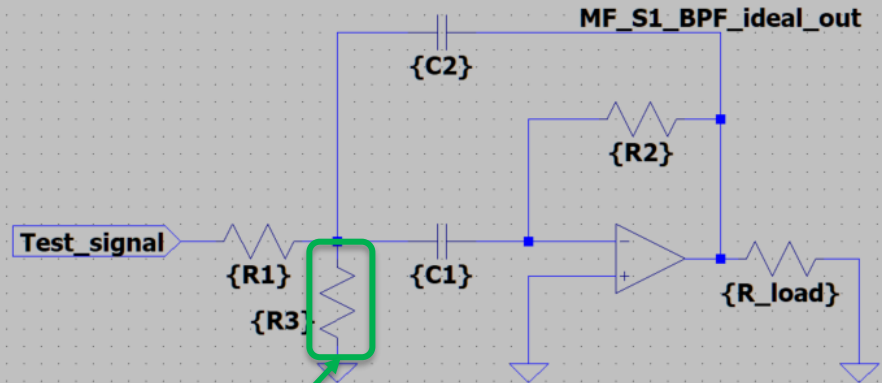

Element parameters for simulation:

R1 [Ω]:

R2 [Ω]:

R3 [Ω]:

C1 [F]:

C2 [F]:

C3 [F]:

.param R1=

.param R2=

.param R3=

.param C1=

.param C2=


.param C3=

R_3


You have R1, R2, R3 in the task and you have to choose C1, C2 by yourself to provide f_0 value from your variant

Stage 1 Multiple Feedback (Bandpass)

REAL OPERATIONAL AMPLIFIER

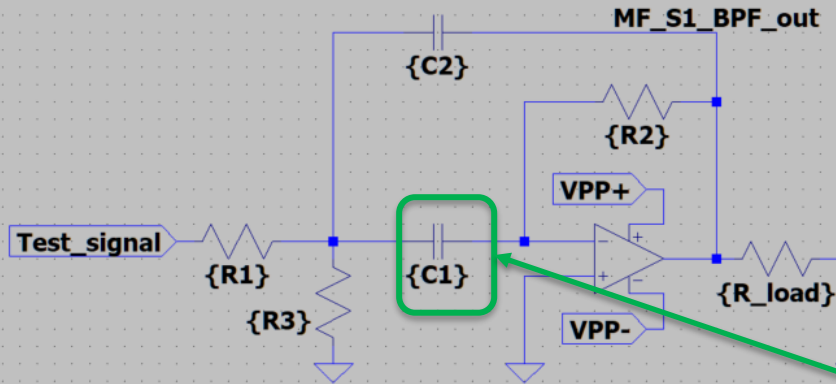

IDEAL OPERATIONAL AMPLIFIER

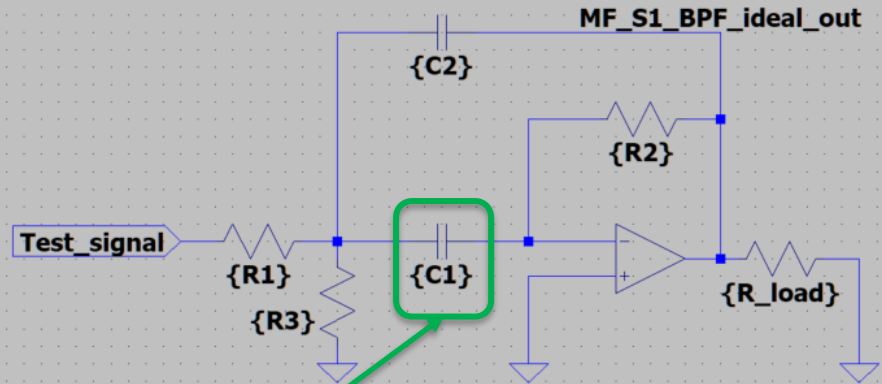

Element parameters for simulation:

R1 [Ω]:

R2 [Ω]:

R3 [Ω]:

C1 [F]:

C2 [F]:

C3 [F]:

.param R1=

.param R2=

.param R3=

.param C1=

.param C2=


.param C3=

C_1


You have R1, R2, R3 in the task and you have to choose C1, C2 by yourself to provide f_0 value from your variant

Stage 1 Multiple Feedback (Bandpass)

REAL OPERATIONAL AMPLIFIER

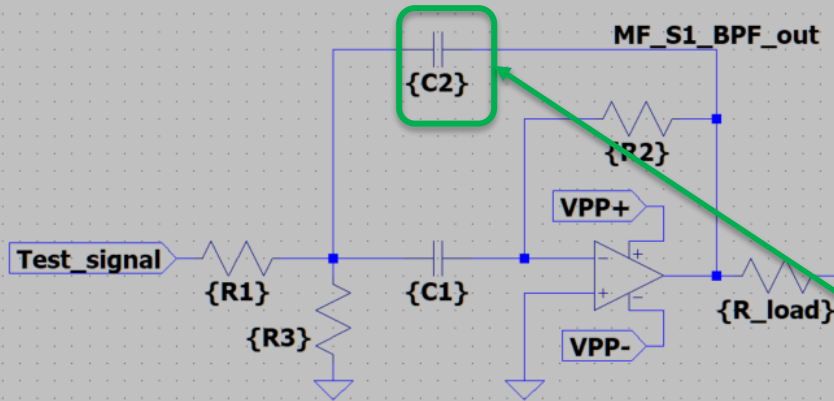

IDEAL OPERATIONAL AMPLIFIER

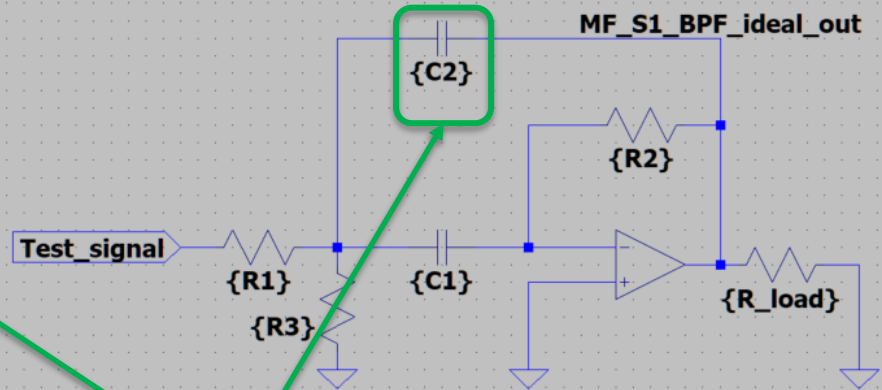

Element parameters for simulation:

R1 [Ω]:

R2 [Ω]:

R3 [Ω]:

C1 [F]:

C2 [F]:

C3 [F]:

.param R1=

.param R2=

.param R3=

.param C1=

.param C2=

.param C3=


C_2

You have R1, R2, R3 in the task and you have to choose C1, C2 by yourself to provide f_0 value from your variant

Stage 1 Sallen-Key (Bandpass)

REAL OPERATIONAL AMPLIFIER

IDEAL OPERATIONAL AMPLIFIER

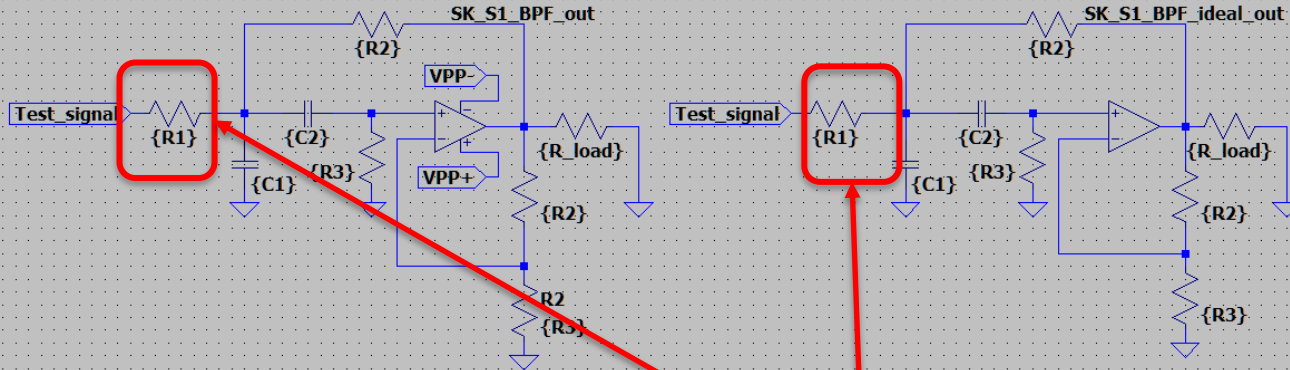

Element parameters for simulation:

R1 [Ω]:

R2 [Ω]:

R3 [Ω]:

C1 [F]:

C2 [F]:

C3 [F]:

.param R1=

.param R2=

.param R3=

.param C1=


.param C2=

.param C3=

R_1

You have R1, R2, R3 in the task and you have to choose C1, C2 by yourself to provide f0 value from your variant

Stage 1 Sallen-Key (Bandpass)

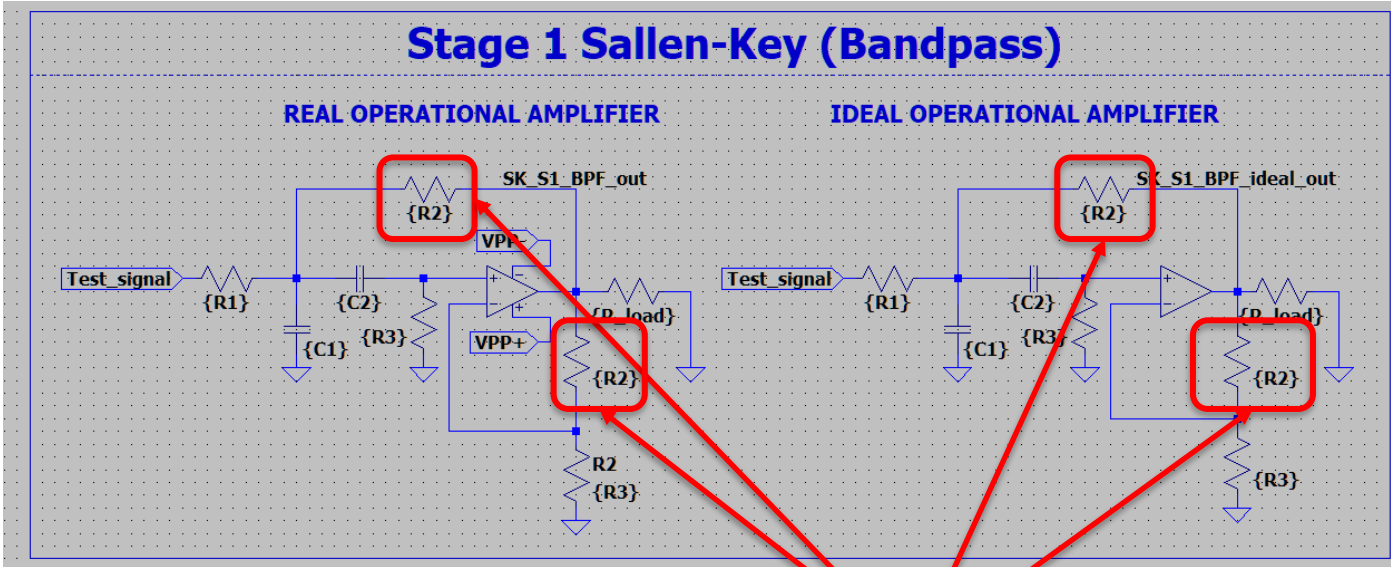

Element parameters for simulation:

R1 [Ω]:

R2 [Ω]:

R3 [Ω]:

C1 [F]:

C2 [F]:

C3 [F]:

.param R1=

.param R2=

.param R3=

.param C1=


.param C2=

.param C3=

R_2

You have R1, R2, R3 in the task and you have to choose C1, C2 by yourself to provide f_0 value from your variant

Stage 1 Sallen-Key (Bandpass)

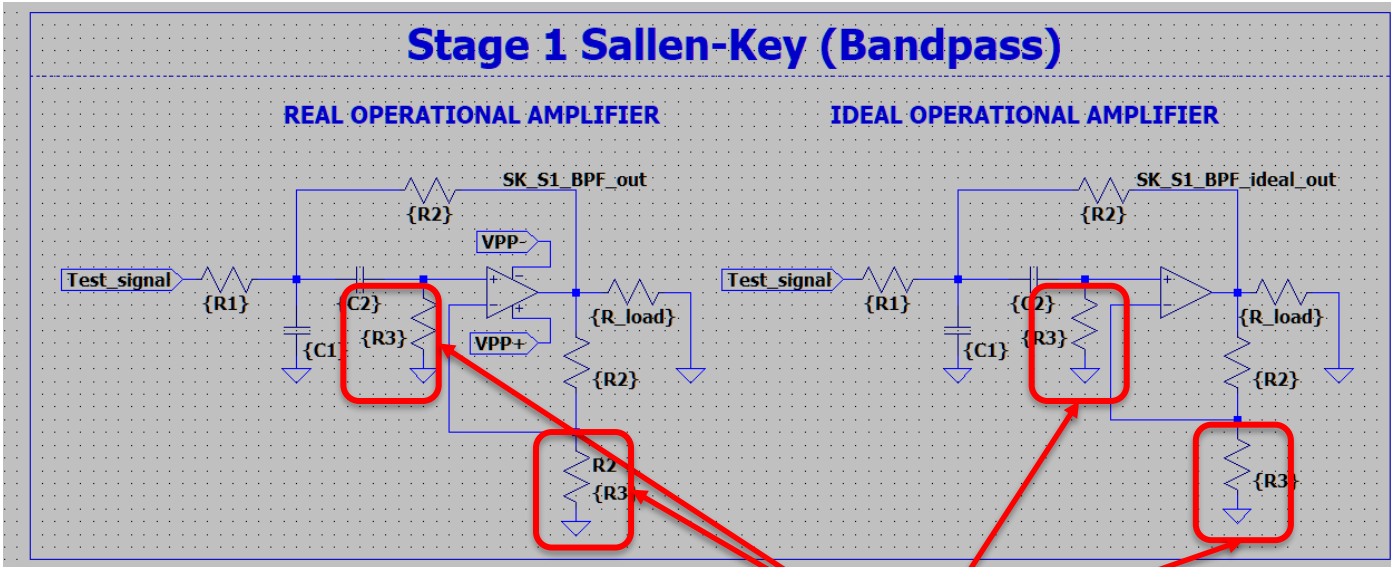


Element parameters for simulation:

R1 [Ω]:	.param R1=
R2 [Ω]:	.param R2=
R3 [Ω]:	.param R3=
C1 [F]:	.param C1=
C2 [F]:	.param C2=
C3 [F]:	.param C3=

R_3

You have R1, R2, R3 in the task and you have to choose C1, C2 by yourself to provide f_0 value from your variant

Stage 1 Sallen-Key (Bandpass)

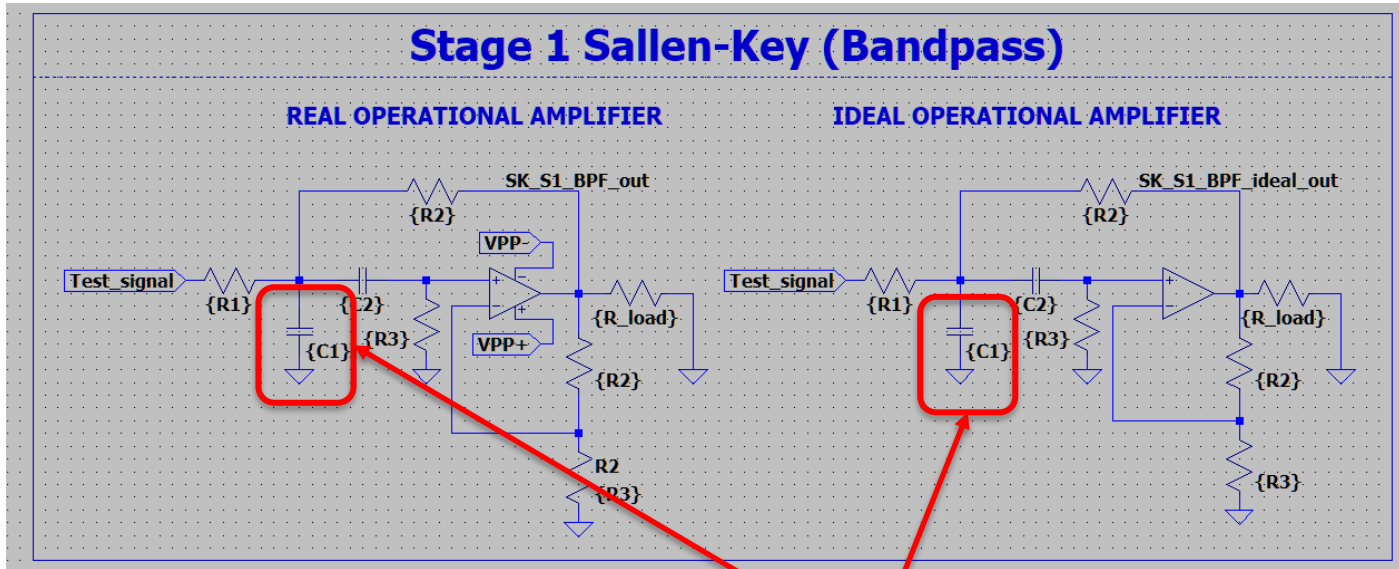


Element parameters for simulation:

R1 [Ω]:	.param R1=
R2 [Ω]:	.param R2=
R3 [Ω]:	.param R3=
C1 [F]:	.param C1=
C2 [F]:	.param C2=
C3 [F]:	.param C3=

C_1

You have R1, R2, R3 in the task and you have to choose C1, C2 by yourself to provide f_0 value from your variant

Stage 1 Sallen-Key (Bandpass)

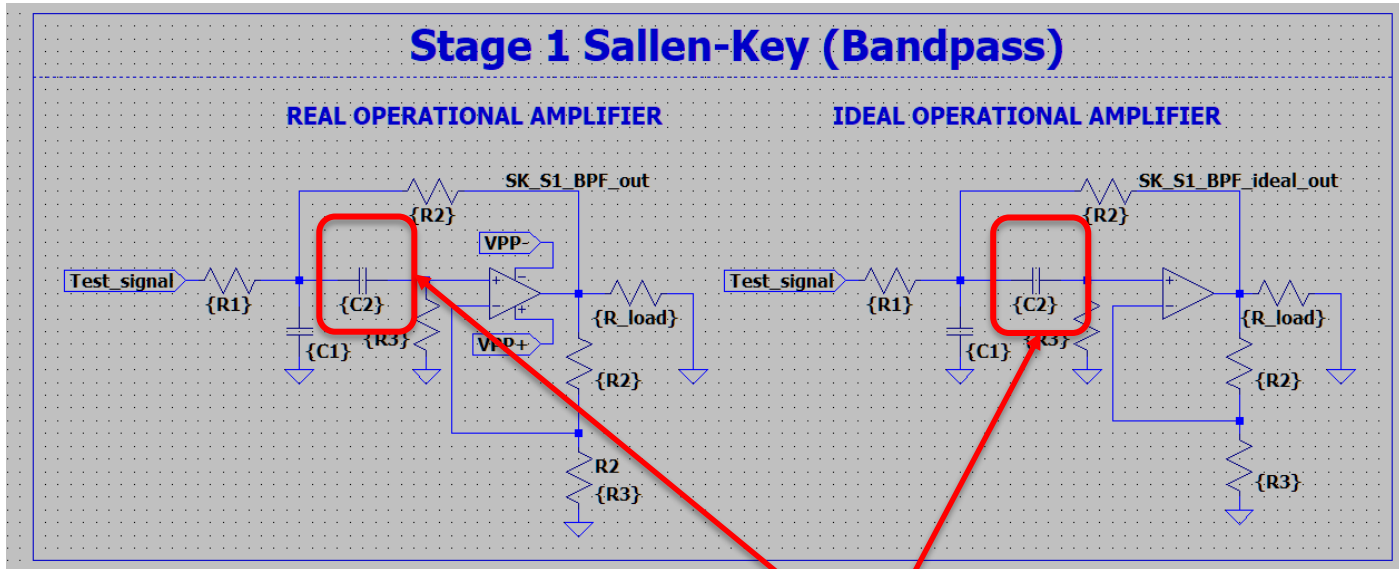

Element parameters for simulation:



R1 [Ω]:	.param R1=
R2 [Ω]:	.param R2=
R3 [Ω]:	.param R3=
C1 [F]:	.param C1=
C2 [F]:	.param C2=
C3 [F]:	.param C3=

C_2

You have R1, R2, R3 in the task and you have to choose C1, C2 by yourself to provide f_0 value from your variant



Define the bandwidth in **Hz** from simulation results of scheme with an **ideal** operational amplifier

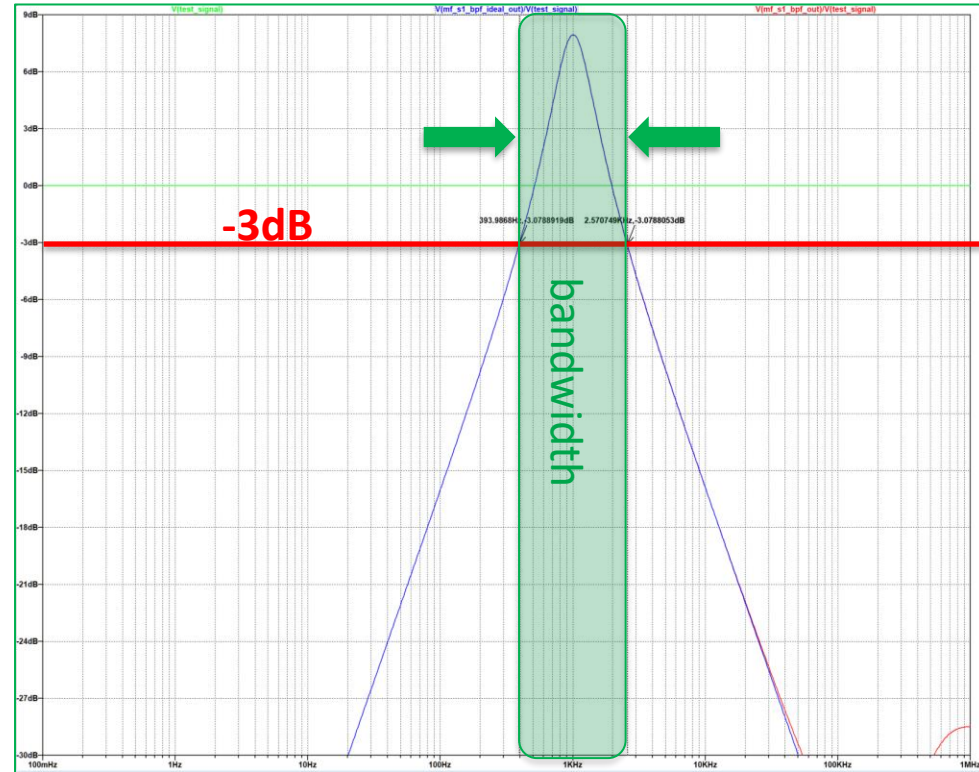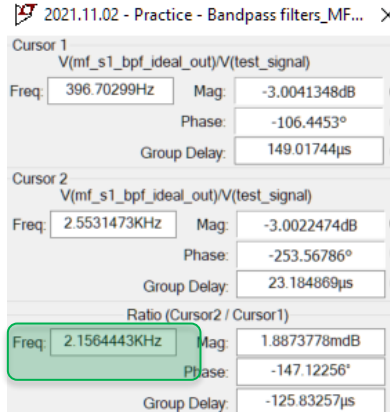Define the bandwidth in **Hz** from simulation results of scheme with a **real** operational amplifier




Define f_0 as a middle of bandwidth from simulation results of scheme with an **ideal** operational amplifier

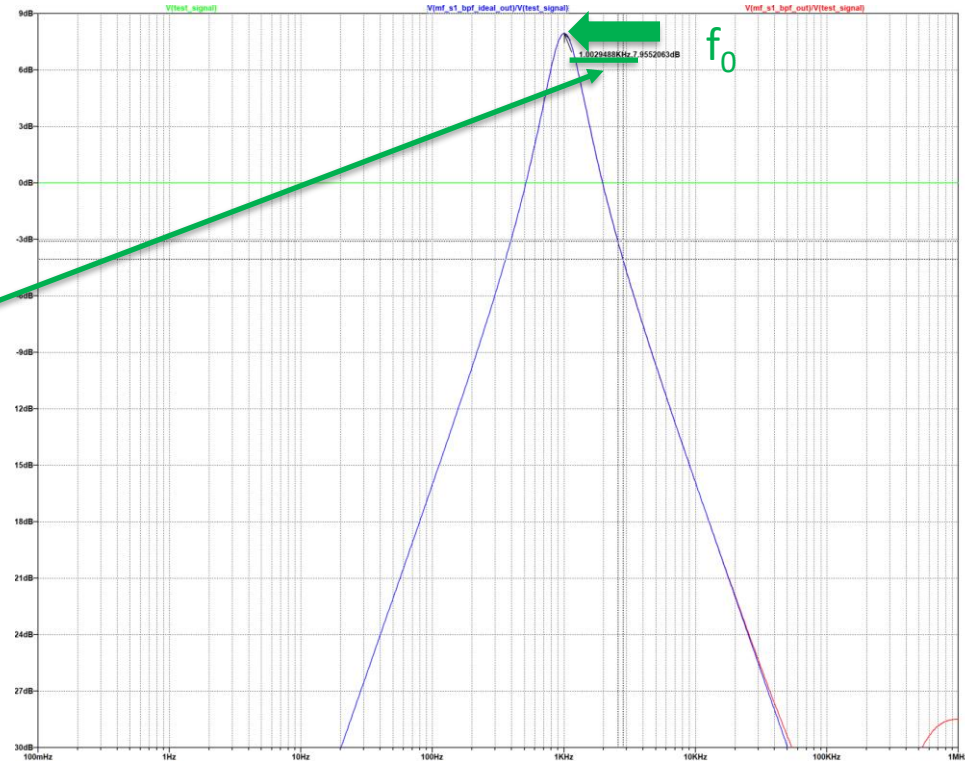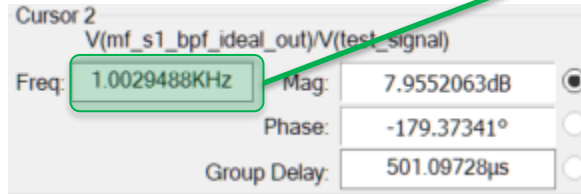Define f_0 as a middle of bandwidth from simulation results of scheme with a **real** operational amplifier



Sallen-Key Band Pass Active Filter

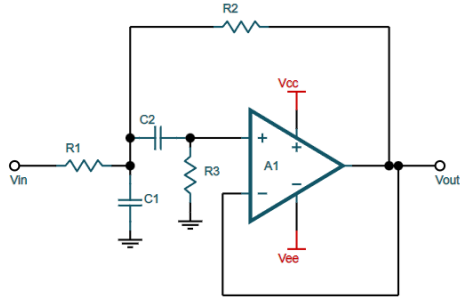

$$B = f_0(3-K) \text{ [Hz]}$$

$$C_1 = C_2 = C$$

$$R_1 = R_2 = \frac{1}{2} R_3 = R$$

$$R_3 = 2R$$


$$\text{Max gain } K = 1 + \frac{R_2}{R_3}$$

Middle frequency of bandpass: $\omega_0 = \frac{1}{RC} \text{ [rad/s]}$



Bandwidth: $B = \omega_0(3-K) \text{ [rad/s]}$

$$f_0 = \frac{1}{2\pi \cdot RC} \text{ [Hz]}$$

$$B = f_0(3-K) \text{ [Hz]}$$

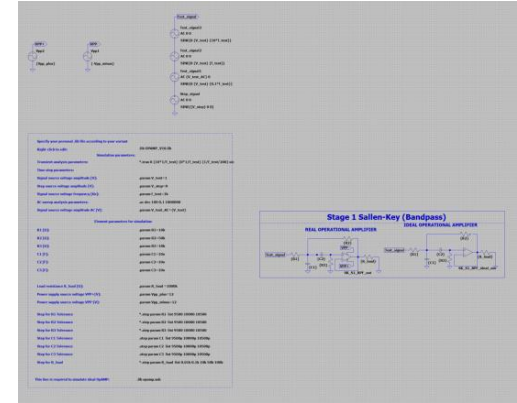

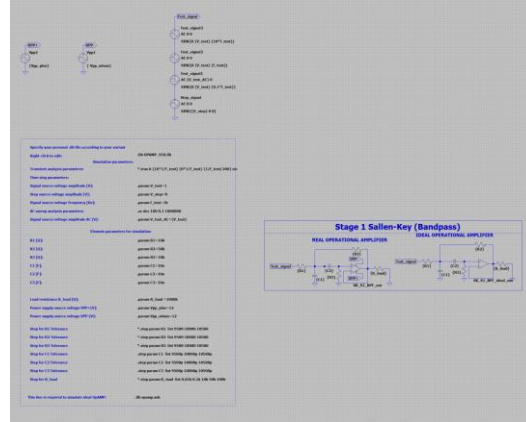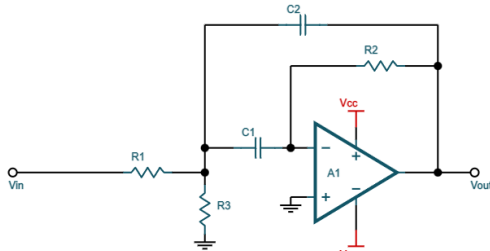Multiple Feedback Band Pass Active Filter



the characteristics of the IGMF filter

$$\frac{U_{out}(p)}{U_{in}(p)} = - \frac{\frac{R_2 R_3}{R_1 + R_3} C \omega_0 p}{\frac{R_1 R_2 R_3}{R_1 + R_3} C^2 \omega_0^2 p^2 + \frac{2 R_1 R_3}{R_1 + R_3} C \omega_0 p + 1}$$

$$Max\ gain \approx - \frac{R_2}{2 R_1} = 2 Q^2$$


$$f_0 = \frac{1}{2\pi \cdot C} \sqrt{\frac{R_1 + R_3}{R_1 R_2 R_3}} \text{ [Hz]}$$

$$C_1 = C_2 = C$$


Middle frequency of bandpass: $\omega_0 = \frac{1}{C} \sqrt{\frac{R_1 + R_3}{R_1 R_2 R_3}} \text{ [rad/s]}$

$$\text{Bandwidth: } B = \frac{1}{\pi \cdot R_2 C}$$

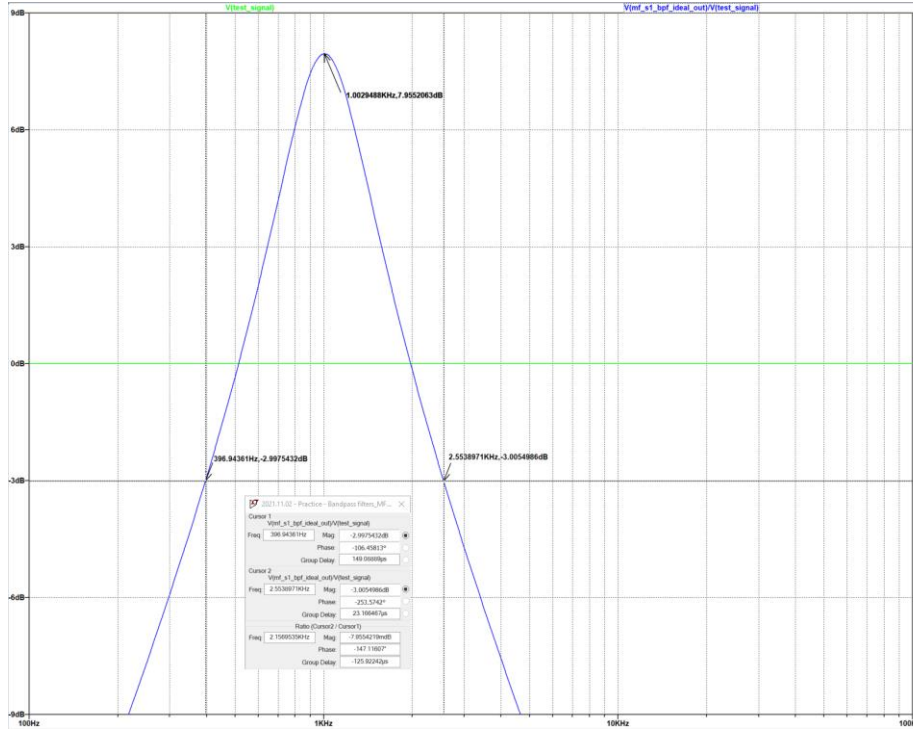
Stage 3 - Save a screenshot of your simulation results with frequency estimation



Ideal OpAMP

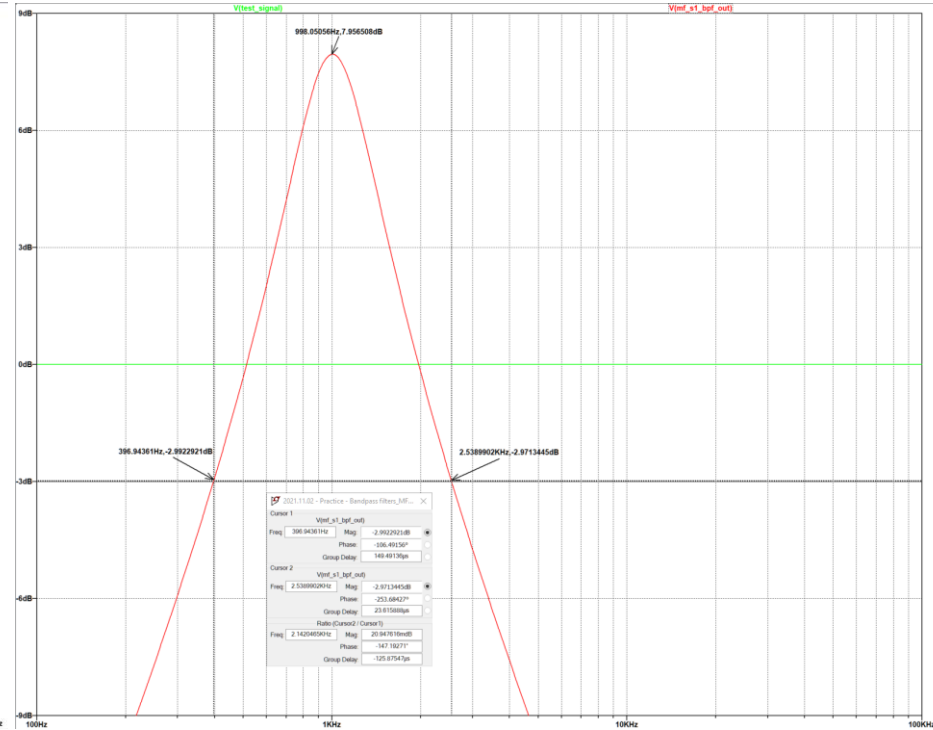


Real OpAMP

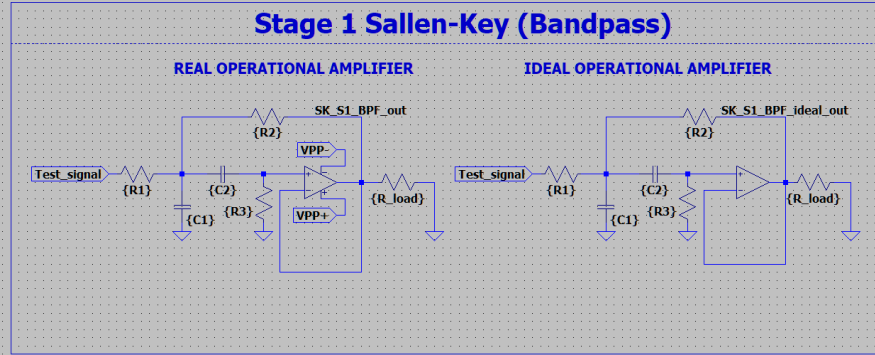

BEFORE

Max gain $K = 1$ (always)
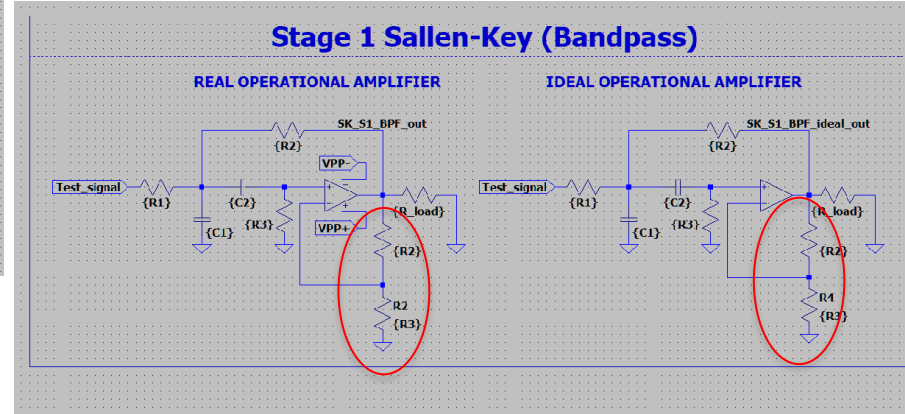
$$K_{\omega 0} = \frac{K}{3 - K} = 0,5 \text{ (-6dB)}$$



AFTER


Max gain $K = 1 + \frac{R_2}{R_3} = 1,5$ (in the task)



$$K_{\omega 0} = \frac{K}{3 - K} = 1 \text{ (0 dB)}$$


<https://forms.yandex.com/cloud/6379029df47e7378d18aa0c4/>

<https://clck.ru/32kU7G>

1st deadline: 23.11.2022 15:15 (GMT +8)

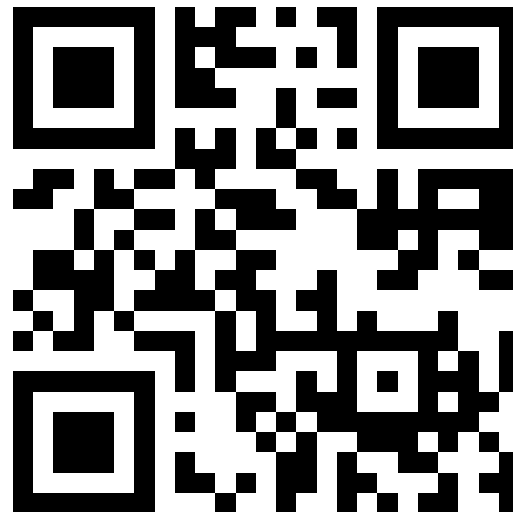


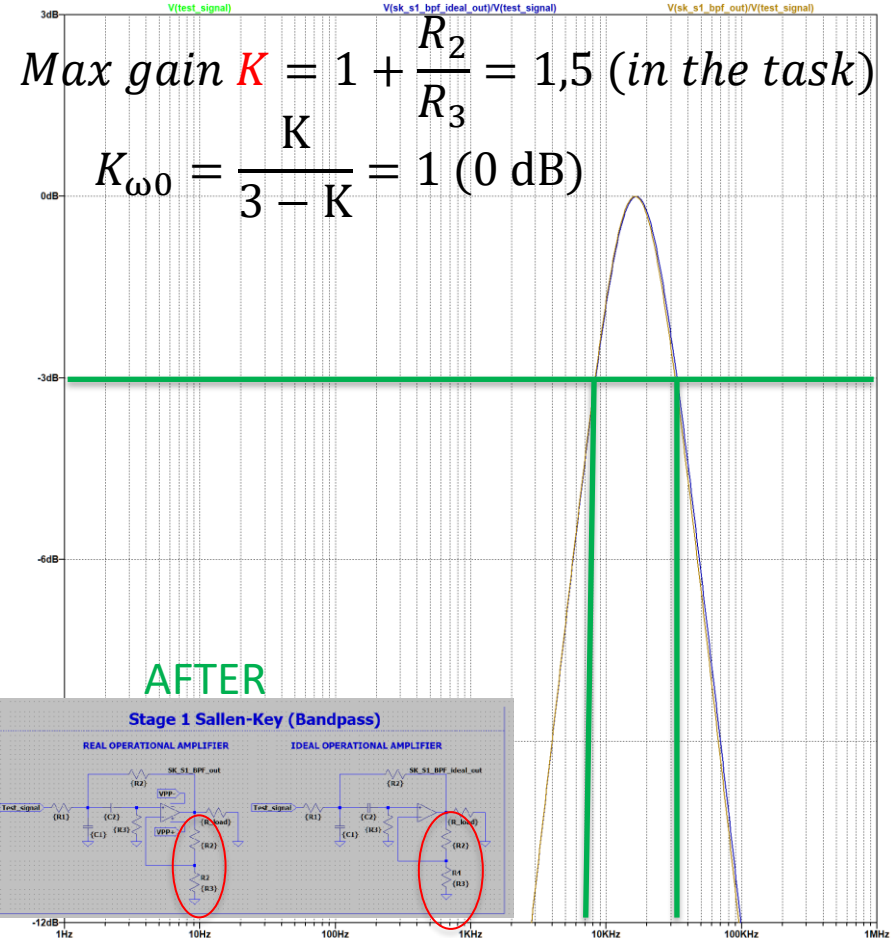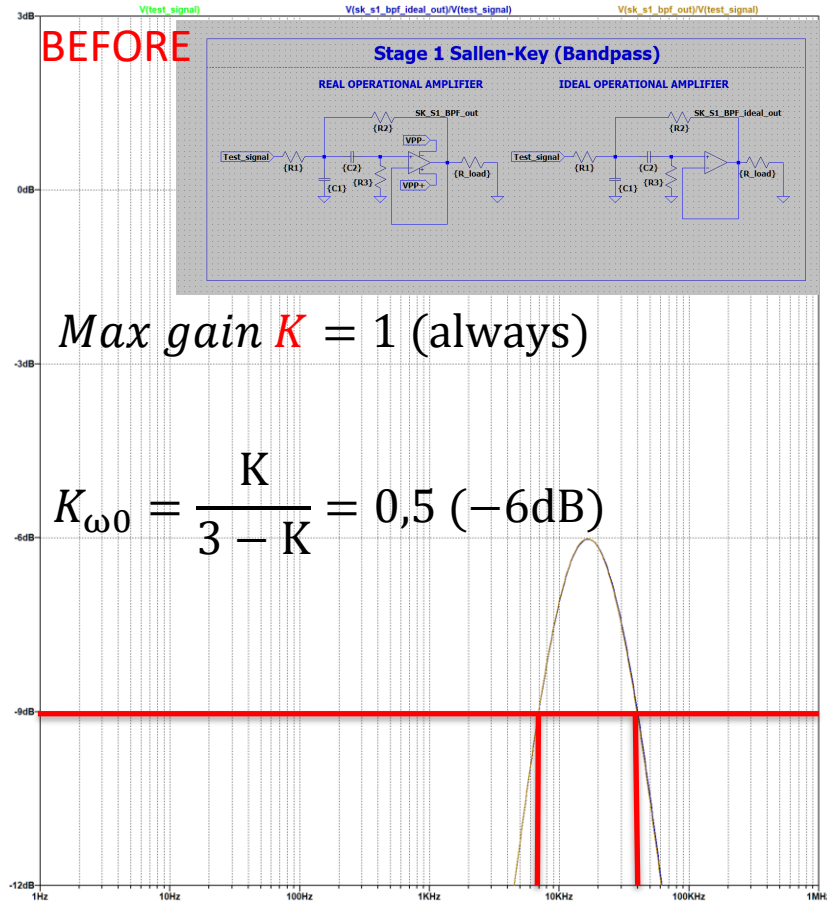

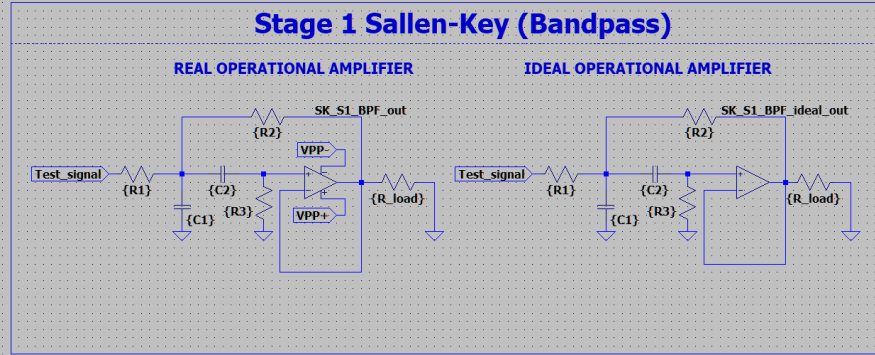

Good news: all evaluations for C1/C2 are correct and the same for both cases

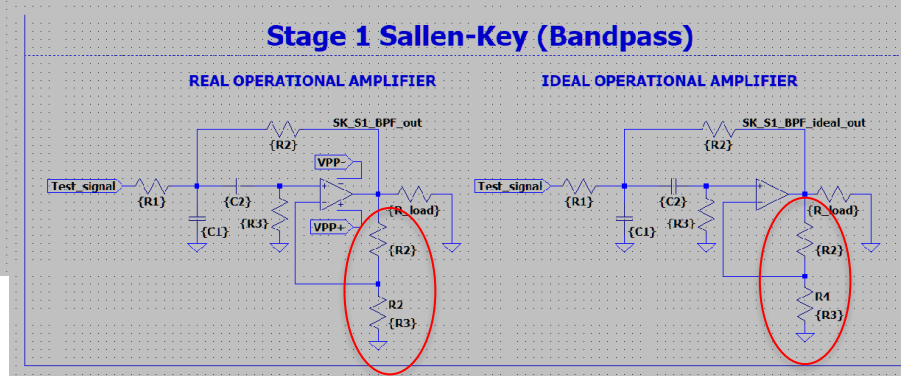You may define the bandwidth at -9dB instead of -3dB or fix the scheme and makes new pictures with a new gain



AFTER

$$\text{Max gain } K = 1 + \frac{R_2}{R_3} = 1,5 \text{ (in the task)}$$

$$K_{\omega 0} = \frac{K}{3 - K} = 1 \text{ (0 dB)}$$

The background features a dark gray grid pattern. In the top right and bottom left corners, there are decorative wavy lines in a vibrant purple color, creating a modern, abstract aesthetic.

iTMO

Thanks for your attention!