



Parametric linear voltage regulator

Nikolay Nikolaev

(nanikolaev@itmo.ru)


Nikolai Poliakov

(polyakov_n_a@itmo.ru)

Roman Olekhnovich

(r.o.olekhnovich@mail.ru)

 1. Parametric linear voltage regulator
2. Control test



$$R_V = \frac{\min V_R}{\min I_D + \max I_L / (h_{FE} + 1)},$$


where

$\min V_R$ is the minimum voltage to be maintained across R_V ,

$\min I_D$ is the minimum current to be maintained through the Zener diode,

$\max I_L$ is the maximum design load current,

 h_{FE} is the forward current gain of the transistor (I_C/I_B).



$$R_V = \frac{\min V_R}{\min I_D + \max I_L / (h_{FE} + 1)},$$

where

min V_R is the minimum voltage to be maintained across R_V ,

min I_D is the minimum current to be maintained through the Zener diode,

max I_L is the maximum design load current,

h_{FE} is the forward current gain of the transistor (I_C/I_B).

1. Calculate load current

$$I_L = \frac{V_{out}}{R_L}$$

2. Define required stabilized voltage


$$V_Z = V_{out} + V_{BE}$$

3. Chose the transistor according to the requirement

$$V_{CE_max} = (1.5 \dots 2)V_{in_max}; I_{C_max} > 2I_L$$

 4. Choose R_v is selected based on the condition that current should flow through the transistor at a minimum input voltage

$$R_v = \frac{V_Z}{(1.5 \dots 2)I_Z + \frac{V_{out}}{R_L(1 + h_{FE})}}$$



<https://forms.yandex.com/cloud/6363408243f74f24464db4b5/>

<https://clck.ru/32Zfm6>

1st deadline: 04.11.2022 15:15 (GMT +8)



The background is a dark purple grid. In the top right corner, there is a wavy white line that curves downwards and to the right. In the bottom left corner, there is a similar wavy white line that curves upwards and to the right.

iTMO

Thank you for your attention!