

LABORATORY WORK REPORT №1
«Simple semiconductor device circuits design and simulation»
(Includes Practice 1 Report)
Principles of Circuits

Student: CAO Xinyang 20321308
Program of Automation/ of Computer Science and Technology

group №
Name Surname

1. Work purpose: to study parameters of semiconductor elements and basis of the semiconductor device design

Goals:

- 1) Design rectifier model on the basis of diode «diode name»
- 2) Simulate rectifier scheme and analyze dependencies of DC voltage ripple from load and filter capacitor values variation
- 3) Simulate overvoltage and overcurrent states (optional)

2. Starting data

2.1.1. Parameters of the voltage source:

- One-phase sine voltage source
- Rectifier scheme: Half-Wave Rectifier (HWR) /Central tap rectifier (CTR) /Full -Bridge rectifier (FBR)
- Source voltage amplitude
$$V_s = 50 \quad (\text{V})$$
- Source voltage frequency
$$f = 100 \quad (\text{Hz})$$

2.1.2. Diode: (copy the 1stand the second line of .lib file of your variant)

2.1.3. Required parameters of DC output:

- Load resistance:
$$R_L = R_{\text{LOAD_HWR/CTR/FBR}} = 180 \quad (\text{V})$$
- Desired DC voltage ripple factor:
$$K_p = .035$$

3. Simulation report

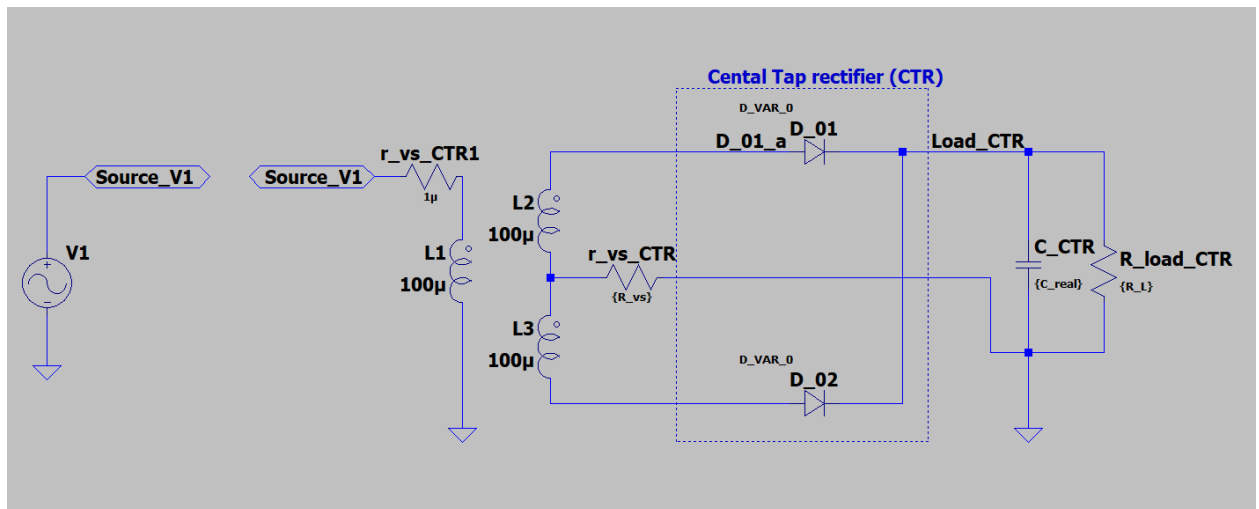


Fig. 3.1 – Rectifier scheme model

3.1.1. Filter parameters:

— $C_{real} =$ 300 (uF)

3.1.2. Load parameters:

— $R_L = R_{LOAD_HWR} =$ 180 (Ω)

— $V_{RLAVG} =$ 46.84 (V)

— $V_{RLRMS} =$ 46.91 (V)

— $K_p = K_p = \frac{\Delta V_{RL}}{2V_{RLAVG}} =$ 0.035

— $I_{VDON} =$ 28.69 (A)

— $I_{VDmax} =$ 1.81 (A)

— $\Delta V_{RL} =$ 3.28 (V)

3.2. Simulation results

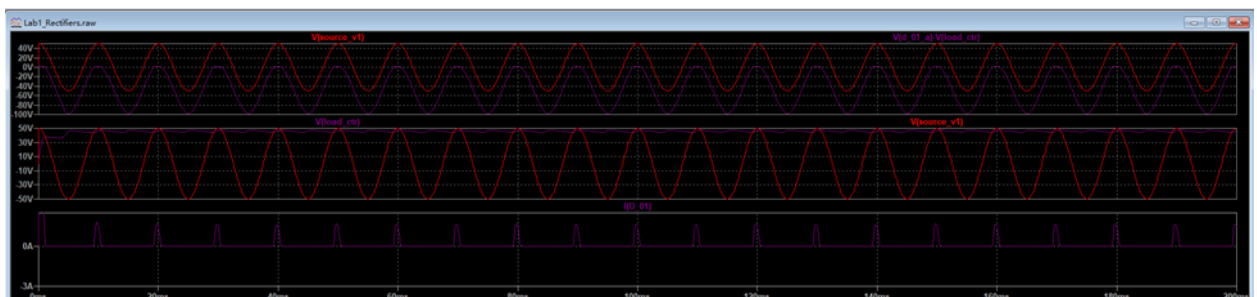


Fig 3.2 – Simulation results


3.2.1. Ripple factor:

Required:

$$— K_p = \underline{\hspace{10em}} 0.035$$

Simulated with $0.8 C_{real}$
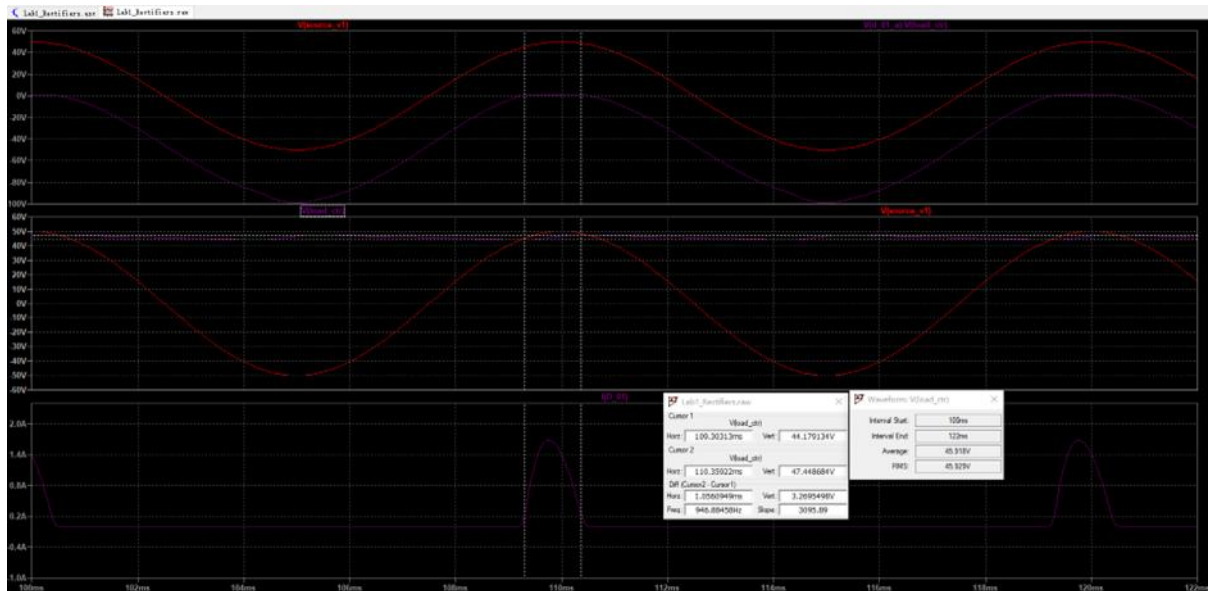
$$— K_{P_EXP} = \underline{\hspace{10em}} 0.034$$



b) Full-bridge rectifier

Fig 3.3 –Voltage ripple analysis

To define Average and RMS values use CTRL+left click mouse button on the signal name. Use 2-3 Voltage periods in the end of simulation interval

Right-click with mouse on the signal name gives access to the signal cursor

3.2.2. Voltage ripple from simulation results

$$V_{R_{L_{AVG}}exp} = 45.918 \quad (V)$$

$$V_{R_{L_{RMS}}exp} = 45.929 \quad (V)$$

$$V_{R_{Lmax}} = 47.45 \quad (V)$$

$$V_{R_{Lmin}} = 44.18 \quad (V)$$

$$\Delta V_{R_{Lexp}} = V_{R_{Lmax}} - V_{R_{Lmin}} = 3.27 \quad (V)$$

3.2.3. Ripple factor

$$K_{Pexp} = \sqrt{\left(\frac{V_{R_{L-RMS}}}{V_{R_{L-AVG}}}\right)^2 - 1} = 0.021$$

$$K_{pRMS} \approx \sqrt{\left(\frac{V_{RLRMS}}{V_{RLAVG}}\right)^2 - 1} \approx \frac{\frac{V_{RLmax} - V_{RLmin}}{2\sqrt{3}}}{V_{RLAVGexp}} = 0.021$$

3.2.4. Diode opening state angle:

$$\tau_1 = 0.00107 \quad (s)$$

$$\theta_{exp} = \tau_1 \cdot f \cdot 2\pi = \frac{\tau_1}{T} \cdot 2\pi = 0.672 \quad (rad)$$

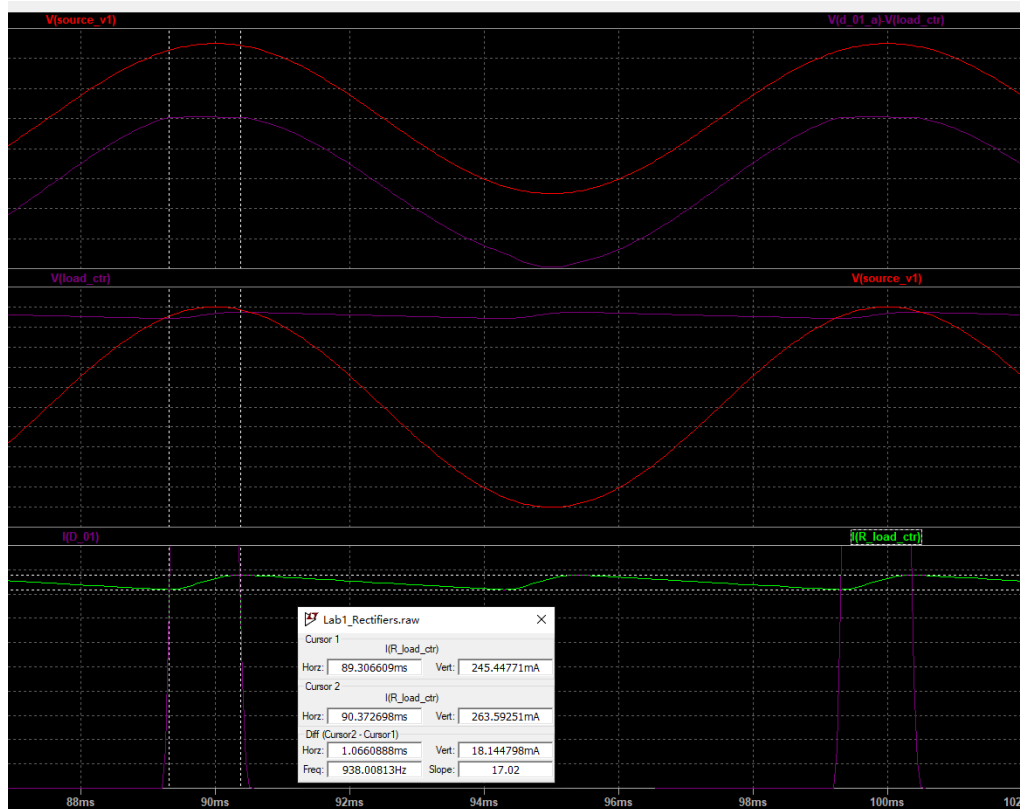


Fig 3.4 – θ_{exp} angle definition from simulation results

(It is recommended to consider diode open state at current level 0.05-0.1A or determine theta on the capacitor charging interval)

3.2.5. Average rectifier scheme diode current (To define Average and RMS values use CTRL+left click mouse button on the signal name. Use 2-3 Voltage periods in the end of simulation interval)

$$I_{VDexp} = 0.133 \quad (A)$$

3.2.6. Starting (Non-repetitive) maximum peak surge diode current in rectifier scheme

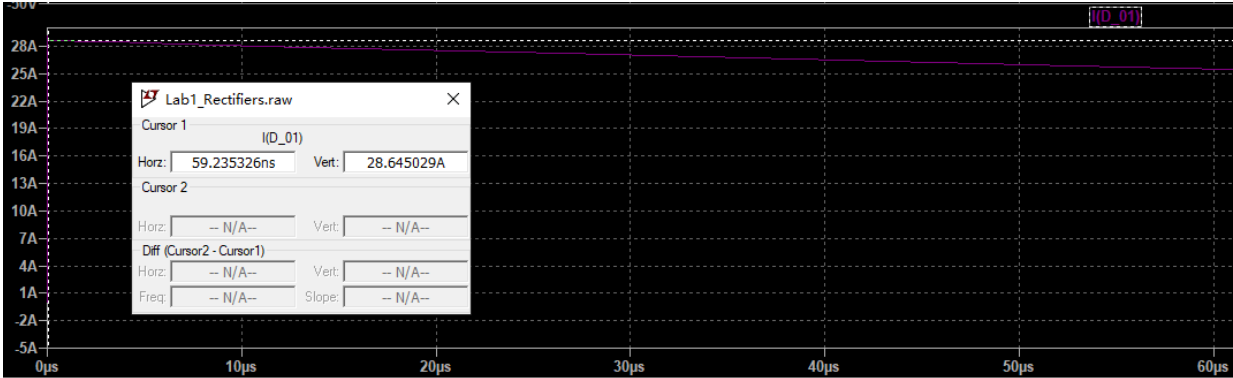


Fig 3.5 –Starting current

$$I_{VDONexp} = 28.65 \tag{A}$$

PRACTICE REPORT №1
«Simple semiconductor device circuits design and simulation»

4. Rectifier evaluation

4.1. Diode simulation parameters evaluation

4.1.1. Datasheet parameters:

Maximum Ratings (@T_A = +25 °C, unless otherwise specified.)

Single phase, half wave, 60Hz, resistive or inductive load.
For capacitance load, derate current by 20%.

Characteristic	Symbol	ES1A	ES1B	ES1C	ES1D	ES1G	Unit
Peak Repetitive Reverse Voltage	V _{RRM}	50	100	150	200	400	V
Working Peak Reverse Voltage	V _{RWM}						
DC Blocking Voltage (Note 6)	V _R						
RMS Reverse Voltage	V _{R(RMS)}	35	70	105	140	280	V
Average Rectified Output Current @ T _T = +110°C	I _O	1.0					A
Non-Repetitive Peak Forward Surge Current 8.3ms	I _{FSM}	30					A
Single Half Sine-Wave Superimposed on Rated Load							

a)

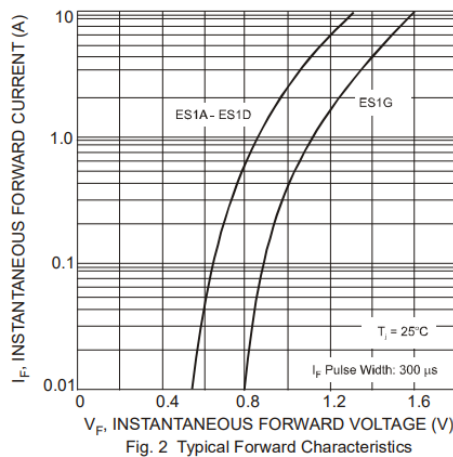


Fig.4.1 – Diode parameters for 25°C

- Maximum average rectified current

$$I_{fwd_AVG} = 1.0 \quad (A)$$

- Maximum peak reverse voltage

$$V_{reverse_imp} = 100 \quad (V)$$

- Maximum peak surge current (as known as Maximum forward surge current or Non-repetitive peak surge current)

$$I_{FSM} = 30 \quad (A)$$

- Maximum repetitive peak surge current

$$I_{fwd_imp} = 10 \quad (A)$$

4.1.2. Diode forward bias voltage

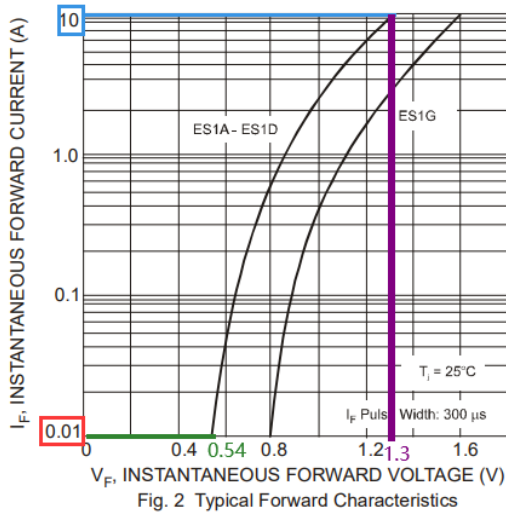


Fig.4.2 – Diode parameters for 25°C

$$V_{fwd_max}(I_{fwd_imp}) = 1.3 \quad (V)$$

4.1.3. Diode threshold voltage:

$$v_{ON} = 0.54 \quad (V)$$

4.1.4. Diode active resistance:

$$r_{VD} = \frac{V_{fwd_max} - v_{ON}}{I_{fwd_imp} - I_{fwd}(v_{ON})} = 0.0761 \quad (\Omega)$$

4.2. Diode rectifier without filter (Part 4.3 is optional for LAB 1 report. It is considered as Practice 1 Task)

4.2.1. Average load voltage

$$V_{R_{LAVG}} = \begin{cases} \frac{V_S}{\pi}, & \text{for HWR schemes} \\ \frac{2 \cdot V_S}{\pi}, & \text{for FBR or CTR schemes} \end{cases} = 31.831 \quad (V)$$

4.2.2. RMS load voltage:

$$V_{R_{LRMS}} = \begin{cases} \frac{V_S}{2}, & \text{for HWR schemes} \\ \frac{V_S}{\sqrt{2}}, & \text{for FBR or CTR schemes} \end{cases} = 35.3553 \quad (V)$$

4.2.3. Max peak diode reverse voltage:

$$V_{VD_{max}} = V_S = 50 \quad (V)$$

4.2.4. Average load current:

$$I_{L_{AVG}} = \frac{V_{R_{L_{AVG}}}}{R_L} = \begin{cases} \frac{V_S}{\pi R_L}, & \text{for HWR schemes} \\ \frac{2 \cdot V_S}{\pi R_L}, & \text{for FBR or CTR schemes} \end{cases} = 0.1768 \quad (\text{A})$$

4.2.5. RMS load current:

$$I_{L_{RMS}} = \frac{V_{R_{L_{RMS}}}}{R_L} = \begin{cases} \frac{V_S}{2 R_L}, & \text{for HWR schemes} \\ \frac{V_S}{\sqrt{2} R_L}, & \text{for FBR or CTR schemes} \end{cases} = 0.1964 \quad (\text{A})$$

4.2.6. Average diode rectified output current:

$$I_{VD} = \begin{cases} I_{L_{AVG}}, & \text{for HWR schemes} \\ \frac{I_{L_{AVG}}}{2}, & \text{for FBR or CTR schemes} \end{cases} = 0.0884 \quad (\text{A})$$

4.2.7. Peak repetitive forward output current:

$$I_{VD_{max}} = \begin{cases} \frac{V_S}{R_L}, & \text{for HWR schemes} \\ \frac{V_S}{2 R_L}, & \text{for FBR or CTR schemes} \end{cases} = 0.1389 \quad (\text{A})$$

4.2.8. Voltage ripple evaluated from desired K_p :

$$\Delta U_{R_L} = 2 \cdot K_p \cdot U_{R_{L_{AVG}}} = 30.7758 \quad (\text{V})$$

4.2.9. Voltage ripple evaluated:

$$K_p = \sqrt{\left(\frac{V_{R_{L_{RMS}}}}{V_{R_{L_{AVG}}}}\right)^2 - 1} = 0.4834 \quad (\text{V})$$

4.2.10. Voltage ripple evaluated for the rectifier scheme:

$$\Delta V_{R_L} = 2 \cdot K_p \cdot V_{R_{L_{AVG}}} = 30.5 \quad (\text{V})$$

Conclusion: to provide required K_p (ΔV_{R_L}) additional C- filter is required

4.3. Diode rectifier with filter (Part 4.3 is optional for LAB 1 report. It is considered as Practice 1 Task)

4.3.1. Source output resistance (overcurrent protection):

$$r_{on} = r_{V_S} = \frac{V_S}{I_{FSM}} = 1.6667 \quad (\Omega)$$

4.3.2. Input rectifier resistance:

$$r_{IN} = \begin{cases} r_{vd} + r_{V_S}, & \text{for HWR or CTR schemes} \\ 2 \cdot r_{vd} + r_{V_S}, & \text{for FBR schemes} \end{cases} = 1.7427 \quad (\Omega)$$

4.3.3. Starting (Non-repetitive) maximum peak surge diode current in rectifier scheme

$$I_{VD_{ON}} = \frac{V_S}{r_{IN}} = 28.6904$$

Maximum Ratings (@T_A = +25 °C, unless otherwise specified.)

Single phase, half wave, 60Hz, resistive or inductive load.
For capacitance load, derate current by 20%.

Characteristic	Symbol	ES1A	ES1B	ES1C	ES1D	ES1G	Unit
Peak Repetitive Reverse Voltage	V _{RRM}						
Working Peak Reverse Voltage	V _{RWM}	50	100	150	200	400	V
DC Blocking Voltage (Note 6)	V _R						
RMS Reverse Voltage	V _{R(RMS)}	35	70	105	140	280	V
Average Rectified Output Current @ T _T = +110°C	I _O	1.0					A
Non-Repetitive Peak Forward Surge Current 8.3ms	I _{FSM}	30					A
Single Half Sine-Wave Superimposed on Rated Load							

At this state, if $I_{VD_{ON}} > I_{FSM}$ it is necessary to increase $r_{V_S} = \frac{V_S}{I_{VD_{ON}}}$ and repeat evaluations 4.3.1-4.3.3.

4.3.4. Diode opening state angle:

$$\theta = \begin{cases} 2 \cdot \sqrt[3]{3 \cdot \pi \cdot \frac{r_{IN}}{R_L}}, & \text{for HWR schemes} \\ 2 \cdot \sqrt[3]{\frac{3}{2} \cdot \pi \cdot \frac{r_{IN}}{R_L}}, & \text{for FBR or CTR schemes} \end{cases} = 0.7147 \quad (\text{rad})$$

4.3.5. Average load voltage

$$V_{R_{L_{AVG}}} = V_S \cdot \cos\left(\frac{\theta}{2}\right) = 46.8417 \quad (\text{V})$$

4.3.6. Average load current:

$$I_{L_{AVG}} = \frac{V_{R_{L_{AVG}}}}{R_L} = \begin{cases} \frac{1}{\pi \cdot r_{IN}} (V_S \cdot \sin\left(\frac{\theta}{2}\right) - V_{R_{L_{AVG}}} \cdot \frac{\theta}{2}), & \text{for HWR schemes} \\ \frac{2}{\pi \cdot r_{IN}} (V_S \cdot \sin\left(\frac{\theta}{2}\right) - V_{R_{L_{AVG}}} \cdot \frac{\theta}{2}), & \text{for FBR or CTR schemes} \end{cases} = 0.2742 \quad (\text{A})$$

4.3.7. Average diode current:

$$I_{VD} = \begin{cases} \frac{V_S}{R_L} \cdot \cos\left(\frac{\theta}{2}\right) = \frac{V_S}{R_L} \cdot \cos\left(\sqrt[3]{3 \cdot \pi \cdot \frac{r_{IN}}{R_L}}\right), & \text{for HWR schemes} \\ \frac{V_S}{2 \cdot R_L} \cdot \cos\left(\frac{\theta}{2}\right) = \frac{V_S}{2 \cdot R_L} \cdot \cos\left(\sqrt[3]{\frac{3}{2} \cdot \pi \cdot \frac{r_{IN}}{R_L}}\right), & \text{for FBR or CTR schemes} \end{cases} =$$

0.1301 (A)

Compare with:

Maximum Ratings (@T_A = +25 °C, unless otherwise specified.)

Single phase, half wave, 60Hz, resistive or inductive load.
For capacitance load, derate current by 20%.

Characteristic	Symbol	ES1A	ES1B	ES1C	ES1D	ES1G	Unit
Peak Repetitive Reverse Voltage	V _{RRM}	50	100	150	200	400	V
Working Peak Reverse Voltage	V _{RWM}						
DC Blocking Voltage (Note 6)	V _R						
RMS Reverse Voltage	V _{R(RMS)}	35	70	105	140	280	V
Average Rectified Output Current @ T _T = +110°C	I _O	1.0					A
Non-Repetitive Peak Forward Surge Current 8.3ms	I _{FSM}	30					A
Single Half Sine-Wave Superimposed on Rated Load							

4.3.8. Maximum repetitive rectifier scheme diode current:

$$I_{VDmax} = \frac{V_S - V_{RLAVG}}{r_{IN}} = \begin{cases} \frac{V_S \left(1 - \cos\left(\sqrt[3]{3 \cdot \pi \cdot \frac{r_{vd} + r_{VS}}{R_L}}\right)\right)}{r_{vd} + r_{VS}}, & \text{for HWR schemes} \\ \frac{V_S \left(1 - \cos\left(\sqrt[3]{\frac{3}{2} \cdot \pi \cdot \frac{r_{vd} + r_{VS}}{R_L}}\right)\right)}{r_{vd} + r_{VS}}, & \text{for CTR schemes} \\ \frac{V_S \left(1 - \cos\left(\sqrt[3]{\frac{3}{2} \cdot \pi \cdot \frac{2 \cdot r_{vd} + r_{VS}}{R_L}}\right)\right)}{2 \cdot r_{vd} + r_{VS}}, & \text{for FBR schemes} \end{cases} = 1.8122$$

(A)

Electrical Characteristics (@T_A = +25 °C, unless otherwise specified.)

Characteristic	Symbol	ES1A	ES1B	ES1C	ES1D	ES1G	Unit
Minimum Reverse Breakdown Voltage (Note 6)	V _{(BR)R}	50	100	150	200	400	V
Maximum Forward Voltage Drop	V _{FM}		0.90			1.25	V
			0.92				
Peak Reverse Current at Rated DC Blocking Voltage (Note 6)	I _{RM}			5.0	200		μA
Maximum Reverse Recovery Time (Note 7)	t _{RR}			25			ns
Typical Total Capacitance (Note 8)	C _T			20			pF

Notes: 5. Unit mounted on PC board with 5.0 mm² (0.013 mm thick) copper pad as heat sink.
6. Short duration pulse test used to minimize self-heating effect.
7. Measured with I_F = 0.5A, I_R = 1.0A, I_{RR} = 0.25A. See figure 5.
8. Measured at 1.0MHz and applied reverse voltage of 4.0V DC.

Compare with capacitor rated current.

4.3.9. Peak repetitive reverse voltage:

$$V_{VDmax} = \begin{cases} V_S + V_{RLAVG}, & \text{for HWR schemes or CTR schemes} \\ \frac{V_S + V_{RLAVG}}{2}, & \text{for FBR} \end{cases} = 96.8417$$

Compare with:

Maximum Ratings (@T_A = +25 °C, unless otherwise specified.)

Single phase, half wave, 60Hz, resistive or inductive load.
For capacitance load, derate current by 20%.

Characteristic	Symbol	ES1A	ES1B	ES1C	ES1D	ES1G	Unit
Peak Repetitive Reverse Voltage	V _{RRM}	50	100	150	200	400	V
Working Peak Reverse Voltage	V _{RWM}						
DC Blocking Voltage (Note 6)	V _R						
RMS Reverse Voltage	V _{R(RMS)}	35	70	105	140	280	V
Average Rectified Output Current @ T _T = +110°C	I _O	1.0					A
Non-Repetitive Peak Forward Surge Current 8.3ms	I _{FSM}	30					A
Single Half Sine-Wave Superimposed on Rated Load							

4.3.10. Voltage ripple evaluated for the K_p from given variant data:

	Rectifier scheme	Source voltage amplitude, [V]	Load resistance, [Ω]	Desired DC voltage ripple factor	Source voltage frequency, [Hz]
Variant #	wave rectifier, CTR-	V_s	R_L	K_p	f
72	CTR	120	180	0.035	100

$$\Delta V_{R_L} = \begin{cases} \frac{I_{L_{AVG}}}{2\pi f \cdot C} (2\pi - \theta) = K_p V_{R_{L_{AVG}}} 2\sqrt{3}, \text{ for HWR schemes} \\ \frac{I_{L_{AVG}}}{2\pi f \cdot C} (\pi - \theta) = K_p V_{R_{L_{AVG}}} 2\sqrt{3}, \text{ for FBR or CTR schemes} \end{cases} = 3.2789 \text{ (V)}$$

4.4. Capacitor evaluation

4.4.1. Capacitance evaluation:

$$C = \begin{cases} \frac{I_{L_{AVG}}}{2\pi f \cdot \Delta V_{R_L}} (2\pi - \theta), \text{ for HWR schemes} \\ \frac{I_{L_{AVG}}}{2\pi f \cdot \Delta V_{R_L}} (\pi - \theta), \text{ for FBR or CTR schemes} \end{cases} = 0.0003 \text{ (F)}$$

Pay attention to maximum tolerance rating: for the example in this case 20%

$$C_{real} = \frac{C}{0.8} = 1.25C = 0.000375 \text{ (F)}$$

$$(100\% - 20\%)C_{real} \geq C = 0.0003 \text{ (F)}$$

4.4.2. After the nominal value is chosen:

$$C_{real} = 0.000375 \text{ (F)}$$

$$0.8C_{real} = 0.0003 \text{ (F)}$$

$$1.2C_{real} = 0.00045 \text{ (F)}$$

4.5. Expected parameters of the developed rectifier

4.5.1. Voltage ripple:

$$\Delta V_{R_L} = \begin{cases} \frac{I_{L_{AVG}}}{2\pi f \cdot 0.8 C_{real}} (2\pi - \theta), \text{ for HWR schemes} \\ \frac{I_{L_{AVG}}}{2\pi f \cdot 0.8 C_{real}} (\pi - \theta), \text{ for FBR or CTR schemes} \end{cases} = 3.2789 \quad (V)$$

$$\Delta V_{R_L} = \begin{cases} \frac{I_{L_{AVG}}}{2\pi f \cdot C_{real}} (2\pi - \theta), \text{ for HWR schemes} \\ \frac{I_{L_{AVG}}}{2\pi f \cdot C_{real}} (\pi - \theta), \text{ for FBR or CTR schemes} \end{cases} = 2.6231 \quad (V)$$

$$\Delta V_{R_L} = \begin{cases} \frac{I_{L_{AVG}}}{2\pi f \cdot 1.2 C_{real}} (2\pi - \theta), \text{ for HWR schemes} \\ \frac{I_{L_{AVG}}}{2\pi f \cdot 1.2 C_{real}} (\pi - \theta), \text{ for FBR or CTR schemes} \end{cases} = 2.1859 \quad (V)$$

4.5.2. Voltage ripple factor:

$$K_p \approx \frac{\frac{\Delta V_{R_L}}{2\sqrt{3}}}{V_{R_{L_{AVG}}}} = 0.021$$

4.6. Comparing simulation and estimation results

4.6.1. Average load voltage tolerance

$$\Delta V_{R_{L_{AVG}}} = \frac{|V_{R_{L_{AVG}}^{exp}} - V_{R_{L_{AVG}}}|}{V_{R_{L_{AVG}}}} = 1.97 \quad (\%)$$

4.6.2. Ripple factor tolerance:

$$\Delta K_P = \frac{|K_{P^{exp}} - K_P|}{K_P} \cdot 100\% = 40 \quad (\%)$$

4.6.3. Voltage ripple tolerance:

$$\Delta \Delta V_{R_L} = 0.27 \quad (\%)$$

4.6.4. Diode opening state angle tolerance:

$$\Delta \theta = 5.97 \quad (\%)$$

4.6.5. Maximum repetitive rectifier scheme diode current tolerance:

$$\Delta I_{VD_{max}} = 1.23 \quad (\%)$$

4.6.6. Average rectifier scheme diode current tolerance:

$$\Delta I_{VD} = 0.077 \quad (\%)$$

4.6.7. Starting (Non-repetitive) maximum peak surge diode current in rectifier scheme tolerance:

$$\Delta I_{VD_{ON}} = 13.9 \quad (\%)$$

Table 4.1 Tolerance report

Parameter	Desired/evaluated value	Simulation result	Tolerance %
$V_{RL_{AVG}}$ (V)	46.8417	45.918	1.97
K_p	0.035	0.021	40
ΔV_{RL} (V)	3.2789	3.27	0.27
θ (rad)	0.7147	0.672	5.97
$I_{VD_{max}}$ (A)	1.8122	1.79	1.23
I_{VD} (A)	0.1301	0.13	0.077

Conclusions

Conclusions should contain:

1) Diode check results:

- Is breakdown voltage check passed? /Is voltage source changed because of overvoltage?

Yes/Yes

- Is starting current check passed? /Is additional resistance r_{vs} added to prevent overcurrent in diode/capacitor?

Yes/Yes

2) Capacitor information: nominal value, tolerance, allowed current

.MODEL D_VAR_0 D (IS=123n RS=42.0m BV=100 IBV=5.00u+ CJO=18.5p
M=0.333 N=2.12 TT=28.8n)


3) Provided ripple factor value

0.035

Appendix A.

ES1B

Maximum Ratings (@T _A = +25 °C, unless otherwise specified.)							
Single phase, half wave, 60Hz, resistive or inductive load. For capacitance load, derate current by 20%.							
Characteristic	Symbol	ES1A	ES1B	ES1C	ES1D	ES1G	Unit
Peak Repetitive Reverse Voltage	V _{RRM}	50	100	150	200	400	V
Working Peak Reverse Voltage	V _{RWM}						
DC Blocking Voltage (Note 6)	V _R						
RMS Reverse Voltage	V _{R(RMS)}	35	70	105	140	280	V
Average Rectified Output Current @ T _T = +110°C	I _O	1.0					A
Non-Repetitive Peak Forward Surge Current 8.3ms	I _{FSM}	30					A
Single Half Sine-Wave Superimposed on Rated Load							

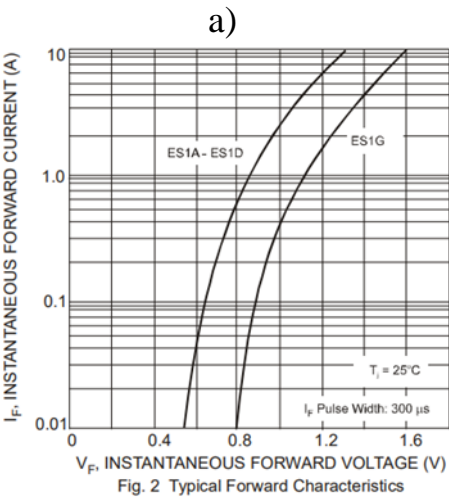

b)

Fig.1. Diode parameters for 25°C

Appendix B. VariantNo72.lib listing