



**ITMO UNIVERSITY**

Research on series and parallel resonant  
circuits

---

Madina Tsvetkova, Konstantin Gorshkov, Sergey Lovlin

Faculty of Control Systems and Industrial Robotics, ITMO University, Saint Petersburg

# Contents

- Objectives
- Program of work
- Guidance
- Content of the report
- Special tasks



# Objectives


to investigate linear alternating current (AC) circuits properties, and its special modes of operation, such as series resonance and parallel resonance.

# Program of work

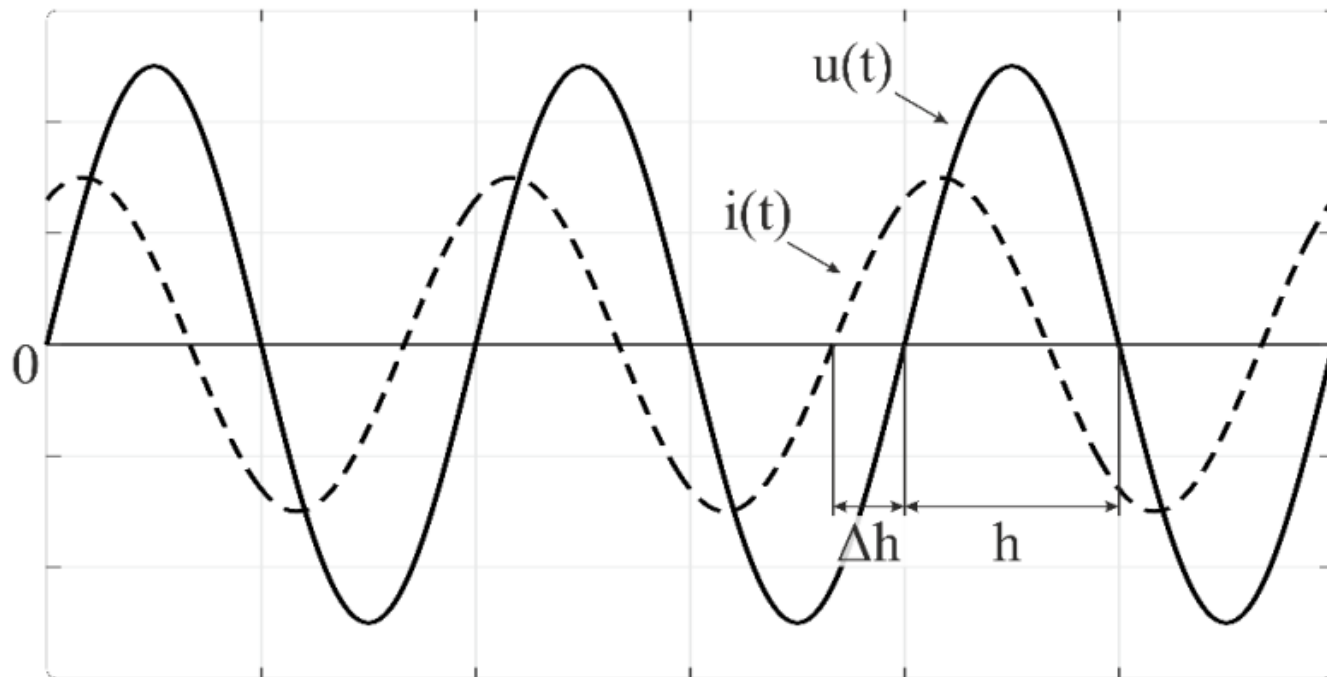
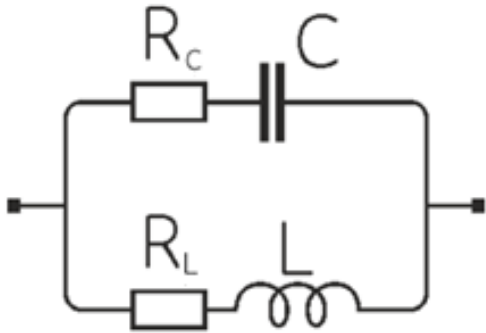
1. To study and to analyze the frequency characteristics of the electrical circuit with the serial connection of resistive, inductive and capacitive elements.
2. To study and to analyze the frequency characteristics of electric circuit with the parallel connection of branches with inductive and capacitive elements.

# Phase shift

Measure phase shift  $\varphi = 180^\circ \cdot \Delta h / h$  as shown in the Figure (h - half of the sine wave period, measured in seconds,  $\Delta h$  - the length in seconds of the segment between moments of time when sine waves of voltage and current change sign from negative to positive. If the current is ahead of the voltage, as shown in the Figure then  $\varphi < 0$ , if it falls behind -  $\varphi > 0$ .



# Resonant circuits

№	Passive two-terminal load	Calculation equations
1		$I = U/Z, R = R_1 + R_L,$ $X = X_L - X_C = \omega \cdot L - 1/(\omega \cdot C)$ $Z = \sqrt{R^2 + X^2}, \varphi = \arctg(X/R)$
2		$I = U \cdot Y, G = G_C + G_L, G_C = R_C / (R_C^2 + X_C^2),$ $G_L = R_L / (R_L^2 + X_L^2), B = B_L - B_C,$ $B_C = X_C / (R_C^2 + X_C^2), B_L = X_L / (R_L^2 + X_L^2)$ $Y = \sqrt{G^2 + B^2}, \varphi = \arctg(B/G)$

# Series resonant circuit

Calculate resonant frequency for specified parameters of elements -

$$f_0 = 1/(2\pi\sqrt{LC}) \text{ [Hz]}.$$

Set the source voltage frequency corresponding to the calculated value of the resonant frequency  $f_0$ .

Measure RMS values of current  $I$ , voltage across the resistor  $U_R$ , voltage across the capacitor  $U_C$ , voltage across the inductor  $U_L$  and the phase shift between voltage and current  $\varphi_0$  in the resonance mode. Add measurements and calculations results to the Table.

Put the calculated  $Q$  and experimental  $Q_e$  quality factor values in the Table ( $Q = \rho/(R_1 + R_L)$ , where  $\rho = \sqrt{L/C}$ ;  $Q_e = U_{C0}/U$ ,  $U_{C0}$  and  $U$  - RMS values of capacitor voltage and source (input) voltage measured in resonance mode).

# Series resonant circuit

f	U = __ [V]; R <sub>1</sub> = __ [Ω]; R <sub>L</sub> = __ [Ω]; L = __ [mH]; C = __ [mkF]; f <sub>0</sub> = __ [Hz]									
	Calculations					Experiment				
	Q = __					Q <sub>e</sub> = __				
	φ °	I A	U <sub>R1</sub>	U <sub>L</sub>	U <sub>C</sub>	φ °	I A	U <sub>R1</sub>	U <sub>L</sub>	U <sub>C</sub>
Hz	°	A	B			°	A	B		
0.1·f <sub>0</sub>										
...										
f <sub>0</sub>										
...										
2·f <sub>0</sub>										

Get the measurements for 20 constraint points in range from 0.1f<sub>0</sub> up to 2f<sub>0</sub> by changing the source frequency and enter the results of experiment and calculations in the Table.



# Parallel resonant circuit

Calculate resonant frequency

$$f'_0 = \frac{1}{2\pi} \sqrt{\frac{(R_c + R_L)^2}{4L^2} - \frac{1}{LC}} \text{ [Hz]}$$

Set the source voltage frequency corresponding to the calculated value of the resonant frequency  $f'_0$ .

Measure RMS values of input current  $I$ , current in the branch with the inductor  $I_1$ , current in the branch with the capacitor  $I_2$  and phase shift angle  $\phi$  between the input voltage and the current in resonance mode. Add the measured and calculated values to the Table

# Parallel resonant circuit

f	U = __ [V]; $R_C$ = __ [ $\Omega$ ]; $R_L$ = __ [ $\Omega$ ]; L = __ [mH]; C = __ [mkF]; $f'_0$ = __ [Hz]							
	Calculations				Experiment			
	$\varphi$	I	$I_1$	$I_2$	$\varphi$	I	$I_1$	$I_2$
Hz	$^\circ$	A			$^\circ$	A		
$0.1 \cdot f'_0$								
...								
$f'_0$								
...								
$2 \cdot f'_0$								

Get the measurements for 20 constraint points in range from  $0.1f'_0$  up to  $2f'_0$  by changing the source frequency and enter the results of experiment and calculations in the Table.

# Special tasks

**Task 2.1.** Find the expression of group delay  $\tau(\omega)$  of series resonant circuit. Use the transfer function  $H(j\omega)=U_{R1}(j\omega)/U_{in}(j\omega)$ .

**Task 2.2.** Find the expression of group delay of parallel resonant circuit. Use the transfer function  $H(j\omega)=U_R(j\omega)/U_{in}(j\omega)$ .

The report must include the solution and group delay plot. You can use the numerical values of parameters from your variant.