

# **ITMO**

## **Laboratory Work 1**

### **Simple semiconductor device circuits design and simulation**

**Nikolay Nikolaev**

([nanikolaev@itmo.ru](mailto:nanikolaev@itmo.ru))

**Nikolai Poliakov**

([polyakov\\_n\\_a@itmo.ru](mailto:polyakov_n_a@itmo.ru))

**Roman Olekhnovich**

([r.o.olekhnovich@mail.ru](mailto:r.o.olekhnovich@mail.ru))




1. LT Spice simulation for electronic device analysis
2. Diode parameters analysis
3. Rectifier scheme simulation
4. Capacitor parameter analysis
5. Overvoltage test
6. Starting current test
7. Uploading report to the

The goal of laboratory work «Simple semiconductor device circuits design and simulation» is to study rectifier scheme on the basis of proposed diode.


Laboratory work task are:

1. Rectifier scheme simulation
2. Diode parameters analysis
3. Capacitor parameter analysis
4. Overvoltage check
5. Starting current check

# pn-junction under external voltage

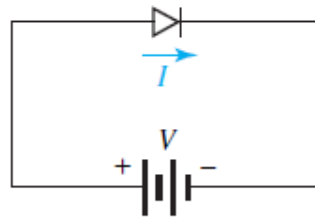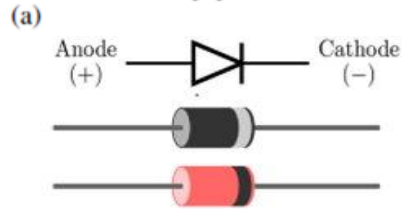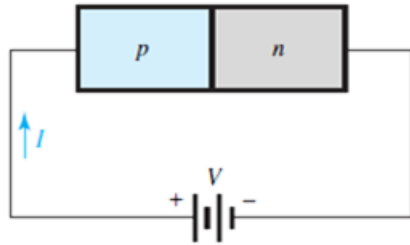

(b)

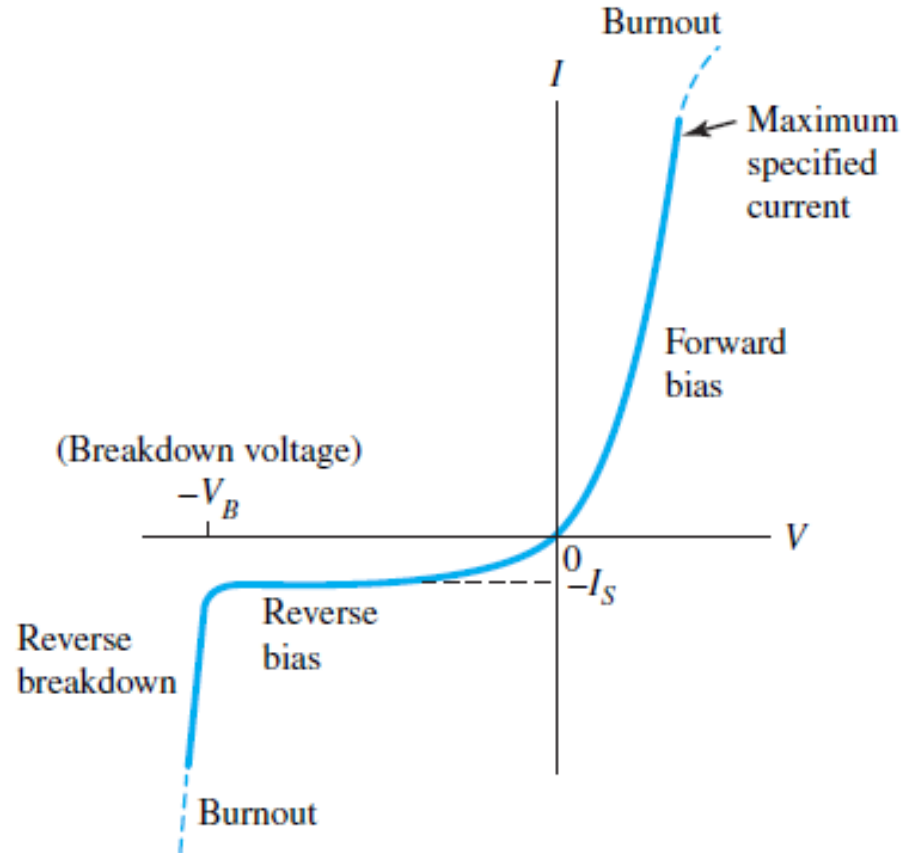







the *Boltzmann diode equation*


$$I = I_S(e^{V/\eta V_T} - 1)$$

$$V_T = \frac{kT}{q}$$

$$\eta = \begin{cases} 1, & \text{for Si} \\ 2, & \text{for Ge} \end{cases}$$

# Forward-biased diode models

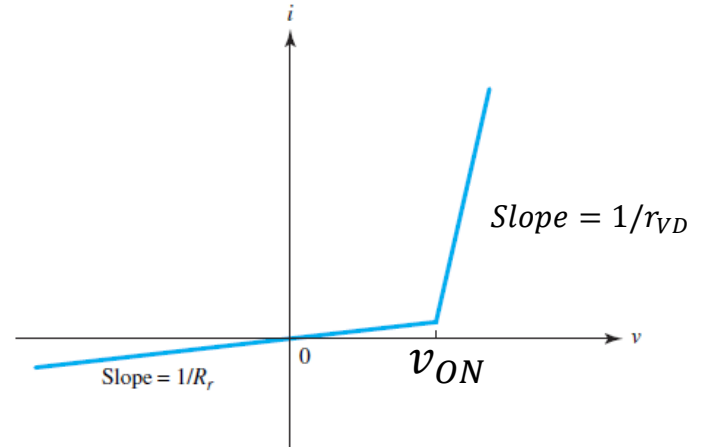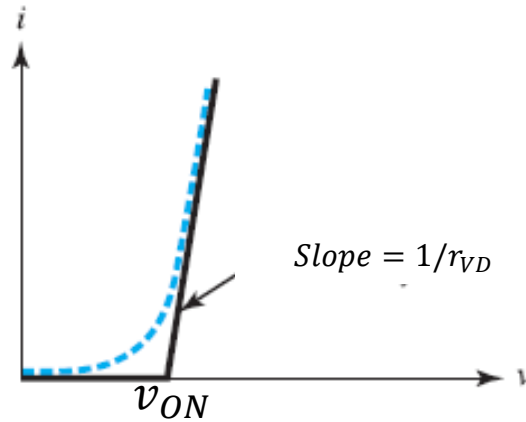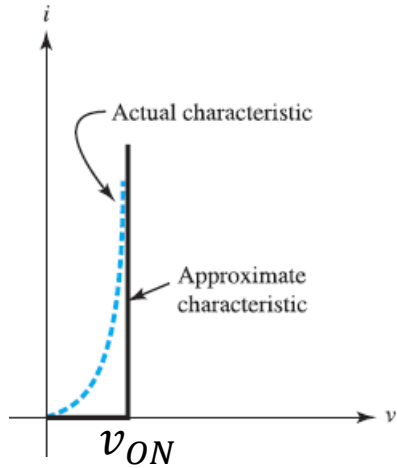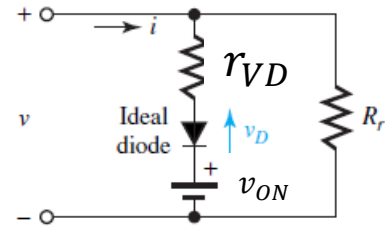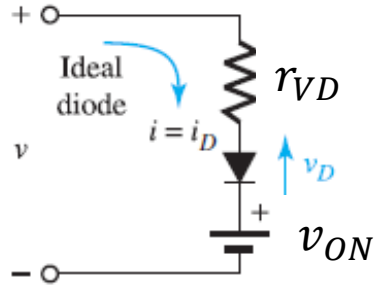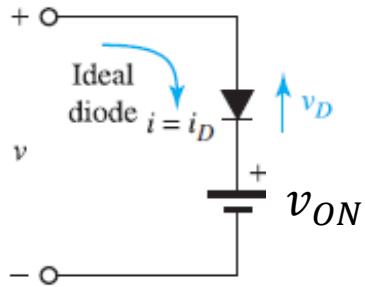

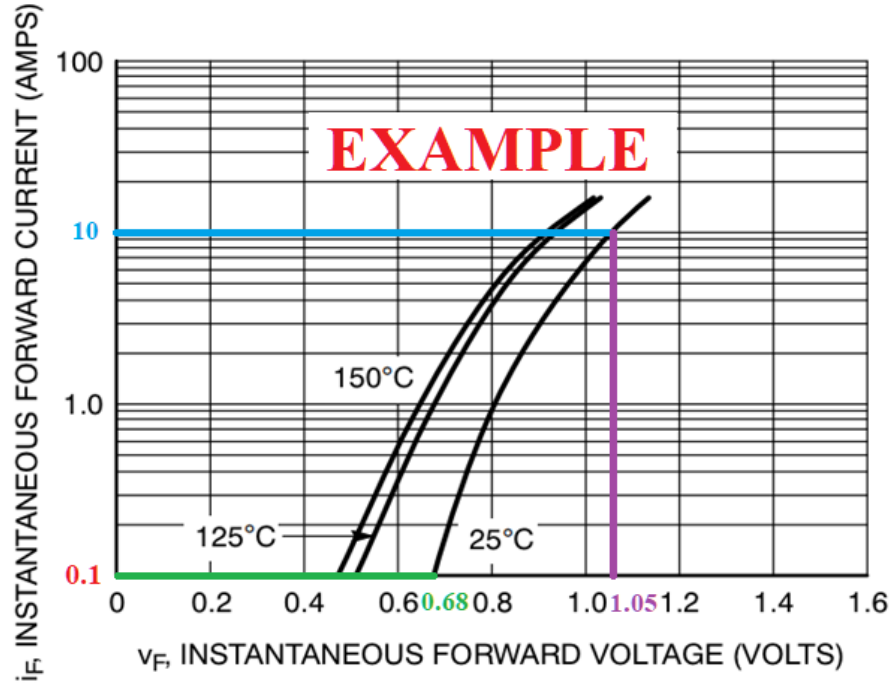

Maximum repetitive peak surge forward current

$$I_{fwd\_imp} = 10 \quad (A)$$

Diode forward bias voltage


$$V_{fwd\_max}(I_{fwd\_imp}) = 1.05 \quad (V)$$

Diode threshold voltage:

$$v_{ON} = 0.68 \quad (V)$$

Diode active resistance:
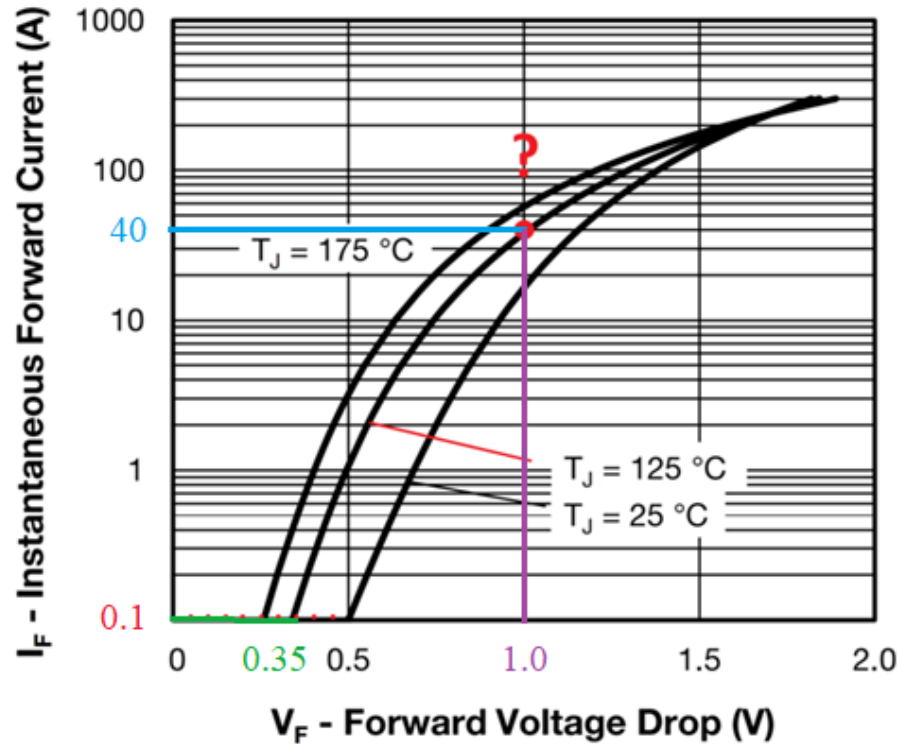
$$r_{VD} = \frac{V_{fwd\_max} - v_{ON}}{I_{fwd\_imp} - I_{fwd}(v_{ON})} = \quad (\Omega)$$



Maximum repetitive peak surge forward current

$$I_{fwd\_imp} = 40 \quad (\text{A})$$

Diode forward bias voltage

$$V_{fwd\_max}(I_{fwd\_imp}) = 1.0 \quad (\text{V})$$

Diode threshold voltage:

$$v_{ON} = 0.35 \quad (\text{V})$$

Diode active resistance:

$$r_{VD} = \frac{V_{fwd\_max} - v_{ON}}{I_{fwd\_imp} - I_{fwd}(v_{ON})} \quad (\Omega)$$

## Diode breakdown


### Reversible:

- *Zener breakdown* (at low voltages)
- *Avalanche breakdown* (at higher voltages)
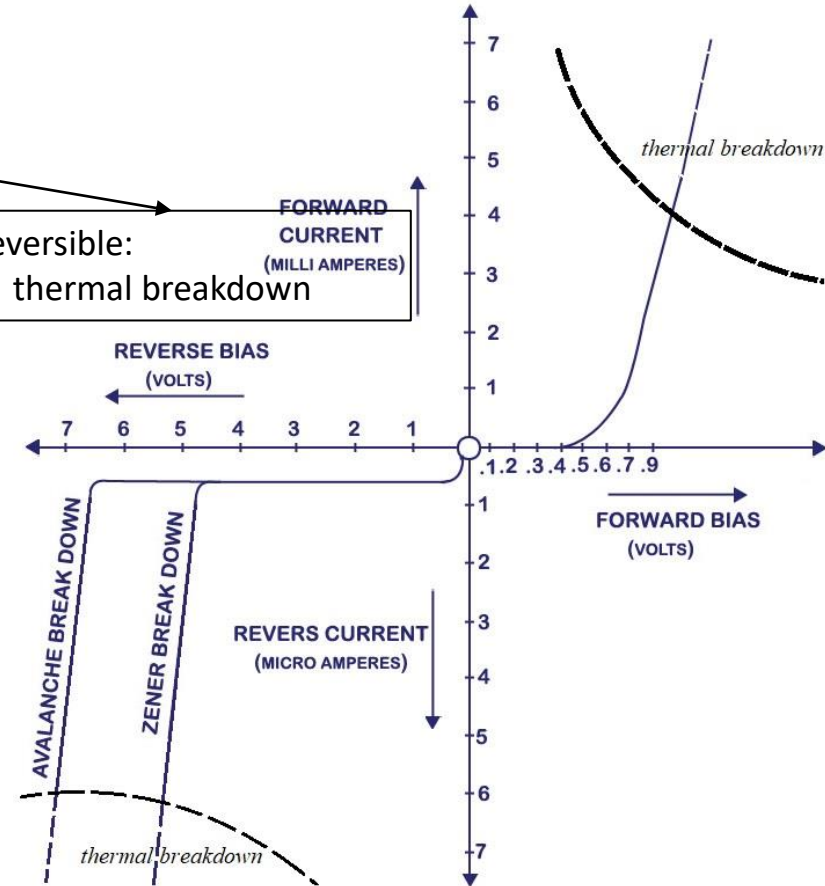
### Irreversible:


- thermal breakdown

Zener and Avalanche breakdown find application in stabilitrons.





# Half-Wave Rectifier (HWR)

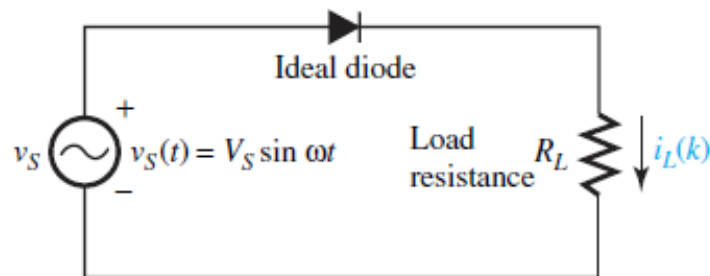

## Load parameters:

$$V_{RLAVG} = \frac{V_s}{\pi} = \frac{\sqrt{2}V_{SRMS}}{\pi} \approx 0.45V_{SRMS}$$

$$V_{RLRMS} = \frac{V_s}{2} = \frac{V_{SRMS}}{\sqrt{2}} \approx 0.707V_{SRMS}$$

Average load current

$$I_{LAVG} = \frac{V_{RLAVG}}{R_L} = \frac{\sqrt{2}V_{SRMS}}{\pi R_L} \approx 0.45 \frac{V_{SRMS}}{R_L}$$

RMS load current through diode

$$I_{LRMS} = \frac{V_s}{2R_L} = \frac{V_{SRMS}}{\sqrt{2}R_L} \approx 0.707 \frac{V_{SRMS}}{R_L}$$

Source voltage  $v_s(t)$

$$v_s(t) = V_s \cdot \sin(f \cdot 2\pi \cdot t) = V_s \cdot \sin(\omega \cdot t)$$

Voltage on the load resistance  $R_L$

$$v_{RL}(t) = \begin{cases} 0, & \text{if } v_s(t) \leq 0 \\ v_s(t), & \text{if } v_s(t) > 0 \end{cases}$$

## Diode parameters:

Average diode current

$$I_{VD AVG} = I_{L AVG} = \frac{\sqrt{2}V_{SRMS}}{\pi R_L} \approx 0.45 \frac{V_{SRMS}}{R_L}$$







MAX diode current

$$I_{VD max} = \frac{V_s}{R_L}$$

MAX diode reverse voltage

$$V_{VD max} = V_s$$
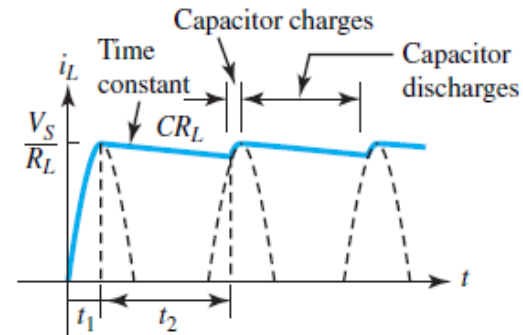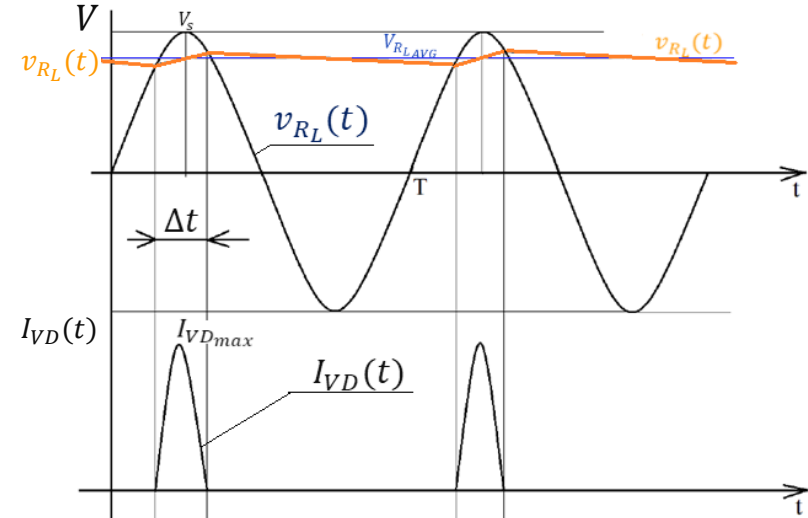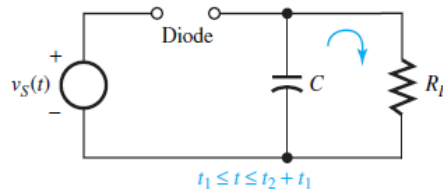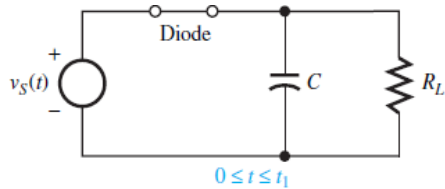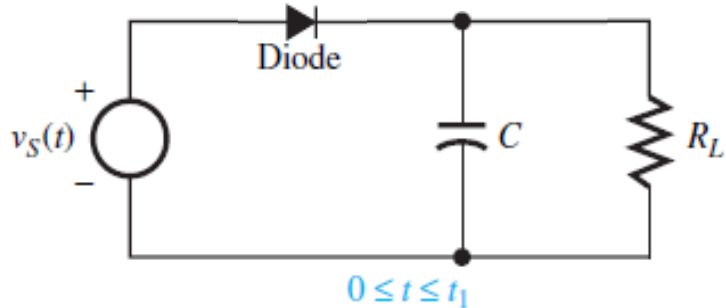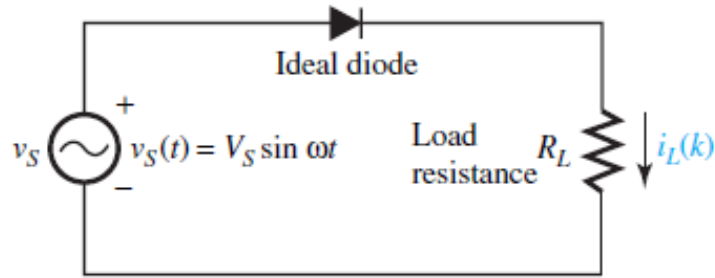
# Half-Wave Rectifier with DC filter capacitor



$$v_{RL}(t) = V_{RLAVG} + v_{RL\sim}(t) \approx V_{RL} = \text{const}$$

Diode voltage:

Average diode current:

$$v_{VD}(t) = v_s(t) - V_{RLAVG}$$

$$I_{LAVG} = I_{VD AVG} = \frac{1}{T} \sqrt{\int_0^T I_{VD}(t) dt}$$

$$I_{LAVG} = \frac{1}{T} \int_{\frac{T}{4} - \frac{\theta}{2\omega}}^{\frac{T}{4} + \frac{\theta}{2\omega}} \frac{1}{r_{IN}} (V_s \cdot \sin(\omega \cdot t) - V_{RLAVG}) dt = \frac{V_{RLAVG}}{R_L}$$

Where

$$r_{IN} = r_{VD} + r_{VS}$$

$r_{VD}$

$r_{VS}$

$$\theta = \omega \cdot \Delta t = \frac{2\pi}{T} \cdot \Delta t$$

$\Delta t$

– input resistance of the rectifier

– diode resistance


– voltage source resistance

– angle of diode open state

– diode open state time interval

$$\frac{V_{RLAVG}}{V_s} = \frac{R_L}{\pi r_{IN}} \left( \sin\left(\frac{\theta}{2}\right) - \frac{V_{RLAVG}}{V_s} \frac{\theta}{2} \right)$$
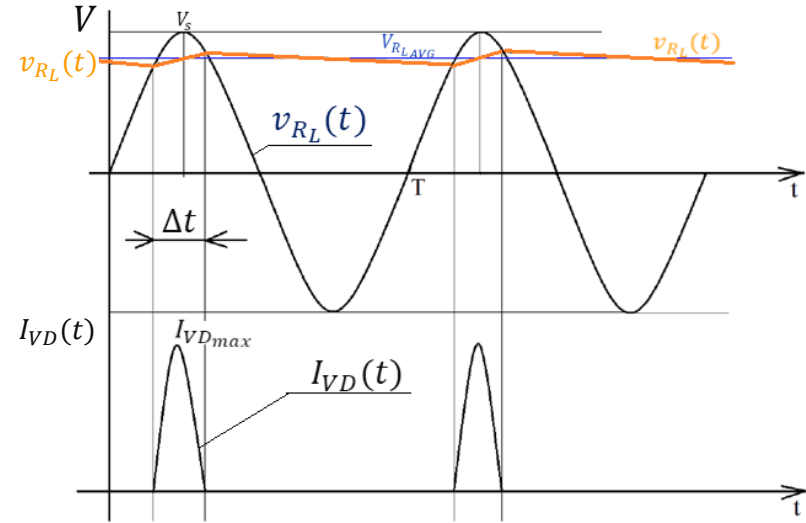
$$V_{VD} \left( \frac{T}{4} \pm \frac{\theta}{2\omega} \right) = V_s \sin\left(\omega \left( \frac{T}{4} \pm \frac{\theta}{2\omega} \right)\right) - V_{RLAVG} = 0 \Rightarrow V_{RLAVG} = V_s \left( \omega \left( \frac{T}{4} \pm \frac{\theta}{2\omega} \right) \right) = V_s \sin\left(\frac{\pi}{2} \pm \frac{\theta}{2}\right)$$



Average diode current:

$$I_{LAVG} = \frac{1}{T} \int_{\frac{T}{4} - \frac{\theta}{2\omega}}^{\frac{T}{4} + \frac{\theta}{2\omega}} \frac{1}{r_{IN}} (V_S \cdot \sin(\omega \cdot t) - V_{RLAVG}) dt = \frac{V_{RLAVG}}{R_L}$$

Where

$$r_{IN} = r_{VD} + r_{VS}$$

$r_{VD}$

$r_{VS}$


$$\theta = \omega \cdot \Delta t = \frac{2\pi}{T} \cdot \Delta t$$

$\Delta t$  — diode open state time interval

$$\frac{V_{RLAVG}}{V_S} = \frac{R_L}{\pi r_{IN}} \left( \sin\left(\frac{\theta}{2}\right) - \frac{V_{RLAVG}}{V_S} \frac{\theta}{2} \right)$$

$$V_{VD} \left( \frac{T}{4} \pm \frac{\theta}{2\omega} \right) = V_S \sin\left(\omega \left( \frac{T}{4} \pm \frac{\theta}{2\omega} \right)\right) - V_{RLAVG} = 0 \Rightarrow V_{RLAVG} = V_S \left( \omega \left( \frac{T}{4} \pm \frac{\theta}{2\omega} \right) \right) = V_S \sin\left(\frac{\pi}{2} \pm \frac{\theta}{2}\right)$$
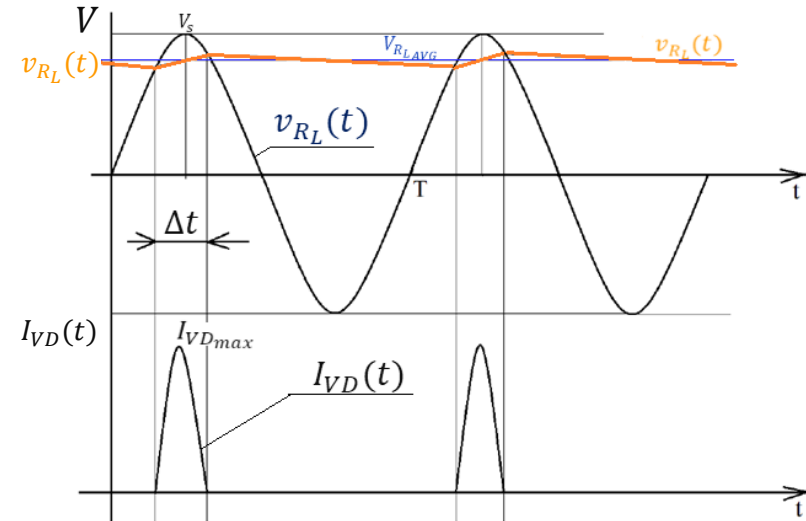
$$\frac{V_{RLAVG}}{V_S} = \cos\left(\frac{\theta}{2}\right) \Rightarrow \cos\left(\frac{\theta}{2}\right) = \frac{R_L}{\pi r_{IN}} \left( \sin\left(\frac{\theta}{2}\right) - \cos\left(\frac{\theta}{2}\right) \cdot \frac{\theta}{2} \right) \Rightarrow \frac{r_{IN}}{R_L} = \frac{1}{\pi} \left( \tan\left(\frac{\theta}{2}\right) - \frac{\theta}{2} \right)$$



From  $\frac{r_{IN}}{R_L} = \frac{1}{\pi} \left( \tan\left(\frac{\theta}{2}\right) - \frac{\theta}{2} \right)$

angle of diode open state  $\theta$  can be evaluated:

$$\tan\left(\frac{\theta}{2}\right) \approx \frac{\theta}{2} + \frac{1}{3}\left(\frac{\theta}{2}\right)^3 \Rightarrow \theta = 2 \cdot \sqrt[3]{3\pi \frac{r_{IN}}{R_L}}$$


Average load voltage:  $V_{R_{L_{AVG}}} = V_S \cos\left(\frac{\theta}{2}\right)$

Average load (diode) current:  $I_{VD} = \frac{V_S}{R_L} \cos\left(\frac{\theta}{2}\right)$

Peak (repetitive) diode current:  $I_{VD_{max}} = \frac{V_S - V_{R_{L_{AVG}}}}{r_{IN}}$

Peak (turn on) diode current:  $I_{VD_{ON}} = \frac{V_S}{r_{IN}}$

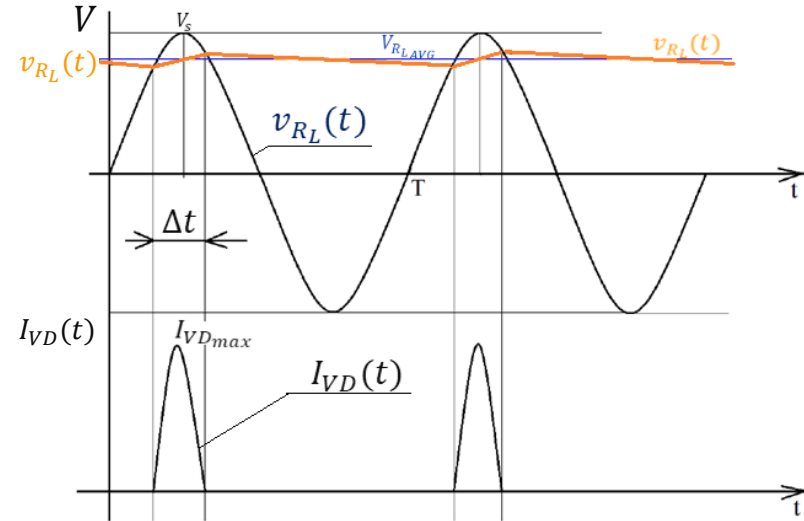Diode reverse voltage:  $V_{VD_{max}} = V_S + V_{R_{L_{AVG}}} \approx 2 \cdot V_S$





From equation of capacitor charge on the interval of  $\tau_1 < t < \tau_2 = T - \frac{\theta}{\omega}$


$$\Delta Q = C \cdot \Delta V_{RL} = I_{L_{AVG}} \left( T - \frac{\theta}{\omega} \right) \quad (C)$$

Power filter capacitor evaluation to provide required ripple factor
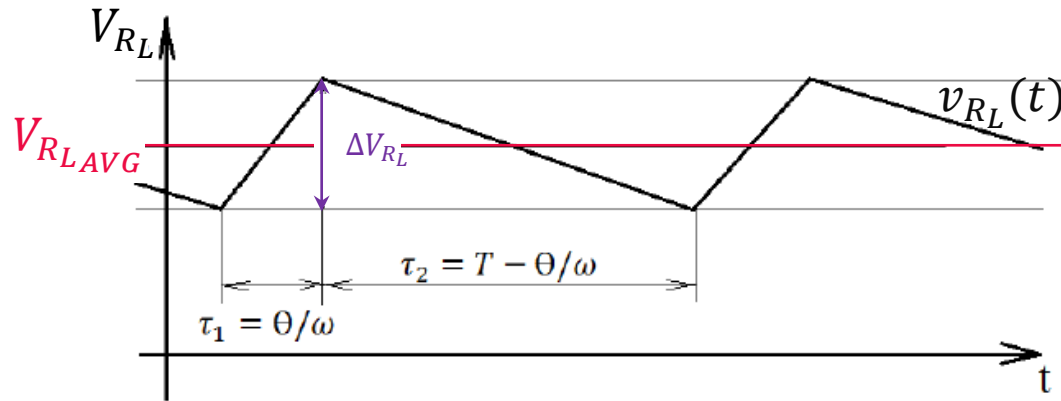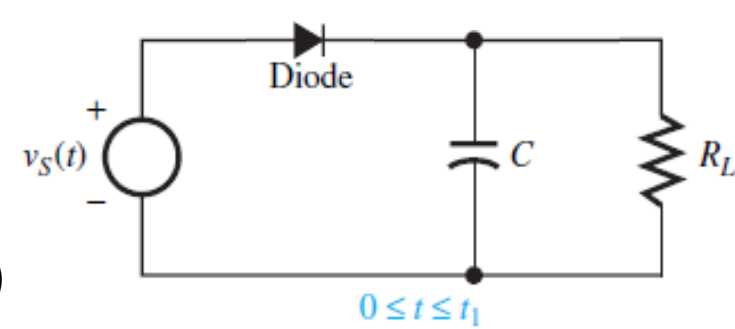
$$C = \frac{I_{L_{AVG}}}{2\pi f \cdot \Delta V_{RL}} (2\pi - \theta) = \frac{I_{L_{AVG}}}{\omega \cdot \Delta V_{RL}} (2\pi - \theta) \quad (F)$$



# Center-Tap Full Wave Rectifier

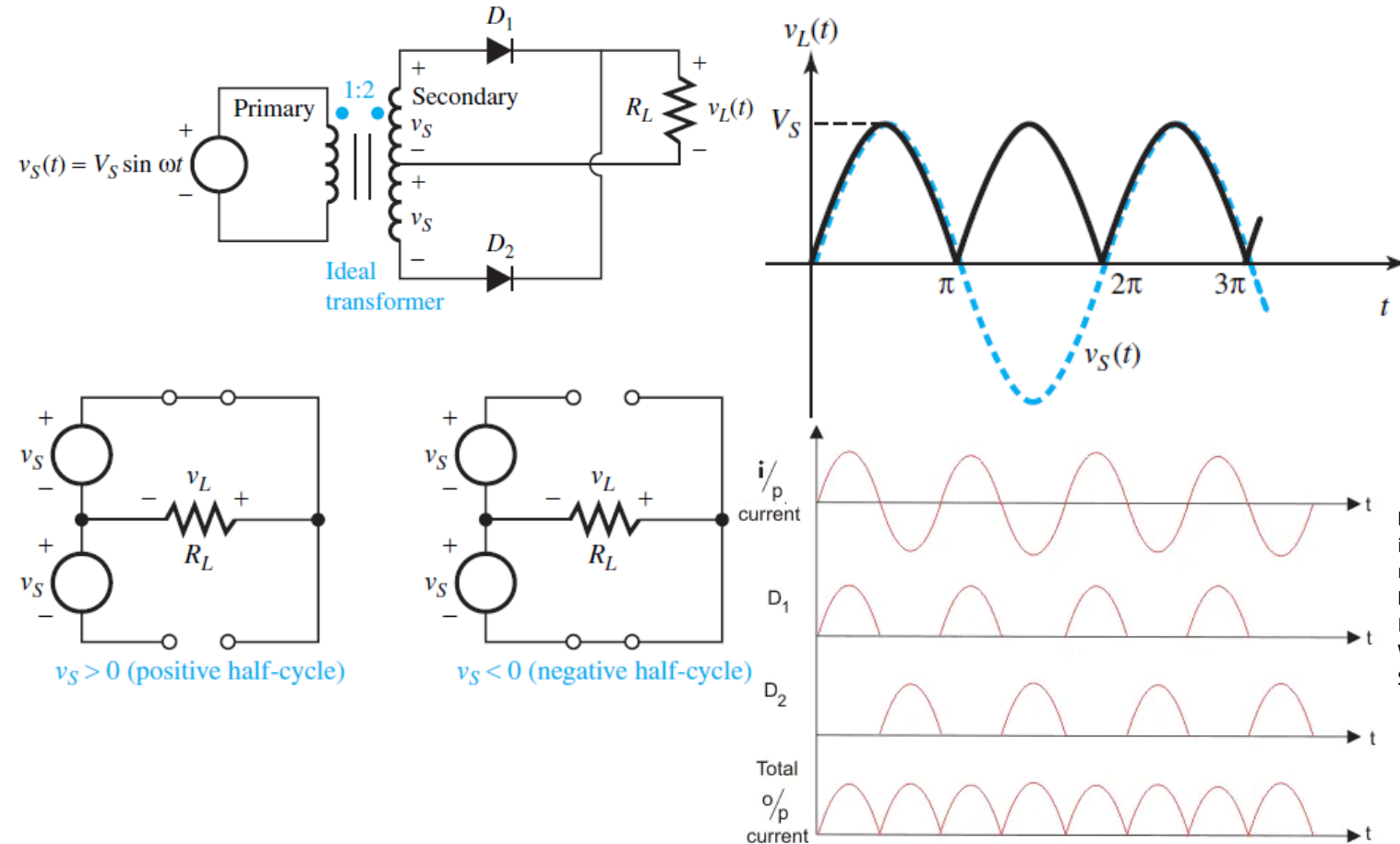

Vladimir Mitkevich

**BORN:** 22/06/1872 (03. 08. 1872)




in MINSK, (Russian Empire,  
now it's the capital of BELARUS)

**Death:** 01/06/1951


Moscow, Soviet Russia

**Worked** in Peter the Great  
St.Petersburg Polytechnic University

# Full Wave Bridge Rectifier

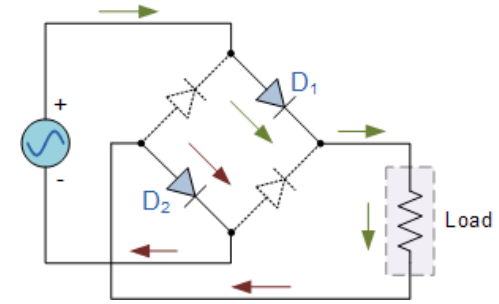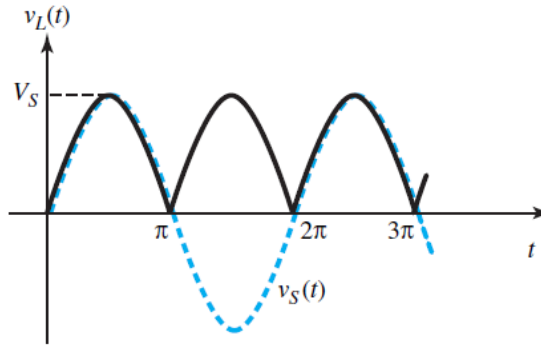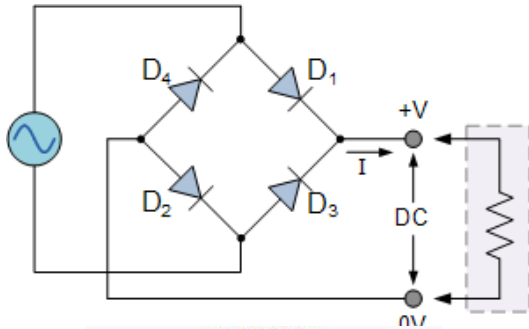

The Positive Half-cycle

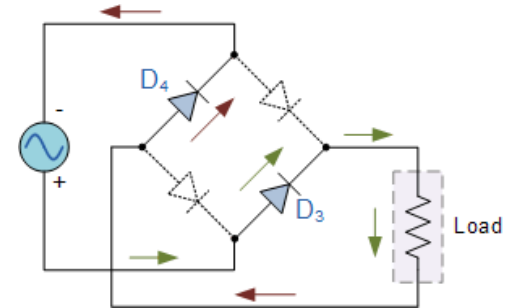

The Negative Half-cycle

Leo Graetz



Leo Graetz, painted by Franz von Stuck (1906)


Born 26 September 1856

Breslau, Prussia

Died 12 November 1941 (aged 85)

Munich, Nazi Germany

Known for Graetz number, Diode bridge

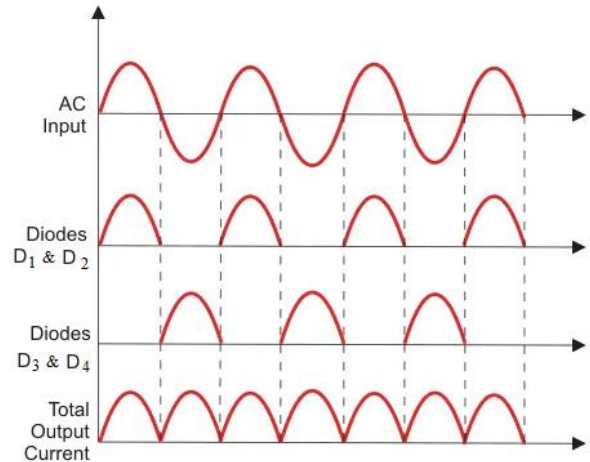



- **Average load voltage:** 
$$V_{RLAVG} = \begin{cases} \frac{V_S}{\pi}, \\ \frac{2 \cdot V_S}{\pi}, \end{cases}$$
 for HWR schemes (V)  
for FBR or CTR schemes
- **RMS load voltage:** 
$$V_{RLRMS} = \begin{cases} \frac{V_S}{2}, \\ \frac{V_S}{\sqrt{2}}, \end{cases}$$
 for HWR schemes (V)  
for FBR or CTR schemes
- **Max peak diode reverse voltage:** 
$$V_{VDmax} = V_S$$
 (V)
- **Average load current:** 
$$I_{LAVG} = \frac{V_{RLAVG}}{R_L} = \begin{cases} \frac{V_S}{\pi R_L}, \\ \frac{2 \cdot V_S}{\pi R_L}, \end{cases}$$
 for HWR schemes (A)  
for FBR or CTR schemes
- **RMS load current:** 
$$I_{LRMS} = \frac{V_{RLRMS}}{R_L} = \begin{cases} \frac{V_S}{2R_L}, \\ \frac{V_S}{\sqrt{2}R_L}, \end{cases}$$
 for HWR schemes (A)  
for FBR or CTR schemes

- Average diode rectified output current:**

$$I_{VD} = \begin{cases} I_{L_{AVG}}, & \text{for HWR schemes} \\ \frac{I_{L_{AVG}}}{2}, & \text{for FBR or CTR schemes} \end{cases} \quad (A)$$
- Peak repetitive forward output current:**

$$I_{VD_{max}} = \begin{cases} \frac{V_S}{R_L}, & \text{for HWR schemes} \\ \frac{V_S}{2R_L}, & \text{for FBR or CTR schemes} \end{cases} \quad (A)$$
- Voltage ripple factor:**

$$K_p = \sqrt{\left(\frac{V_{R_{L_{RMS}}}}{V_{R_{L_{AVG}}}}\right)^2 - 1} = \begin{cases} \sqrt{\left(\frac{\pi}{2}\right)^2 - 1} \approx 1.21, & \text{for HWR schemes} \\ \sqrt{\left(\frac{\pi}{2\sqrt{2}}\right)^2 - 1} \approx 0.48 & \text{for FBR or CTR schemes} \end{cases}$$
- Voltage ripple evaluated for the rectifier scheme:**

$$\Delta V_{R_L} = 2 \cdot K_p \cdot V_{R_{L_{AVG}}} = \begin{cases} \frac{2 \cdot V_S}{\pi} \sqrt{\left(\frac{\pi}{2}\right)^2 - 1} \approx \frac{2.48 \cdot V_S}{\pi} \approx 0.79 V_S, & \text{for HWR schemes} \\ \frac{4 \cdot V_S}{\pi} \sqrt{\left(\frac{\pi}{2\sqrt{2}}\right)^2 - 1} \approx \frac{1.92 \cdot V_S}{\pi} \approx 0.61 V_S & \text{for FBR or CTR schemes} \end{cases} \quad (V)$$

- **Source output resistance (overcurrent protection):**  $r_{on} = \frac{V_S}{I_{FSM}}$  (Ω)
- **Input rectifier resistance:**  $r_{IN} = \begin{cases} r_{vd} + r_{V_S}, & \text{for HWR or CTR schemes} \\ \textcolor{red}{2} \cdot r_{vd} + r_{V_S}, & \text{for FBR schemes} \end{cases}$  (Ω)
- **Diode opening state angle:**  $\theta = \begin{cases} 2 \cdot \sqrt[3]{3 \cdot \pi \cdot \frac{r_{IN}}{R_L}}, & \text{for HWR schemes} \\ 2 \cdot \sqrt[3]{\frac{3}{\textcolor{red}{2}} \cdot \pi \cdot \frac{r_{IN}}{R_L}}, & \text{for FBR or CTR schemes} \end{cases}$  (rad)
- **Average load voltage**  $V_{R_{L_{AVG}}} = V_S \cdot \cos\left(\frac{\theta}{2}\right) = \begin{cases} V_S \cdot \cos\left(\sqrt[3]{3 \cdot \pi \cdot \frac{r_{IN}}{R_L}}\right), & \text{for HWR schemes} \\ V_S \cdot \cos\left(\sqrt[3]{\frac{3}{\textcolor{red}{2}} \cdot \pi \cdot \frac{r_{IN}}{R_L}}\right), & \text{for FBR or CTR schemes} \end{cases}$  (V)
- **Average load current:**  $I_{L_{AVG}} = \begin{cases} \frac{1}{\pi \cdot r_{IN}} (V_S \cdot \sin\left(\frac{\theta}{2}\right) - V_{R_{L_{AVG}}} \cdot \frac{\theta}{2}), & \text{for HWR schemes} \\ \frac{\textcolor{red}{2}}{\pi \cdot r_{IN}} (V_S \cdot \sin\left(\frac{\theta}{2}\right) - V_{R_{L_{AVG}}} \cdot \frac{\theta}{2}), & \text{for FBR or CTR schemes} \end{cases}$  (A)

- Average diode current:

$$I_{VD} = \begin{cases} \frac{V_S}{R_L} \cdot \cos\left(\frac{\theta}{2}\right) = \frac{V_S}{R_L} \cdot \cos\left(\sqrt[3]{3 \cdot \pi \cdot \frac{r_{IN}}{R_L}}\right), & \text{for HWR schemes} \\ \frac{V_S}{2 \cdot R_L} \cdot \cos\left(\frac{\theta}{2}\right) = \frac{V_S}{2 \cdot R_L} \cdot \cos\left(\sqrt[3]{\frac{3}{2} \cdot \pi \cdot \frac{r_{IN}}{R_L}}\right), & \text{for FBR or CTR schemes} \end{cases} \quad (A)$$

- Maximum repetitive rectifier scheme diode current:

$$I_{VDmax} = \frac{V_S - V_{RLAVG}}{r_{IN}} \quad (A)$$

- Starting (Non-repetitive) maximum peak surge diode current in rectifier scheme:  $I_{VDON} = \frac{V_S}{r_{IN}}$

(A)

- Peak repetitive reverse voltage:

$$V_{VDmax} = \begin{cases} V_S + V_{RLAVG}, & \text{for HWR or CTR schemes} \\ \frac{V_S + V_{RLAVG}}{2}, & \text{for FBR schemes} \end{cases} \quad (V)$$

- Capacitance evaluation:

$$C = \begin{cases} \frac{I_{LAVG}}{2\pi f \cdot \Delta V_{RL}} (2\pi - \theta), & \text{for HWR schemes} \\ \frac{I_{LAVG}}{2\pi f \cdot \Delta V_{RL}} (\pi - \theta), & \text{for FBR or CTR schemes} \end{cases} \quad (F)$$

- Voltage ripple:


$$\Delta V_{RL} = \begin{cases} \frac{I_{LAVG}}{2\pi f \cdot C} (2\pi - \theta), & \text{for HWR schemes} \\ \frac{I_{LAVG}}{2\pi f \cdot C} (\pi - \theta), & \text{for FBR or CTR schemes} \end{cases} \quad (V)$$

- Voltage ripple factor

$$K_p = \frac{\Delta V_{RL}}{2V_{RLAVG}}$$

	$I_{VD_{AVG}}$	$I_{VD_{max}}$	$V_{VD_{max}}$	$r_{IN}$
Half - Wave rectifier (HWR)	$= I_{L_{AVG}}$	$\approx 7I_{L_{AVG}}$	$= V_S \cdot 2 \approx 3V_{R_{L_{AVG}}}$	$= r_{VD} + r_{V_S}$
Central Tap Rectifier (CTR)	$= \frac{I_{L_{AVG}}}{2}$	$\approx 3.5I_{L_{AVG}}$	$= V_S \cdot 2 \approx 3V_{R_{L_{AVG}}}$	$= r_{VD} + r_{V_S}$
Full bridge (Graetz) rectifier (FBR)	$= \frac{I_{L_{AVG}}}{2}$	$\approx 3.5I_{L_{AVG}}$	$= V_S \approx 1.5V_{R_{L_{AVG}}}$	$= 2r_{VD} + r_{V_S}$

**ITMO**

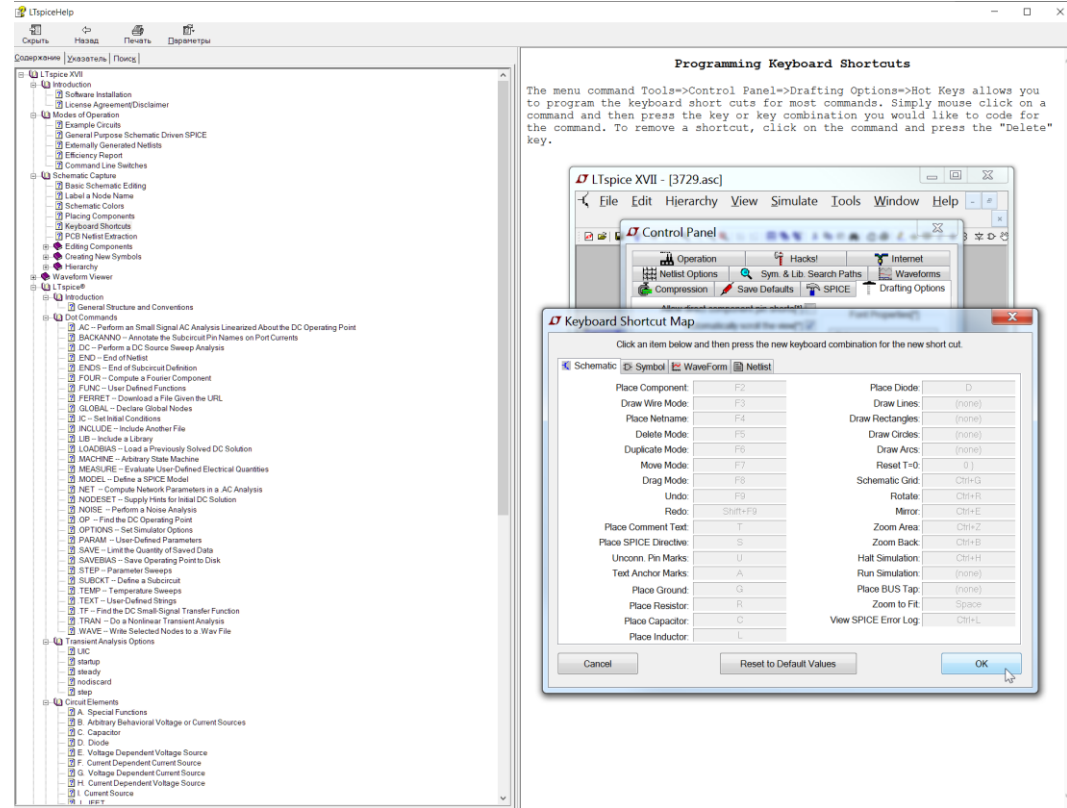

# Step Two: Lab1\_Rectifiers.asc

Specify your personal .lib file according to your variant

Right-click to edit:

.lib Variant\_No.lib

Simulation parameters:

SINE(0 {V\_s} {f} 0 0 90)

tran 0 {20/(f)} {10/(f)} {1/(200\*f)} uic

\*.step param R\_L list 100 1000 10000

\*.step param C\_real list 1n 1u 10u 100u

Element parameters for simulation:

K1 L1 L2 L3 1

\*=<https://cdk.ru/XqKtfl>\*

.param Vs = 10

.param f = 100

.param R\_L = 15k

.param R\_vs = 10

.param C\_real = 10u

.param Vs\_breakdown = 150

.param V\_s = Vs

Source Voltage:

Time step parameters:

Step for R\_load parameters

Step for C\_F parameter

Source voltage amplitude [V]

Source voltage frequency [Hz]

Load resistance [Ω]

Source output resistance (overcurrent protection) [Ω]:

Capacitor [F]

Source voltage amplitude [V] for breakdown

Specify your personal .lib file according to your variant

Right-click to edit:

.lib Variant\_No.lib

Simulation parameters:

Source Voltage:

Time step parameters:

Step for R\_load parameters

Step for C\_F parameter




SINE(0 {V\_s} {f} 0 0 90)  
tran 0 {20/(f)} {10/(f)} {1/(200\*f)} uic  
\*.step param R\_L list 100 1000 10000  
\*.step param C\_real list 1n 1u 10u 100u

Element parameters for simulation:

K1 L1 L2 L3 1  
\*=<https://cdk.ru/XqKtfl>\*

Source voltage amplitude [V]  
Source voltage frequency [Hz]  
Load resistance [Ω]  
Source output resistance (overcurrent protection) [Ω]  
Capacitor [F]  
Source voltage amplitude [V] for breakdown

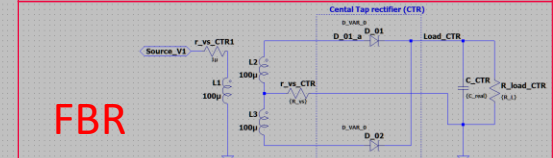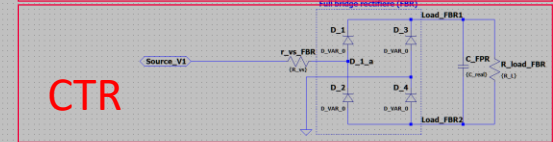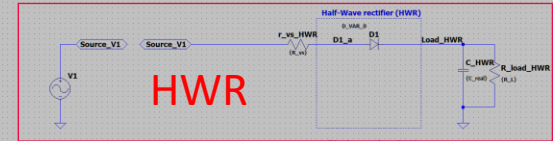.param Vs = 10  
.param f = 100  
.param R\_L = 15k  
.param R\_vs = 10  
.param C\_real = 10u  
.param Vs\_breakdown = 150  
.param V\_s = Vs



# Step Three: Variant data

```

Specify your personal .lib file according to your variant:
Right-click to edit: .lib Variant_No.lib


Simulation parameters:
Source Voltage: SINE(0 {V_s} {f} 0 0 90)
Time step parameters: .tran 0 {20/(f)} {10/(f)} {1/(200*f)} uic
Step for R_load parameters: *.step param R_L list 100 1000 10000
Step for C_F parameter: *.step param C_real list 1n 1u 10u 100u

Element parameters for simulation:
*****
Source voltage amplitude [V]
*****
Source voltage frequency [Hz]
*****
Load resistance [Ω]
*****
Source output resistance (overcurrent protection) [Ω]:
*****
Capacitor [F]
*****
Source voltage amplitude [V] for breakdown
*****
    
```

Variant #	Rectifier scheme	Source voltage amplitude, [V]	Load resistance, [Ω]	Desired DC voltage ripple factor	Source voltage frequency, [Hz]
	HWR-half-wave rectifier,	$V_s$			$f$
	CTR-central tap rectifier,				
	FBR - full bridge rectifier			$K_p$	
			$R_L$		



# Step Four: Simulation

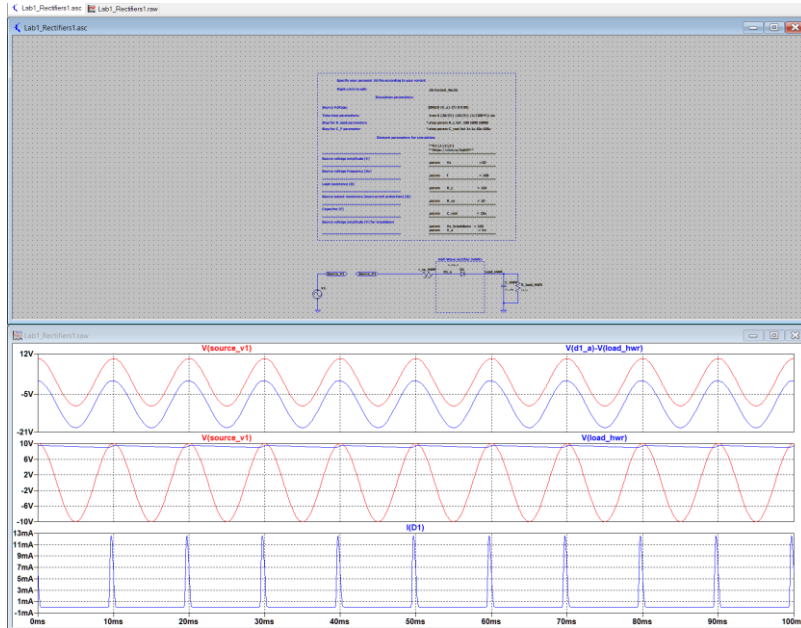

LTspice XVII - [Lab1\_Rectifiers1.asc]

File Edit Hierarchy View Simulate Tools Window Help

Lab1\_Rectifiers1.asc Lab1\_Rectifiers1.raw

Specify your personal .lib file according to your variant

Right-click to edit:

Simulation parameters:

Source Voltage:  $SINE(0 \text{ (V_s)} \{f\} 0 \text{ } 90)$

Time step parameters:  $.tran 0 \{20/(f)\} \{10/(f)\} \{1/(200*f)\} uic$

Step for R\_load parameters  $^*.step param R\_l list 100 1000 10000$

Step for C\_F parameter  $^*.step param C\_real list 1n 1u 10u 100u$

Element parameters for simulation:

\*\*\*\*\*K1 L1 L2 L3 L1 \*\*\*\*\*  
\*\*<https://cick.ru/XqKtfl>\*\*  
\*\*\*\*\*

Source voltage amplitude [V]  $.param \text{Vs} = 10$

Source voltage frequency [Hz]  $.param f = 100$

Load resistance [Ω]  $.param R\_l = 15k$

Source output resistance (overcurrent protection) [Ω]  $.param R\_vs = 10$

Capacitor [F]  $.param C\_real = 10u$

Source voltage amplitude [V] for breakdown  $.param \text{Vs\_breakdown} = 150$   
 $.param V\_s = \text{Vs}$

\*\*\*\*\*

Half-Wave rectifier (HWR)

Source\_V1 Source\_V1


$r_{vs\_HWR}$   $(X_{vs})$

$D1\_a$   $D1$

Load\_HWR

$C\_HWR$   $(C\_real)$

$R\_load\_HWR$   $(R\_l)$

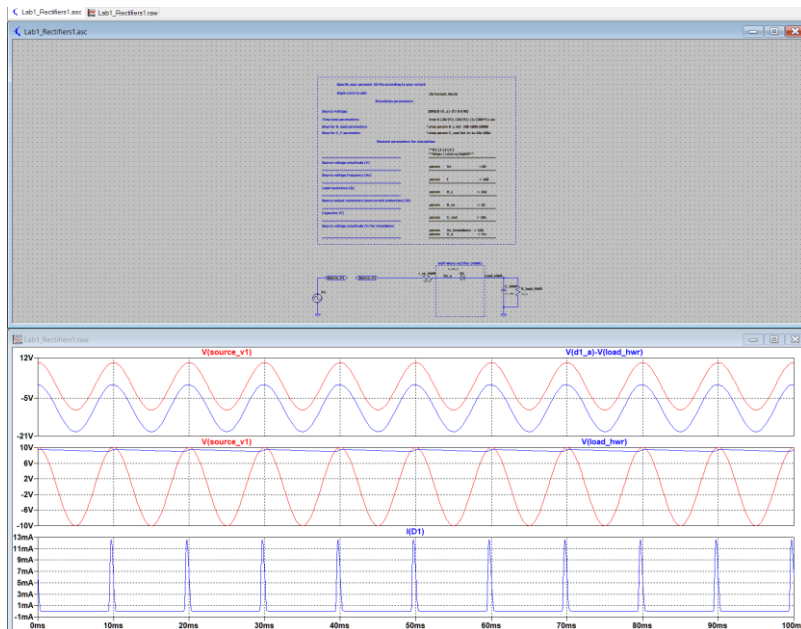

## LABORATORY WORK REPORT №1

2

### 1. Work purpose: to study parameters of semiconductor elements and basis of the semiconductor device design

Goals:

- 1) Design rectifier model on the basis of diode «diode name»
- 2) Simulate rectifier scheme and analyze dependencies of DC voltage ripple from load and filter capacitor values variation
- 3) Simulate overvoltage and overcurrent states (optional)

### 2. Starting data

#### 2.1.1. Parameters of the voltage source:

- One-phase sine voltage source
- Rectifier scheme: Half-Wave Rectifier (HWR) /Central tap rectifier (CTR) /Full -Bridge rectifier (FBR)

- Source voltage amplitude

$$V_s = \quad (\text{V})$$

- Source voltage frequency

$$f = \quad (\text{Hz})$$

#### 2.1.2. Diode: (copy the 1st and the second line of .lib file of your variant)

#### 2.1.3. Required parameters of DC output:


- Load resistance:

$$R_L = R_{\text{LOAD\_HWR\_CTR\_FBR}} = \quad (\text{V})$$

- Desired DC voltage ripple factor:

$$K_{\Delta} =$$

# Step Five: Results

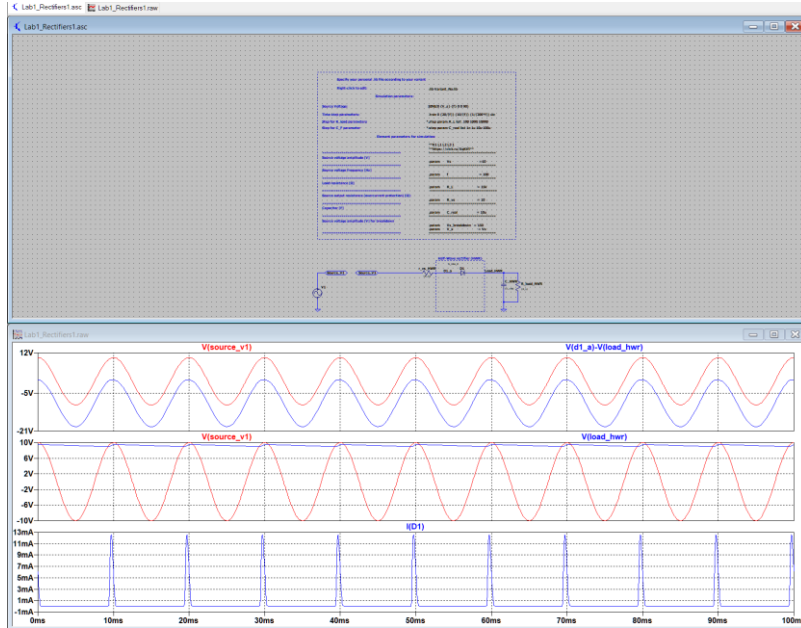

## 3. Simulation report

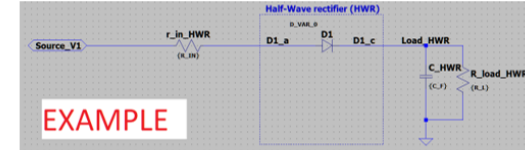


Fig. 3.1 – Rectifier scheme model

### 3.1.1. Filter parameters:

—  $C_{real} = 470$   $\mu F$

### 3.1.2. Load parameters:

—  $R_L = R_{LOAD\_HWR} = 667$   $\Omega$

—  $V_{RL\_AVG} = 23.676V$  (V)

—  $V_{RL\_RMS} = 23.679V$  (V)

—  $K_p = K_p = \frac{\Delta V_{RL}}{2V_{RL\_AVG}} =$

—  $I_{VDON} =$  (A)

—  $I_{VDmax} =$  (A)

—  $\Delta V_{RL} =$  (V)

## 3.2.Simulation results


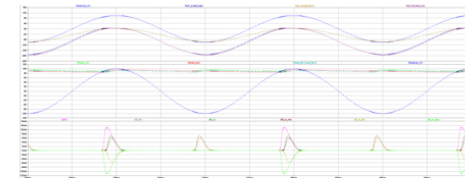


Fig 3.2 – Simulation results

# Step Five: Results

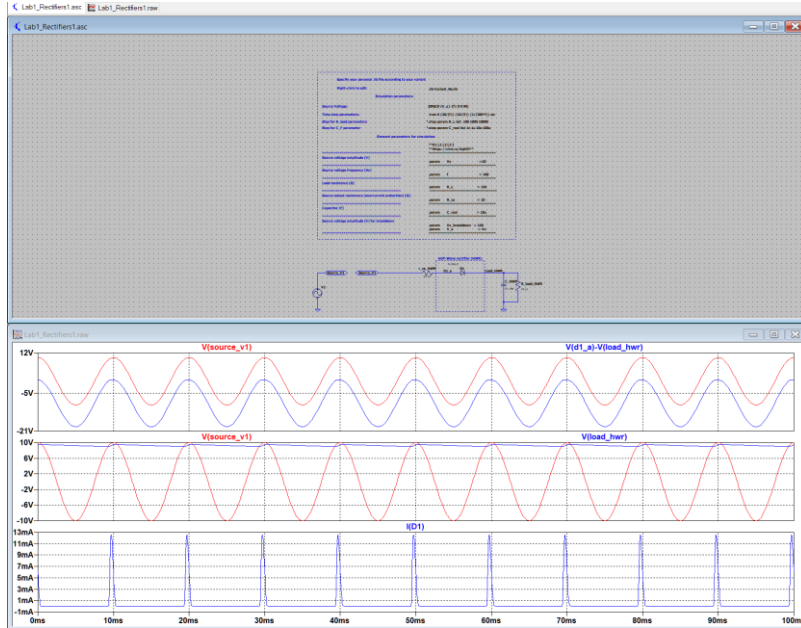

## LABORATORY WORK REPORT №1

4


### 3.2.1. Ripple factor:

Required:

$$- K_p = \underline{\hspace{10cm}}$$

Simulated with  $0.8 C_{real}$
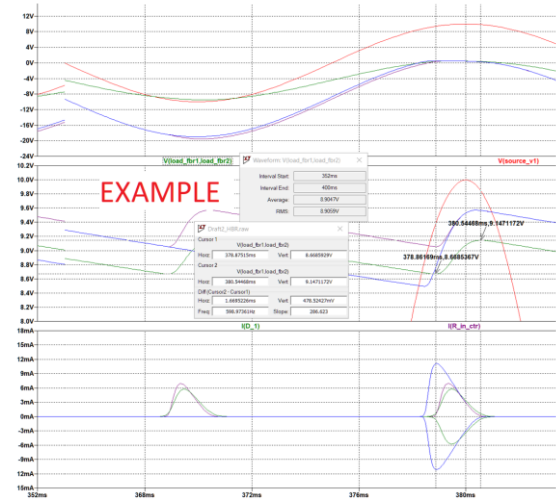
$$- K_{p\_EXP} = \underline{\hspace{10cm}}$$






b) Full-bridge rectifier

Fig 3.3 – Voltage ripple analysis

To define Average and RMS values use **CTRL+left** click mouse button on the signal name. Use **2-3 Voltage periods in the end of simulation interval**

Right-click with mouse on the signal name gives access to the signal cursor

# Step Five: Results

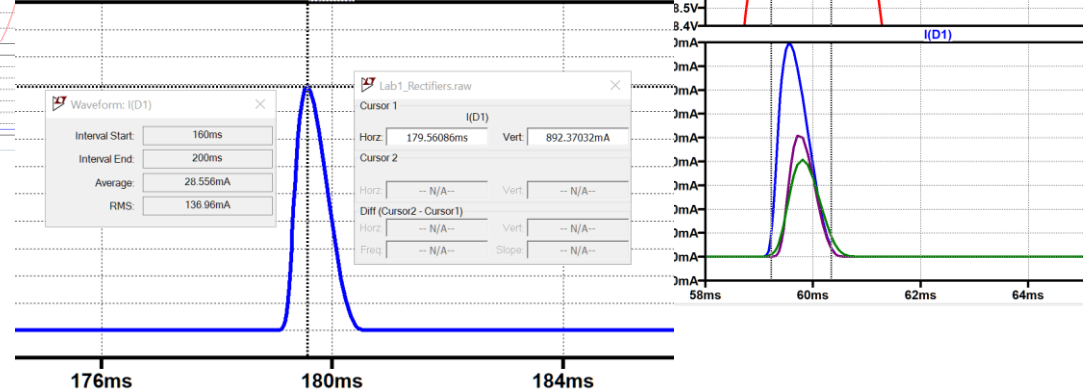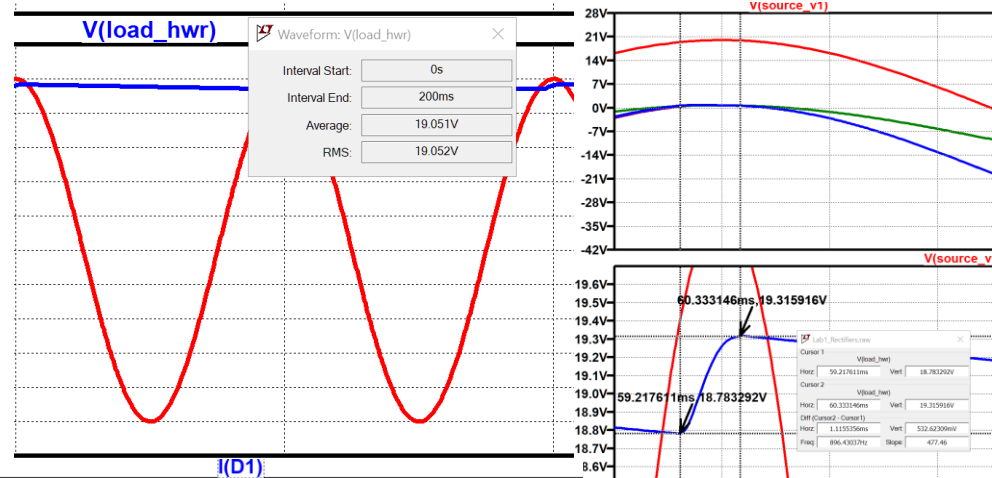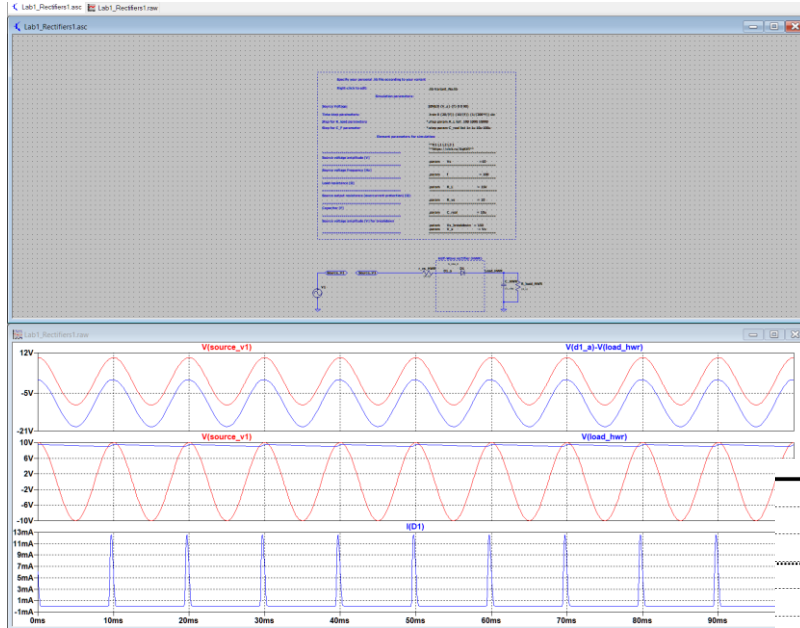



From equation of capacitor charge on the interval of  $\tau_1 < t < \tau_2 = T - \frac{\theta}{\omega}$

Capacitance evaluation:

$$C = \begin{cases} \frac{I_{L_{AVG}}}{2\pi f \cdot \Delta V_{RL}} (2\pi - \theta), & \text{for HWR schemes} \\ \frac{I_{L_{AVG}}}{2\pi f \cdot \Delta V_{RL}} (\pi - \theta), & \text{for FBR or CTR schemes} \end{cases} \quad (F)$$

Voltage ripple:
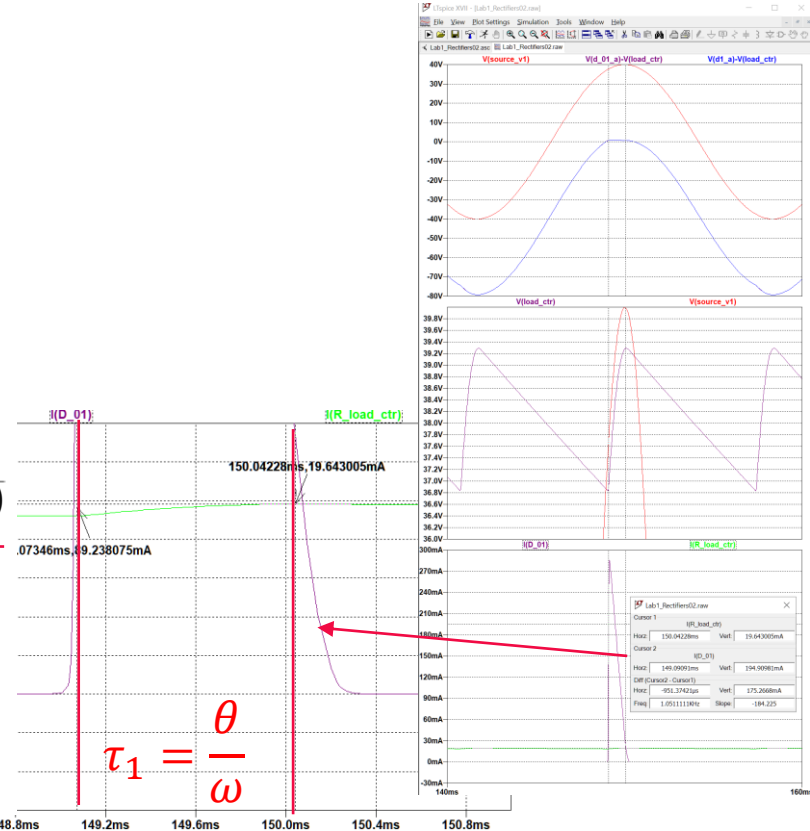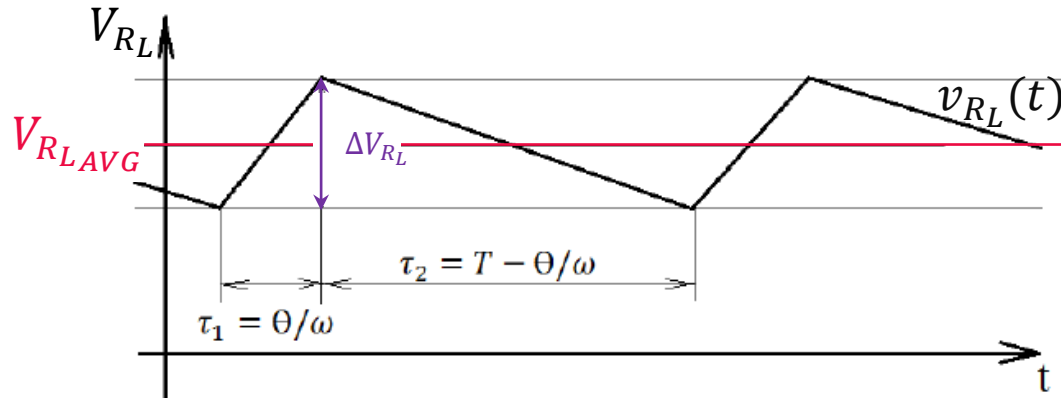
$$\Delta V_{RL} = \begin{cases} \frac{I_{L_{AVG}}}{2\pi f \cdot C} (2\pi - \theta), & \text{for HWR schemes} \\ \frac{I_{L_{AVG}}}{2\pi f \cdot C} (\pi - \theta), & \text{for FBR or CTR schemes} \end{cases} \quad (V)$$



From equation of capacitor charge on the interval of  $\tau_1 < t < \tau_2 = T - \frac{\theta}{\omega}$



Capacitance evaluation:

$$C = \begin{cases} \frac{I_{L_{AVG}}}{2\pi f \cdot \Delta V_{RL}} (2\pi - \theta), & \text{for HWR schemes} \\ \frac{I_{L_{AVG}}}{2\pi f \cdot \Delta V_{RL}} (\pi - \theta), & \text{for FBR or CTR schemes} \end{cases} \quad (F)$$

Voltage ripple:

$$\Delta V_{RL} = \begin{cases} \frac{I_{L_{AVG}}}{2\pi f \cdot C} (2\pi - \theta), & \text{for HWR schemes} \\ \frac{I_{L_{AVG}}}{2\pi f \cdot C} (\pi - \theta), & \text{for FBR or CTR schemes} \end{cases} \quad (V)$$

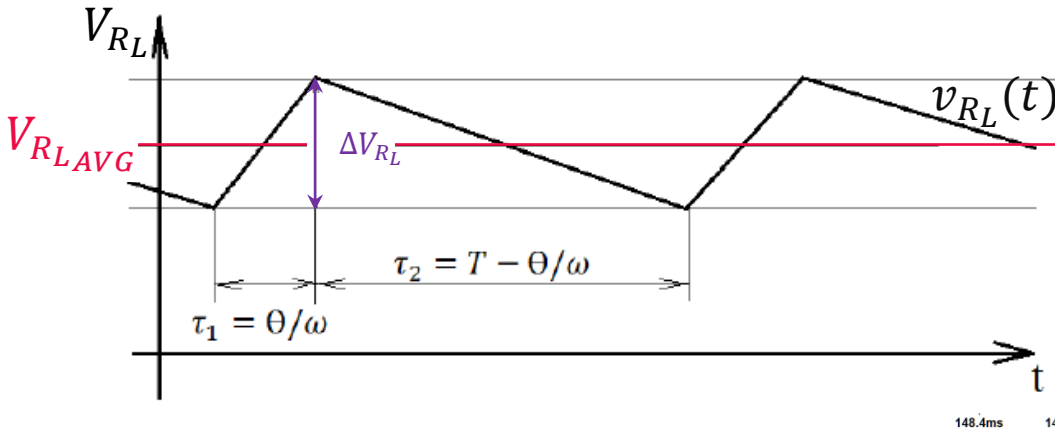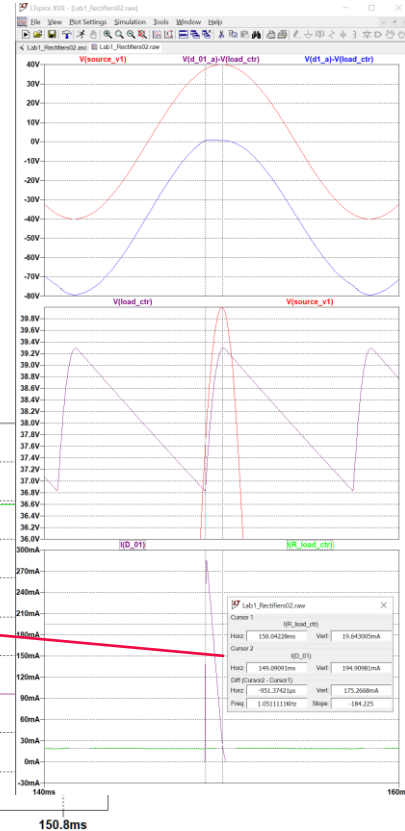If currents are less 1A it is better to use open -state current value at least 100mA to determine theta from simulation





## 3.2.2. Voltage ripple from simulation results¶

$$\begin{aligned} \rightarrow V_{RL_{AVG}^{exp}} &= \rightarrow (V) \\ \rightarrow V_{RL_{RMS}^{exp}} &= \rightarrow (V) \\ \rightarrow V_{RL_{max}} &= \rightarrow (V) \\ \rightarrow V_{RL_{min}} &= \rightarrow (V) \end{aligned}$$

$$\rightarrow \Delta V_{RL}^{exp} = V_{RL_{max}} - V_{RL_{min}} = \rightarrow (V)$$

## 3.2.3. Ripple factor¶

$$\begin{aligned} \rightarrow K_{pexp} &= \frac{\Delta V_{RL}^{exp}}{2 \cdot V_{RL_{AVG}^{exp}}} = \rightarrow \\ K_{pRMS} &\approx \sqrt{\left(\frac{\Delta V_{RL}/2\sqrt{3}}{V_{RL_{AVG}}}\right)^2} = \sqrt{\left(\frac{V_{RL_{RMS}}}{V_{RL_{AVG}}}\right)^2 - 1} \end{aligned}$$

## 3.2.4. Diode opening state angle:¶

$$\begin{aligned} \rightarrow \tau_1 &= \rightarrow (s) \\ \rightarrow \theta_{exp} &= \tau_1 \cdot f \cdot 2\pi = \frac{\tau_1}{T} \cdot 2\pi = \rightarrow (rad) \end{aligned}$$

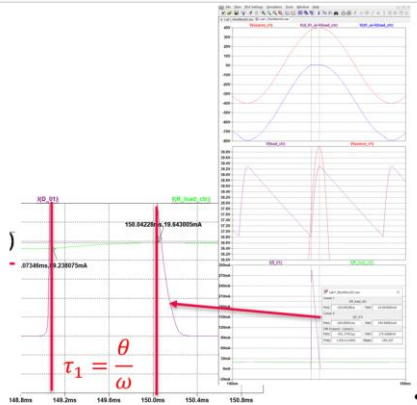


Fig 3.4 –  $\theta_{exp}$  angle definition from simulation results¶  
(It is recommended to consider diode open state at current level 0.05-0.1 A or determine theta on the capacitor charging interval)¶

## LABORATORY WORK REPORT №1

6

## 3.2.6. Starting (Non-repetitive) maximum peak surge diode current in rectifier scheme

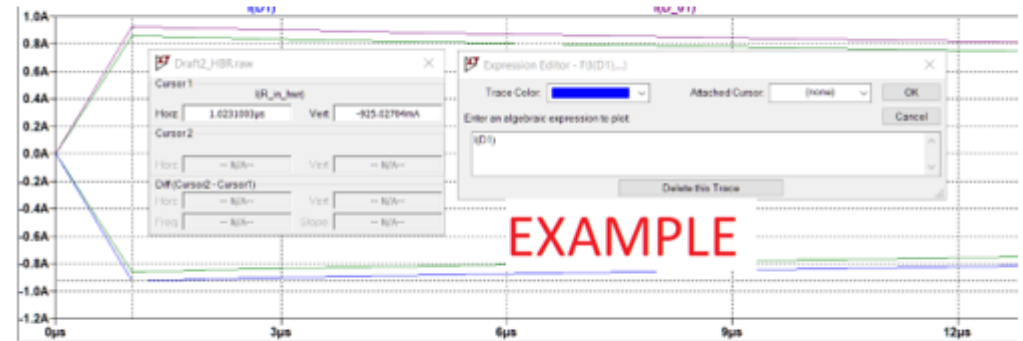


Fig 3.5 –Starting current

$$I_{VDONexp} = 2.493 \quad (A)$$



## Conclusions should contain:

- 1) Diode check results:
  - Is breakdown voltage check passed? /Is voltage source changed because of overvoltage?
  - Is starting current check passed? /Is additional resistance  $r_{vs}$  added to prevent overcurrent in diode/capacitor?
- 2) Capacitor information: nominal value, tolerance, allowed current
- 3) Provided ripple factor value

Conclusion should contain:

- 1) Diode check results:
  - Is breakdown voltage check passed? /Is voltage source changed because of overvoltage?
  - Is starting current check passed? /Is additional resistance  $r_{vs}$  added to prevent overcurrent in diode/capacitor?
- 2) Capacitor information: nominal value, tolerance, allowed current
- 3) Provided ripple factor value

If there are no conclusion or some parts of conclusion is missing – the score will be reduced by 1 point of 3

- Evaluations (pp 4.2-4.6. of the report are not obligatory, it's optional).
- It is better to delete this parts from the report, if you didn't fulfill this parts
- However, if you do optional parts with mistakes, were will be penalty for that, and you will have no extra points while fixes won't be done.

If there are no conclusion or some parts o conclusion is missing – the score will be reduced by 1 point of 3



# **ITMO**

## **Practice task 1**

### **Simple semiconductor device circuits design**

**Nikolay Nikolaev**


([nanikolaev@itmo.ru](mailto:nanikolaev@itmo.ru))

**Nikolai Poliakov**

([polyakov\\_n\\_a@itmo.ru](mailto:polyakov_n_a@itmo.ru))

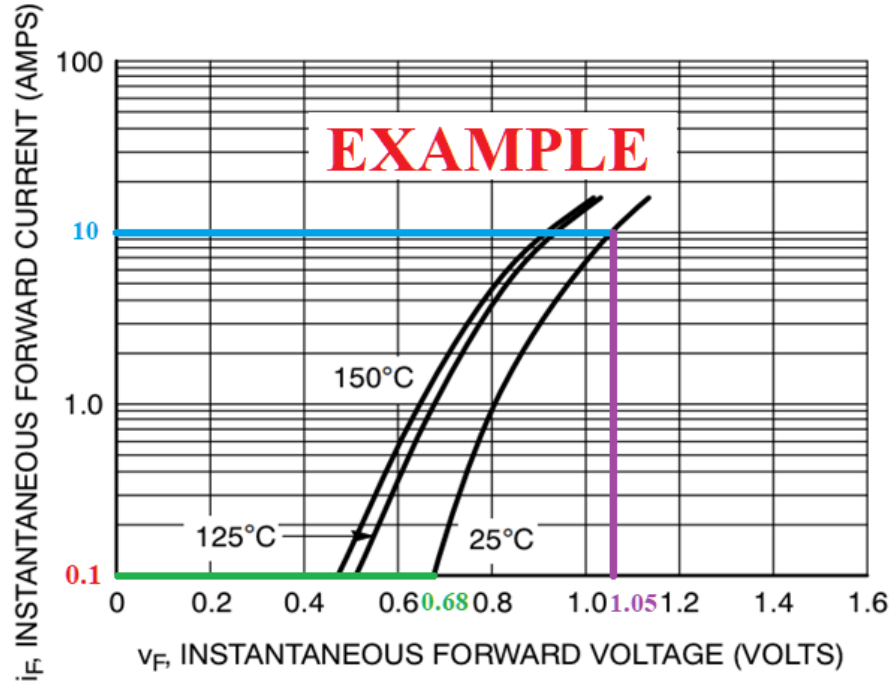**Roman Olekhnovich**

([r.o.olekhnovich@mail.ru](mailto:r.o.olekhnovich@mail.ru))



Maximum repetitive peak surge forward current

$$I_{fwd\_imp} = 10 \quad (A)$$

Diode forward bias voltage

$$V_{fwd\_max}(I_{fwd\_imp}) = 1.05 \quad (V)$$


Diode threshold voltage:

$$v_{ON} = 0.68 \quad (V)$$

Diode active resistance:



$$r_{VD} = \frac{V_{fwd\_max} - v_{ON}}{I_{fwd\_imp} - I_{fwd}(v_{ON})} = \quad (\Omega)$$

# Diode active resistance

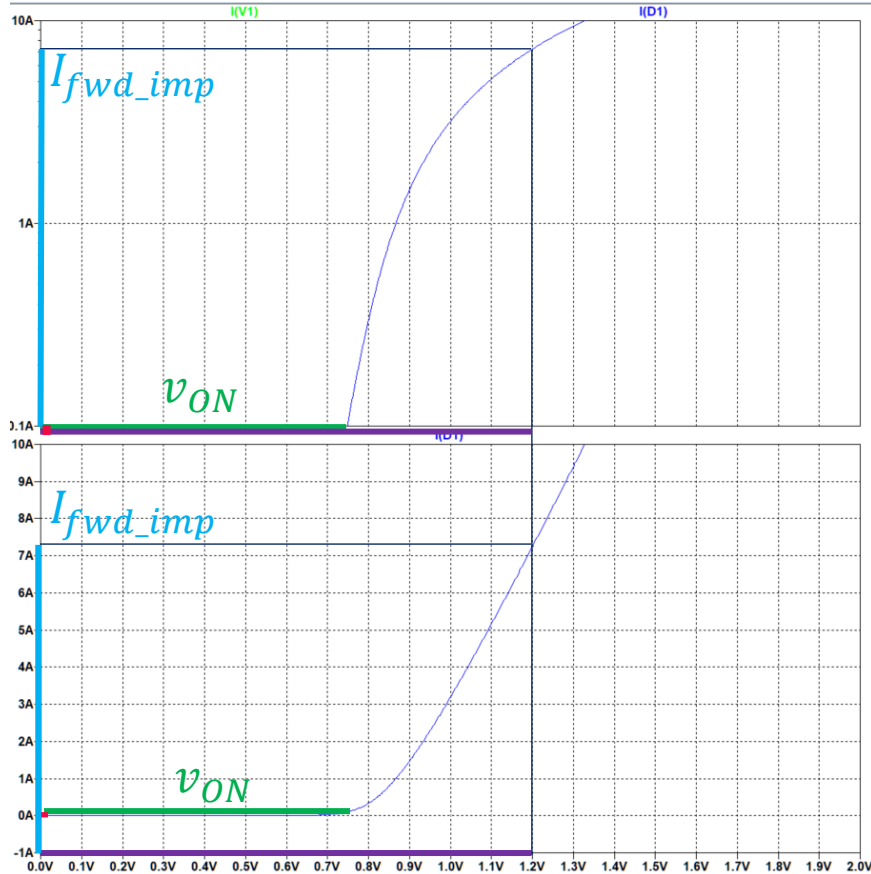


Diode active resistance:
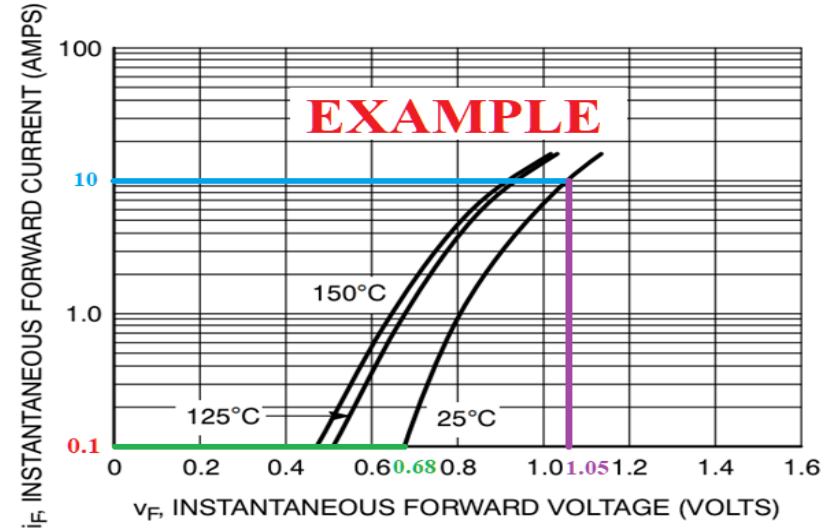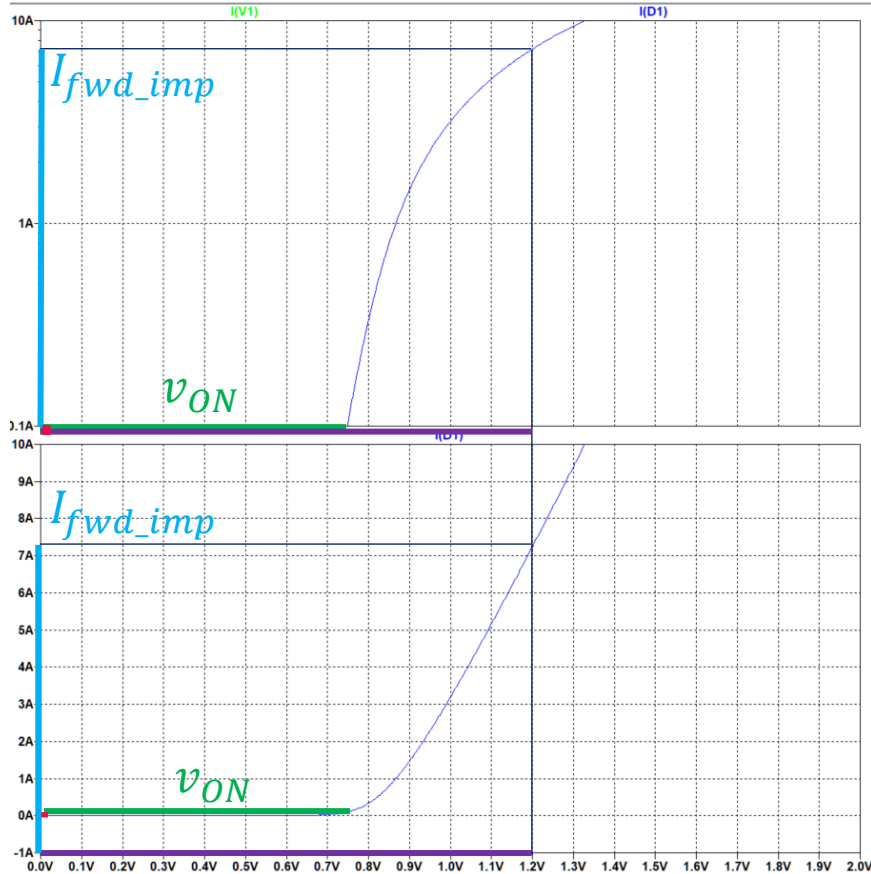
$$r_{VD} = \frac{V_{fwd\_max} - v_{ON}}{I_{fwd\_imp} - I_{fwd}(v_{ON})} \quad (\Omega)$$



Diode current at starting conduct state:

$$I_{fwd}(v_{ON}) = \quad (\Omega)$$

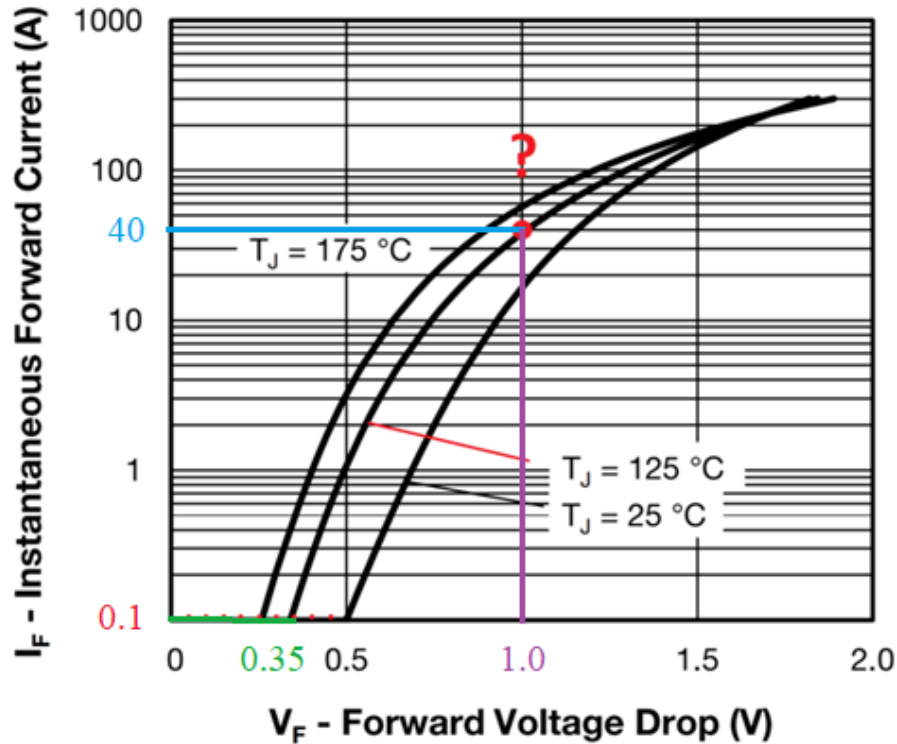

Maximum repetitive peak surge forward current

$$I_{fwd\_imp} = 40 \quad (\text{A})$$

Diode forward bias voltage

$$V_{fwd\_max}(I_{fwd\_imp}) = 1.0 \quad (\text{V})$$

Diode threshold voltage:


$$v_{ON} = 0.35 \quad (\text{V})$$

Diode active resistance:

$$r_{VD} = \frac{V_{fwd\_max} - v_{ON}}{I_{fwd\_imp} - I_{fwd}(v_{ON})} \quad (\Omega)$$
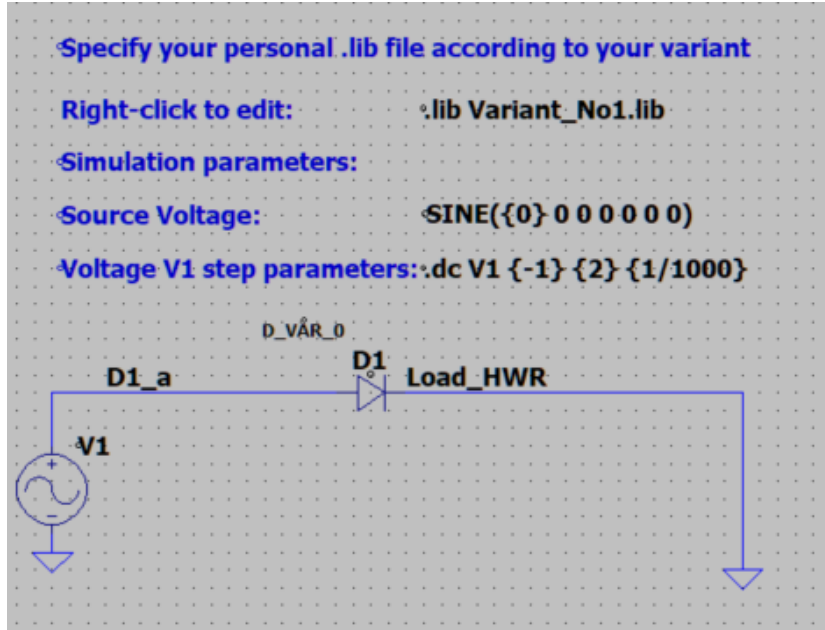
$$r_{VD} = \frac{1 - 0.35}{40 - 0.1} = 0.0163 \, \Omega$$





Maximum repetitive peak surge forward current

$$I_{fwd\_imp} = \quad (A)$$

Diode forward bias voltage

$$V_{fwd\_max}(I_{fwd\_imp}) = \quad (V)$$


Diode threshold voltage:

$$v_{ON} = \quad (V)$$

Diode active resistance:

$$r_{VD} = \frac{V_{fwd\_max} - v_{ON}}{I_{fwd\_imp} - I_{fwd}(v_{ON})} \quad (\Omega)$$

$$r_{VD} = - = \quad \Omega$$

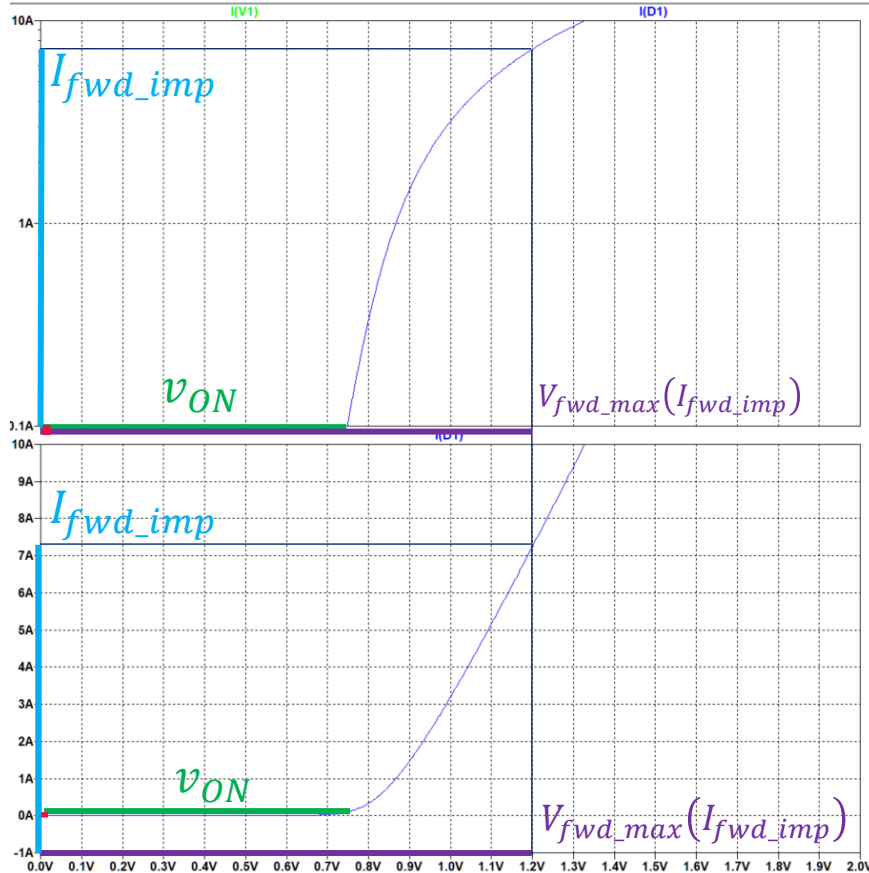

Maximum repetitive peak surge forward current

$$I_{fwd\_imp} = 7 \quad (A)$$

Diode forward bias voltage

$$V_{fwd\_max}(I_{fwd\_imp}) = 1.2 \quad (V)$$

Diode threshold voltage:



$$v_{ON} = 0.75 \quad (V)$$

Diode active resistance:

$$r_{VD} = \frac{V_{fwd\_max} - v_{ON}}{I_{fwd\_imp} - I_{fwd}(v_{ON})} \quad (\Omega)$$

$$r_{VD} = \frac{1.2 - 0.75}{7 - 0.1} = 0,065 \, \Omega$$

# Diode active resistance

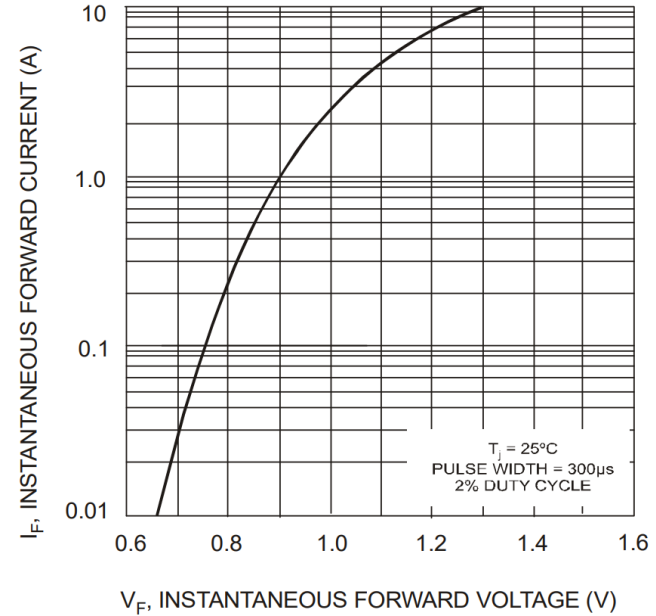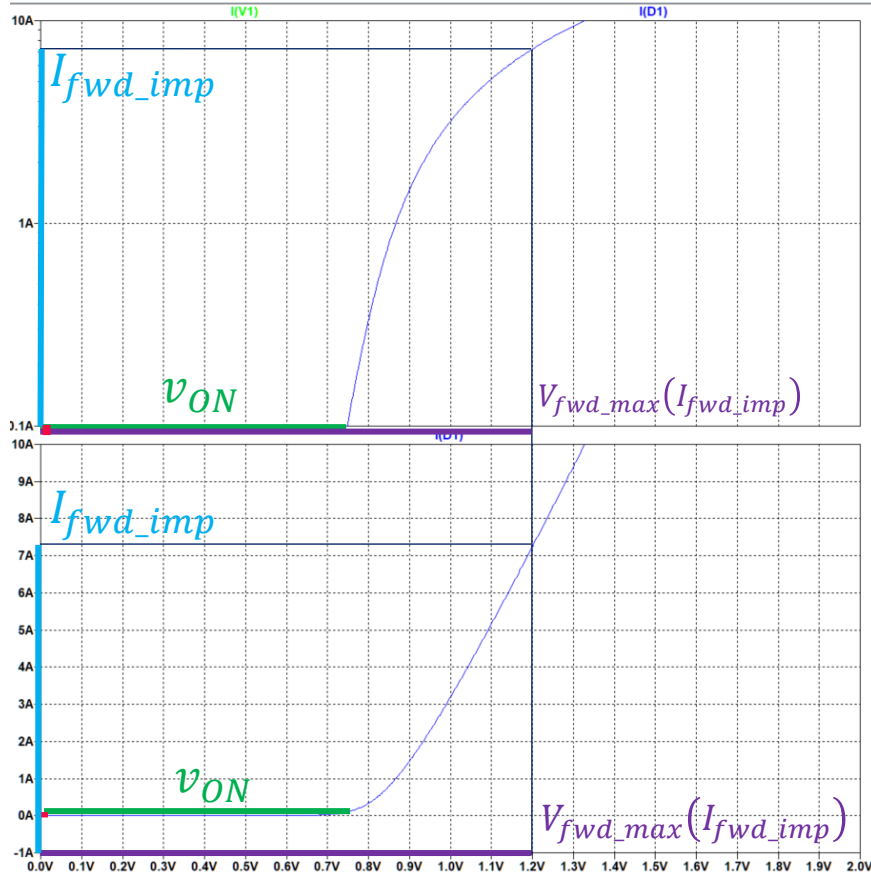

## Stage III. Practice Report

Save your final LT SPICE model and upload here .zip file with your .asc file (this is optional)

[Загрузить](#) До 20 файлов (общий размер — до 20 МБ)

\* Save a screenshot of your LTSPICE schematic





[Загрузить](#) До 20 файлов (общий размер — до 20 МБ)


\* Save a screenshot of your simulation results

[Загрузить](#) До 20 файлов (общий размер — до 20 МБ)

Your  $v_{on}$  result from LT Spice

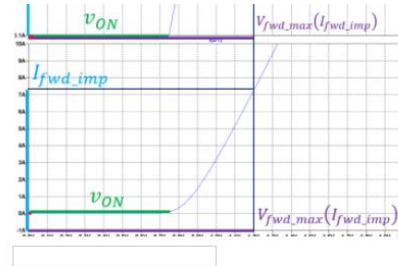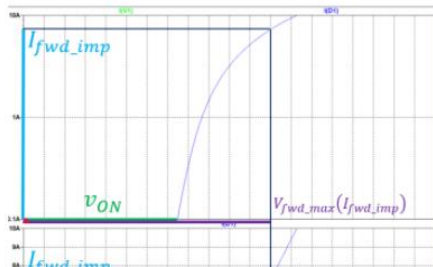

Your  $r_{vd}$  result from LT Spice

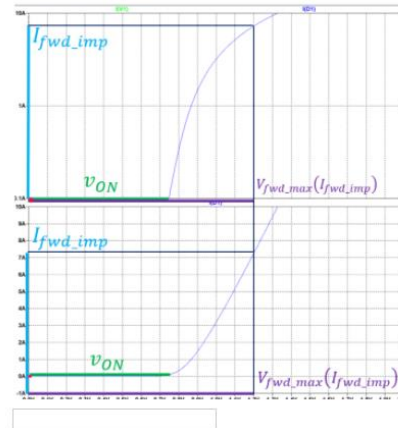

[Назад](#)

[Далее](#)

The background is a dark purple grid. In the top right corner, there is a wavy white line that curves downwards and to the right. In the bottom left corner, there is a similar wavy white line that curves upwards and to the right.

**iTMO**

**Thank you for your attention!**